

## Chapter 5 – Arithmetic Operations and the ALU

The subject for this chapter is the ALU (Arithmetic Logic Unit) of a typical stored program computer. This chapter, by necessity, includes materials on binary addition (half adders, full adders, and several parallel adders), binary subtraction, binary shifting, and binary multiplication as implemented by a simplistic algorithm. In this chapter, we shall reserve the plus symbol “+” for addition and the multiplication symbol “•” for that operation.

As an extension of the arithmetic operations, we shall consider the basic logical operations of the ALU. While some textbooks include a discussion of floating-point arithmetic in a chapter such as this, we note the common practice of assigning all such operations to a coprocessor.

The first thing to note in this chapter is that we are contemplating a significant leap in our reasoning, one that normally merits very little mention in most textbooks. We are planning to use the tools of Boolean algebra in the service of binary arithmetic. But arithmetic and Boolean algebra are completely different topics, built on completely different axiomatic bases.

Despite these significant theoretical differences, there is a mapping between Boolean algebra and binary arithmetic that allows the use of Boolean digital gates in arithmetic circuits. We shall investigate this mapping in the form of truth tables (from Boolean algebra) for two types of addition in binary arithmetic.

### Review of Basic Addition

Consider the decimal number 139. To be precise, this is not a number but a collection of symbols each used to represent a number. We know that the digit “1” represents the number 1, the digit “3” represents the number 3, and the digit “9” represents the number 9. The association of the character string “139” with the number 139 is based on **positional notation**, which states that  $139 = 1 \bullet 100 + 3 \bullet 10 + 9 \bullet 1 = 1 \bullet 10^2 + 3 \bullet 10^1 + 9 \bullet 10^0$ .

The above example assumes decimal (base 10) notation, which is the notation most commonly used by humans for representing integers. In our studies of digital computers, we must consider not only decimal numbers but also binary (base 2), octal (base 8) and hexadecimal (base 16). It is conventional to represent the base of every number system as a decimal number. Any other approach would lead to considerable confusion.

In a positional number system, the value of a string of digits is expressed in terms of powers of the base B. Consider the four-digit number, denoted in the abstract as  $D_3D_2D_1D_0$ . The value of this number is given by  $D_3 \bullet B^3 + D_2 \bullet B^2 + D_1 \bullet B^1 + D_0 \bullet B^0$ . For example, consider the number 1101. The value of this number depends on the base of the number system.

In decimal notation, we have  $1 \bullet 10^3 + 1 \bullet 10^2 + 0 \bullet 10^1 + 1 \bullet 10^0 = 1 \bullet 1000 + 1 \bullet 100 + 0 \bullet 10 + 1 \bullet 1 = 1000 + 100 + 1 = 1101_{10}$ .

In octal numbers (base 8), we have

$$1101_8 = 1 \bullet 8^3 + 1 \bullet 8^2 + 0 \bullet 8^1 + 1 \bullet 8^0 = 1 \bullet 512 + 1 \bullet 64 + 0 \bullet 8 + 1 \bullet 1 = 577_{10}$$

In hexadecimal numbers (base 16), we have

$$1101_{16} = 1 \bullet 16^3 + 1 \bullet 16^2 + 0 \bullet 16^1 + 1 \bullet 16^0 = 1 \bullet 4096 + 1 \bullet 256 + 0 \bullet 16 + 1 \bullet 1 = 4453_{10}$$

In binary numbers (base 2), we have

$$1101_2 = 1 \bullet 2^3 + 1 \bullet 2^2 + 0 \bullet 2^1 + 1 \bullet 2^0 = 1 \bullet 8 + 1 \bullet 4 + 0 \bullet 2 + 1 \bullet 1 = 13_{10}$$

To motivate our discussion of binary addition, let us first look at decimal addition. Consider the sum  $15 + 17 = 32$ . In the standard form in which most of us learned addition, the problem would be stated as follows:

$$\begin{array}{r} 15 \\ + 17 \\ \hline 32 \end{array}$$

First, note that  $5 + 7 = 12$ . In order to speak of binary addition, we must revert to a more basic way to describe  $5 + 7$ ; we say that the sum is 2 with a **carry-out** of 1. Consider the sum  $1 + 1$ , which is known to be 2. However, the correct answer to our simple problem is 32, not 22, because in computing the sum  $1 + 1$  we must consider the **carry-in** digit, here a 1. With that in mind, we show two addition tables – for a half-adder and a full-adder. The half-adder table is simpler as it does not involve a carry-in. The following table considers the sum and carry from  $A + B$ .

#### Half-Adder $A + B$

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Note the last row where we claim that  $1 + 1$  yields a sum of zero and a carry of 1. This is similar to the statement in decimal arithmetic that  $5 + 5$  yields a sum of 0 and carry of 1 when  $5 + 5 = 10$ .

Remember that when the sum of two numbers equals or exceeds the value of the base of the numbering system (here 2) that we decrease the sum by the value of the base and generate a carry. Here the base of the number system is 2 (decimal), which is  $1 + 1$ , and the sum is 0. Say “One plus one equals two plus zero:  $1 + 1 = 10$ ”.

For us the half-adder is only a step in the understanding of a full-adder, which implements binary addition when a carry-in is allowed. We now view the table for the sum  $A + B$ , with a carry-in denoted by  $C$ . One can consider this  $A + B + C$ , if that helps.

#### Full-Adder: $A + B$ with Carry

A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

As an example, we shall consider a number of examples of addition of four-bit binary numbers. The problem will first be stated in decimal, then converted to binary, and then done. The last problem is introduced for the express purpose of pointing out an error. We shall see in a minute that four-bit binary numbers can represent decimal numbers in the range 0 to 15 inclusive. Here are the problems, first in decimal and then in binary.

- 1)  $6 + 1$              $0110 + 0001$
- 2)  $11 + 1$             $1011 + 0001$
- 3)  $13 + 5$             $1101 + 0101$

0110	1011	1101	In the first sum, we add 1 to an even number. This is quite easy to do. Just change the last 0 to a 1. Otherwise, we may need to watch the carry bits.
<u>0001</u>	<u>0001</u>	<u>0101</u>	
0111	1100	0010	

In the second sum, let us proceed from right to left.  $1 + 1 = 0$  with carry = 1. The second column has  $1 + 0$  with carry-in of 1 = 0 with carry-out = 1. The third column has  $0 + 0$  with a carry-in of 1 = 1 with carry-out = 0. The fourth column is  $1 + 0 = 1$ .

Analysis of the third sum shows that it is correct bit-wise but seems to be indicating that  $13 + 5 = 2$ . This is an example of “busted arithmetic”, more properly called overflow. A give number of bits can represent integers only in a given range; here  $13 + 5$  is outside the range 0 to 15 inclusive that is proper for four-bit numbers.


### Back to the Half-Adder

The half-adder may be seen as adding the units column in integer addition; there is no carry-in. As we shall see later, it is often convenient to replace a half-adder with a full-adder in which the carry-in is set to 0. The two are equivalent. Here again is the truth table.


A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

What the last row says is simple. In decimal,  $1 + 1$  is 2. But 2 is the basis of the binary system, so we have to say that  $1 + 1 = 1 \cdot 2^1 + 0 \cdot 2^0$ ; in other words, the sum is 0 and the carry-out is 1. This is similar to what might be said in decimal arithmetic;  $5 + 5$  is really 10, but we might say that the sum is 0 and the carry-out is 1,

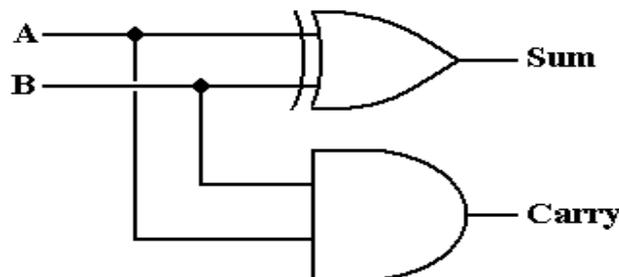The simplest circuit implementation of a half-adder involves an AND gate and a XOR gate.



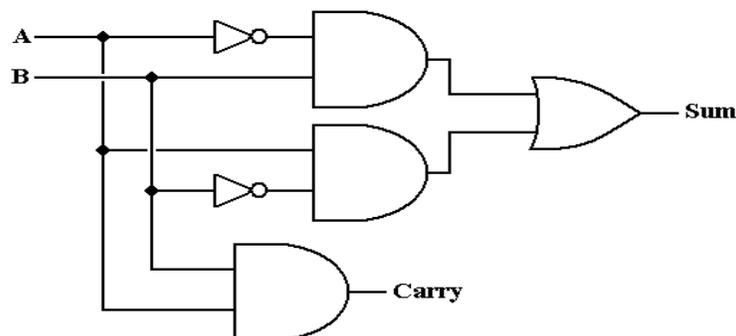An equivalent implementation is shown in order to facilitate discussion of the full-adder.



Back to the Full-Adder

The full-adder might be seen as equivalent to the tens or hundreds column in standard addition; there must be provision for a carry-in from the column to the right. Here again is the truth table for the full adder with an additional column giving comments.

A	B	C <sub>in</sub>	Sum	C <sub>out</sub>	Result = 2 • C <sub>out</sub> + 1 • Sum
0	0	0	0	0	0 = 2 • 0 + 1 • 0
0	0	1	1	0	1 = 2 • 0 + 1 • 1
0	1	0	1	0	1 = 2 • 0 + 1 • 1
0	1	1	0	1	2 = 2 • 1 + 1 • 0
1	0	0	1	0	1 = 2 • 0 + 1 • 1
1	0	1	0	1	2 = 2 • 1 + 1 • 0
1	1	0	0	1	2 = 2 • 1 + 1 • 0
1	1	1	1	1	3 = 2 • 1 + 1 • 1


A bit of Boolean algebra will show that the Sum and Carry (out) can be represented as:

$$\begin{aligned}\text{Sum} &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\ \text{Carry} &= \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC\end{aligned}$$

A bit more Boolean algebra will result in the following simplification of the second expression.


$$\text{Carry} = AB + AC + BC$$

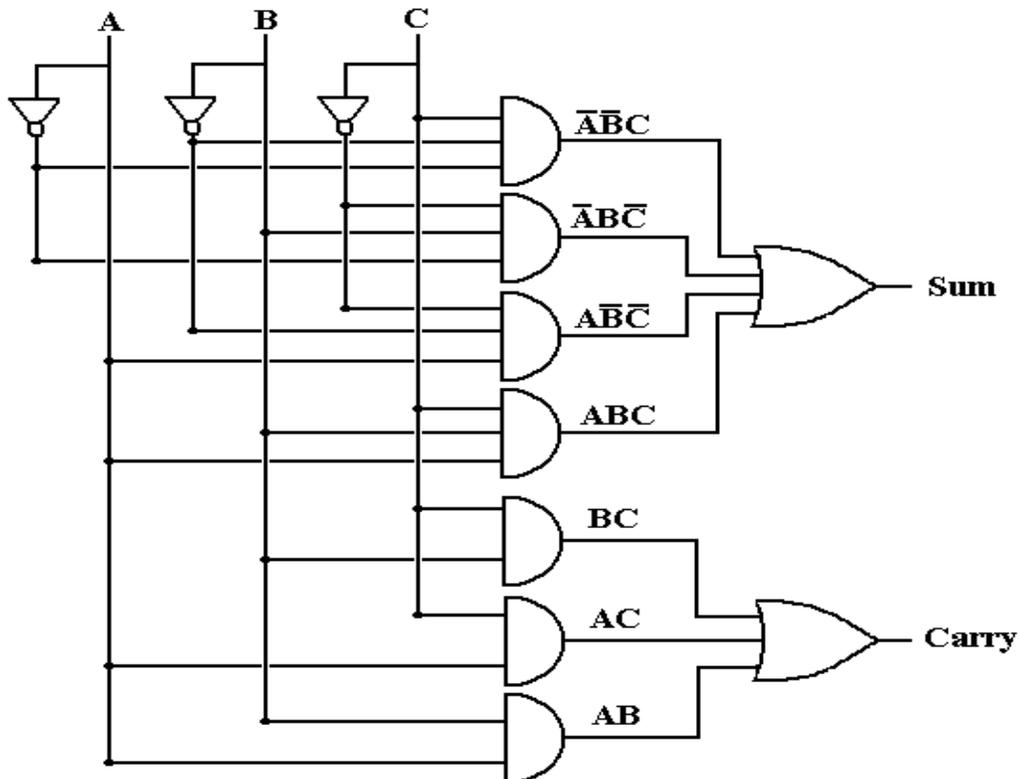Here is the circuit implementing these two expressions.



This is the standard implementation of a full-adder. There is another worth mention.

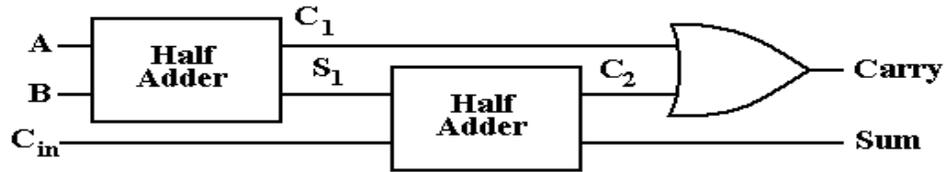This second implementation of a full-adder appears in the text by Rob Williams. It uses two half-adders and an OR gate. Here is the circuit.



First, we must show that the circuit does indeed function as a full-adder. This is done using a truth table. Note a column for each intermediate result. This is a full-adder.


A	B	$C_{in}$	$C_1$	$S_1$	$C_2$	Carry	Sum
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	1
0	1	0	0	1	0	0	1
0	1	1	0	1	1	1	0
1	0	0	0	1	0	0	1
1	0	1	0	1	1	1	0
1	1	0	1	0	0	1	0
1	1	1	1	0	0	1	1

A simple way to confirm that this is the truth table of a full-adder is to count the number of 1's in the triple  $(A, B, C_{in})$ . If the count is odd (1 or 3) the sum is 1, otherwise the sum is 0. If the count is 2 or more, the carry is 1, otherwise the carry is 0.

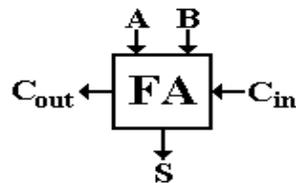
### The Complete Full-Adder

We have just considered a full adder for two one-bit numbers with a carry-in (from somewhere). We now extend the idea to multiple bit binary numbers. Typical examples include 8, 16, 32, and 64 bit numbers. Our example will focus on four bit numbers. We add two four bit numbers  $(A_3, A_2, A_1, A_0)$  and  $(B_3, B_2, B_1, B_0)$ .

We begin with the block diagram of a full-adder. Following standard practice in the study of computer organization and architecture, once the inner details of a circuit have been mastered, we no longer show them, but show the circuit as a single block.



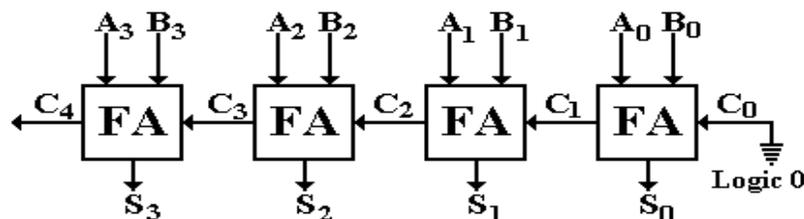We now extend this design to a four-bit parallel adder. This design is the logical basis for the adder in a modern ALU. It is too slow for actual use.



Recall that the “units bit” addition with  $A_0$  and  $B_0$  could have been implemented as a half-adder. For reasons that will appear shortly, this was implemented as a full-adder with the carry input tied to logic 0, here 0 volts (represented by the ground symbol).

This is called a “ripple carry” adder in that the carry bit ripples from right to left. Each full-adder has a time delay before the carry-out bit is valid. Consider  $FA_1$ , the one with inputs  $A_1$ ,  $B_1$ , and  $C_1$ . The input  $C_1$  does not become valid until some time after the inputs to  $FA_0$ ,  $A_0$  and  $B_0$  become valid. Another delay ensues before the outputs  $S_1$  and  $C_1$  are valid.

For details on the timing of a full-adder and a ripple carry adder, please refer to this author’s textbook on Computer Architecture.

### Binary Subtraction


We shall use a full-adder to perform binary subtraction by following the standard rule from arithmetic:  $A - B = A + (-B)$ . We just need to negate one of the inputs to the full-adder and we have a subtractor. How do we do that?

All modern Arithmetic Logic Units implement integer arithmetic using the two’s-complement form. Thus we need to build a two’s-complement negator. As an aside, we note that it is possible to build an adder/subtractor for other formats, but that these designs are quite complex. It is the simplicity of the standard two’s-complement unit that lead to its being the standard.


Remember the rule for negating an integer in two’s-complement arithmetic: take the one’s-complement and add one. As an expression, this is as follows:

$$-B = \overline{B} + 1$$

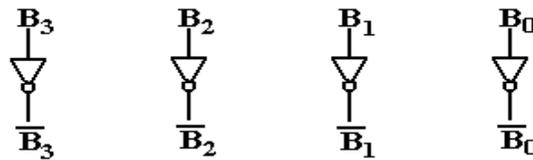But recall that taking the one’s-complement of a binary number is exactly the same as taking the logical NOT of each of its bits. Here is the case for the 4-bit number  $B_3B_2B_1B_0$ . We begin with a circuit to produce the one’s-complement of the number.



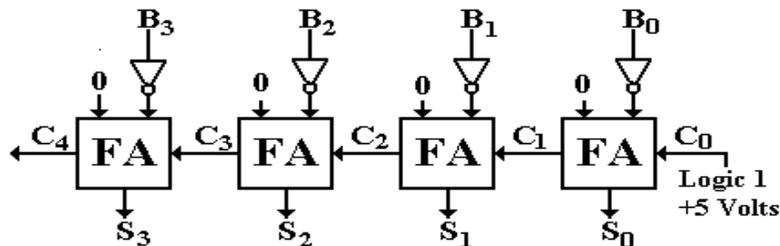In order to get the negative of the number, all we need to do is add 1 to it. Of the several ways this could be done, the best way is to set the carry-in of the units full-adder to 1.




Consider the following positive 4-bit number.  $B = 0100$   
 Take the one’s complement to get this number  $1011$   
 Add one to the number to get the true negative  $1100$

If the left input to each FA had been the bit values of  $A$ , we would have  $(A - B)$ . Now we try to convert this into a unit that will add or subtract.

In order to build the unit, we need a circuit element that can generate either the plain version of its input or the one's-complement of its input. But we have exactly that in the XOR gate. Here is the truth table for the XOR circuit, with two inputs: B and S (select).

B	S	$B \oplus S$
0	0	0
1	0	1
0	1	1
1	1	0

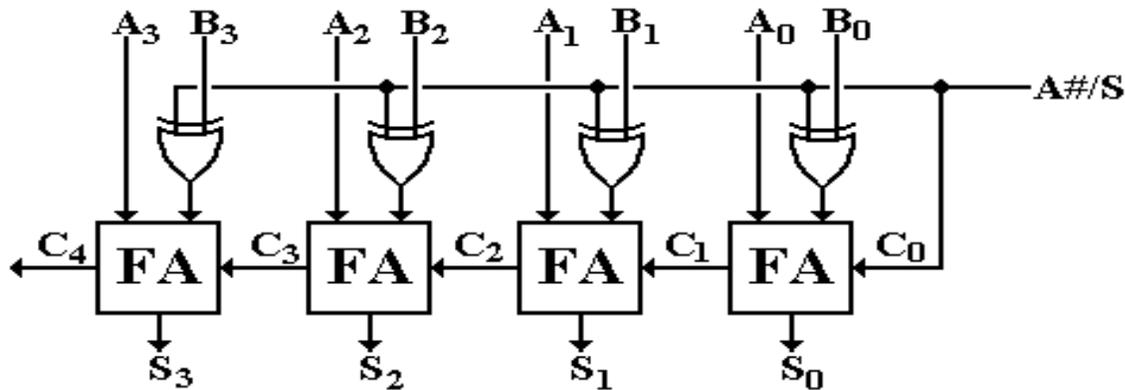Given the above, here is the full circuit for the 4-bit adder/subtractor.



Consider the case when  $A\#/S = 0$ . This indicates that addition is to take place. This signal is fed into the exclusive OR gates feeding the right inputs of the adders, passing the plain form of the B input. This feeds the units carry-in; the result is  $A + B + 0$ , or just  $A + B$ .

Now consider the case when  $A\#/S = 1$ . This indicates that subtraction is to take place. This is fed into the exclusive OR gates, passing the one's complement of B into the right inputs of the adder. The signal feeds the units carry-in, thus the result we get is  $A + \overline{B} + 1 = A - B$ .

Consider the following example of addition and subtraction. In decimal, the numbers are  $A = 5$  and  $B = 2$ . It should be obvious that  $A + B = 7$  and  $A - B = 3$ .

Let's do the arithmetic in 4-bit binary. The addition is straightforward.

A     = 0101  
 B     = 0010  
 Sum   = 0111


In order to evaluate  $A - B$ , it is necessary first to take the two's-complement of B.

B                     = 0010  
 1's complement     = 1101  
 Add 1 to get        = 1110


Here then is the addition to get  $A - B$

A     0101     In the 4's column,  $1 + 1$  with carry-in = 0 is 0, with carry-out = 1.  
 -B   1110     In the 8's column,  $1 + 0$  with carry-in = 1 is 0, with carry-out = 1  
      0011     The carry out from the 8's column is discarded.

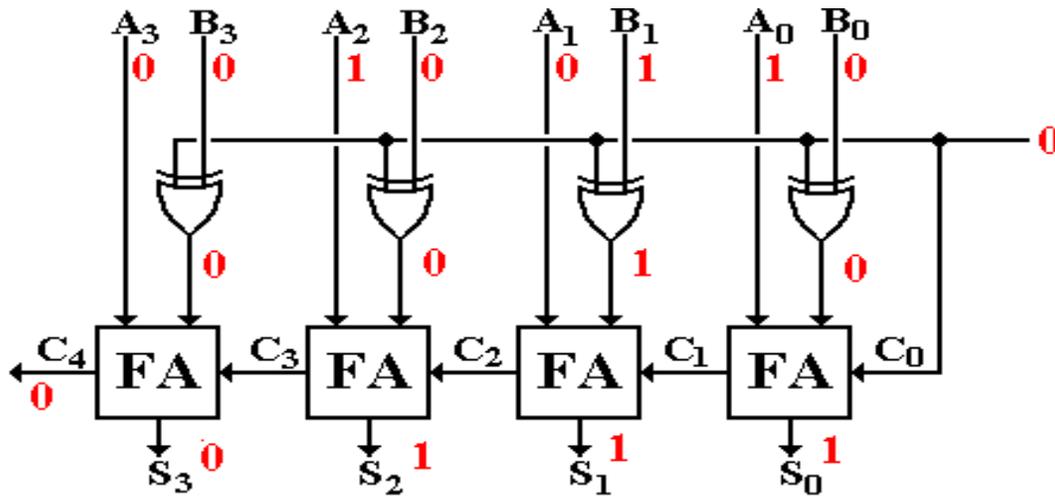Here is the circuit above when addition is called for;  $A\#/S = 0$ . Note that the selector input to the exclusive OR function is a 0, so that the B values are passed unchanged.



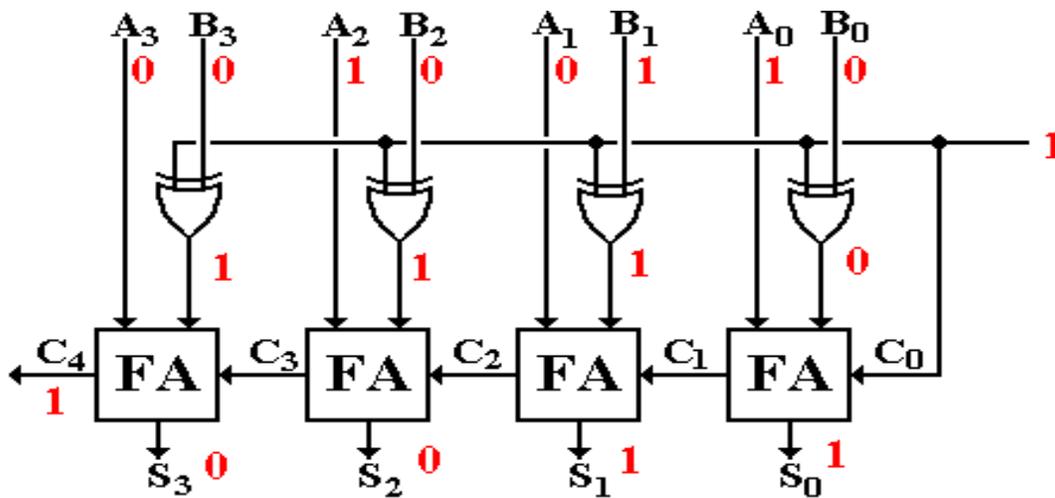Here is the circuit above when subtraction is called for;  $A\#/S = 1$ . The selector input to the exclusive OR function is a 1, so that the value passed is the one's-complement of B



As indicated above, these circuits are correct logical models of an adder/subtractor, but they are not actually used. Consider a 32-bit version of this ripple carry adder. It would have 32 full adders, connected in the same manner as above.

Such a ripple carry adder is much too slow for commercial use. Each full-adder must wait on the completion of the carry-out calculations of all the full-adders to its right before it can begin calculating the sum and carry-out.

The full-adder for the sign bit (FA 31) must wait for all 31 full-adders (FA 0 to FA 30) to its right to complete their calculations before starting. That is a long wait.

### The Shifter

Bits in an addressable unit, such as a byte or word, are considered to have position. A shifter shifts each bit in the unit by a fixed amount, with variations depending on type.

In our examples of shifting, we shall consider 8-bit **bytes**. The term “byte”, coined by IBM, and long thought to be trademarked by them, was chosen for the unit of storage appropriate to store the binary coding for a character. At the time, the complete IBM character set required seven bits to encode; this was extended to 8 bits out of habit.

Each byte, having eight bits, has its bits numbered from 0 through 7. Here is the bit numbering scheme used by all manufacturers except IBM.

Bit #	7	6	5	4	3	2	1	0
Value	1	0	0	1	0	1	1	0

Bit 7 is the most significant bit; bit 0 is the least significant bit. In hexadecimal notation, this would be represented as 96. The unsigned decimal value is  $9 \cdot 16 + 6 = 150$ .

Here are some examples of simple logical shifts, in which a 0 is shifted into the vacated “spot”.

The original value in binary:                   **1001 0110**  
 The original value right shifted one place:   **0100 1011**  
 The original value right shifted two places   **0010 0101**  
 The original value in binary:                   **1001 0110**  
 The original value left shifted one place:     **0010 1100**  
 The original value left shifted two places     **0101 1000**

There is some interesting arithmetic for unsigned integers hidden in these shift operators. It is more easily noticed for smaller numbers. Decimal 11 in binary is **0000 1011**.

The original value in binary:                   **0000 1011**, decimal value = 11  
 The original value shifted right one place   **0000 0101**, decimal value = 5  
 The original value shifted right two places   **0000 0010**, decimal value = 2.  
 The original value in binary:                   **0000 1011**, decimal value = 11  
 The original value shifted left one place     **0001 0110**, decimal value = 22  
 The original value shifted left two places     **0010 1100**, decimal value = 44.

In other words, for unsigned binary integers, a single left shift is equivalent to multiplication by two, and a single right shift is equivalent to division by two, with the remainder discarded. For signed binary integers, the situation is only slightly more complicated. The shift operations are much more time efficient than either integer multiplication or integer division. For this reason, one often sees shift operations substituted for multiplications and divisions by powers of two.

The hardware for the simplest shift units shifts only one place at a time. To shift left by three places requires three calls to the shift operator. There are two types of shifters that are more efficient and hence more complex. The logarithmic shifter has a number of stages that is the logarithm (base 2) of the number of bits; a shifter for 16 bits would have four stages ( $16 = 2^4$ ), and a shifter for 32 bits would have five stages ( $32 = 2^5$ ).

The most efficient shifter is the **barrel shifter**; it has one stage only.


In general, there are two types of shifts – left shifts and right shifts. These names correspond roughly to the way in which we would illustrate these shifts by drawing diagrams. Each of the two shift types comes in three varieties: logical, circular, and arithmetic.

The basic definition of each shift type is in terms of shifting by one place. We should note that multiple shifts are easily defined; shifting by  $N$  places must be equivalent to  $N$  single shifts. For convenience in designing a barrel shifter, we normally think in terms of shifting by  $N =$  a power of two, so that a shift by 13 places is a shift by 1 place, followed by a shift by 4 places, and then a shift by 8 places, as  $13 = 1 + 4 + 8$ .

We shall illustrate the shift types by considering them as applied to an eight-bit shift register, with contents labeled as  $R_7 R_6 R_5 R_4 R_3 R_2 R_1 R_0$ . We use 1001 0110 as an example.
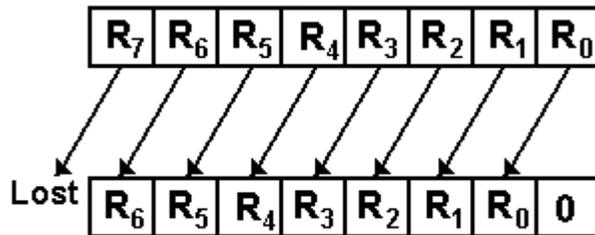
### Logical Shifts

Logical shifts just move bits in the indicated direction, padding out with 0's. Shifts can be by any count, but shifts by more than the size of the register leave it all 0's.



For left shifting an  $N$ -bit register by 1 place


$$R_{J+1} \leftarrow R_J \quad \text{for } 0 \leq J < (N - 1)$$

$$R_0 \leftarrow 0, R_{(N-1)} \text{ is lost}$$

As an example of a shift of an 8-bit register

For a single left shift            1001 0110 becomes 0010 1100

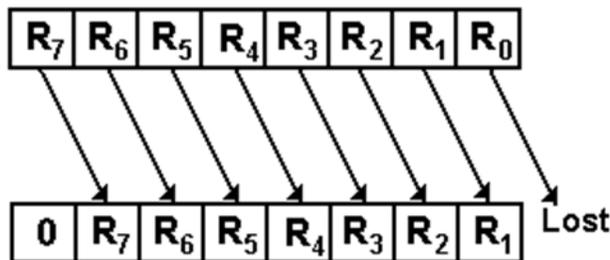Left shift by 2 places:            1001 0110 becomes 0101 1000



For right shifts by 1 place

$$R_{J+1} \rightarrow R_J \quad \text{for } 0 \leq J < (N - 1)$$

$$R_{(N-1)} \leftarrow 0, R_0 \text{ is lost}$$

As an example of a 8-bit register shift

For a single right shift            1001 0110 becomes 0100 1011


Right shift by 2 places:            1001 0110 becomes 0010 0101

Note that shifting either left or right by eight or more places produces the result 0000 0000, so that the shift count will normally be in the range 0 through 7 inclusive.

The general rule for an  $N$ -bit register is that the shift count is usually in the range from 0 to  $(N - 1)$  inclusive, a modulo- $N$  non-negative number.
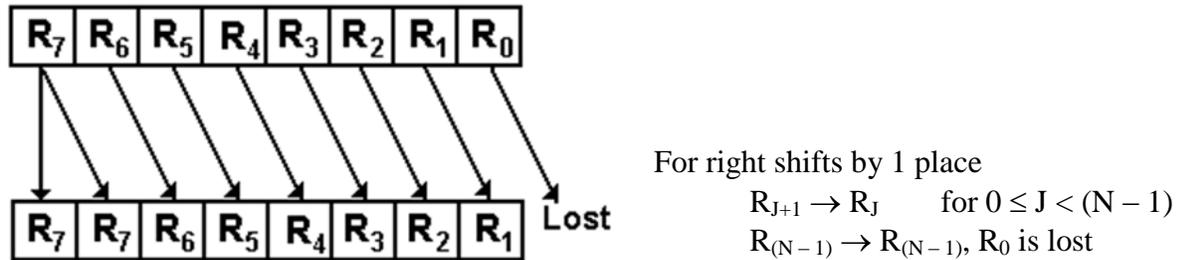
### Arithmetic Shifts

Arithmetic shifts are identical to logical shifts except that the sign bits are preserved. Arithmetic shifting is normally defined only for right shifts.



As an example of an 8-bit register 1001 0110 becomes 1100 1011

The purpose of arithmetic shifts is to cause the right shift to become equivalent to division by two on two's-complement integers. We use 8-bit two's-complement arithmetic to illustrate the correspondence of shifting to multiplication and division. The range of this representation is from  $-128$  to  $127$  inclusive.

Consider the number 52, represented as 0011 0100 in binary. Taking the two's-complement of this binary pattern, we find that the representation of  $-52$  is 1100 1100.

We first apply successive arithmetic right shifts to both 52 and  $-52$ .

00110100	52	11001100	-52
00011010	26	11100110	-26
00001101	13	11110011	-13
00000110	6	11111001	-7
00000011	3	11111100	-4
00000001	1	11111110	-2
00000000	0	11111111	-1


We now apply successive logical left shifts to the same two numbers.

00110100	52	11001100	-52
01101000	104	10011000	-104
11010000	-48	00110000	48
10100000	-96	01100000	96
01000000	64	11000000	-64

Note that this corresponds to multiplication by two whenever the sign bit stays the same.

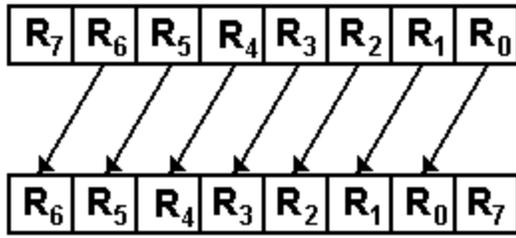
**Circular Shifts**

Circular shifts are identical to logical shifts except that bits “shifted off” one end are put at the other end, thus making the shift appear as a circle.



For left shifts by 1 place  
 $R_{J+1} \leftarrow R_J$  for  $0 \leq J < (N - 1)$      $R_0 \leftarrow R_{(N-1)}$ , nothing is lost

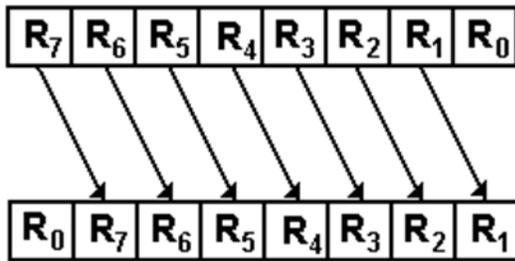As an example for an 8-bit shift  
 1001 0110 becomes 0010 1101



For right shifts by 1 place  
 $R_{J+1} \rightarrow R_J$  for  $0 \leq J < (N - 1)$   
 $R_{(N-1)} \leftarrow R_0$


As an example of an 8-bit shift  
 1001 0110 becomes 0100 1011

The Barrel Shifter

To give a flavor of a barrel shifter, I design a single bit circular shifter for a 4-bit number. We must begin with a table giving the output of the shifter in terms of the input  $R_3R_2R_1R_0$ .

	No shift	Left Circular	Right Circular
$Y_3$	$R_3$	$R_2$	$R_0$
$Y_2$	$R_2$	$R_1$	$R_3$
$Y_1$	$R_1$	$R_0$	$R_2$
$Y_0$	$R_0$	$R_3$	$R_1$

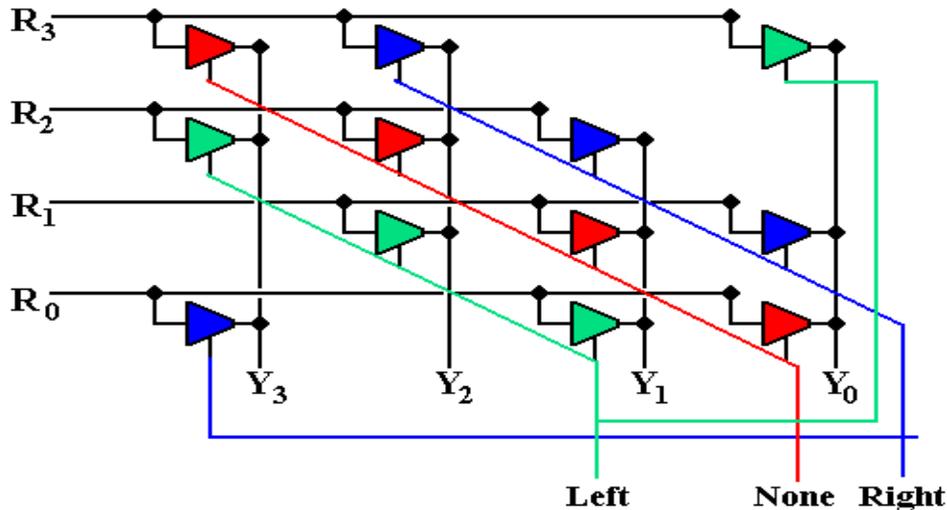
Here is the circuit. It is implemented with tri-state buffers. When there is no shift, the red line is asserted. The green line is asserted for a single left shift and the blue line for a right shift.




As complex as the above circuit appears to be, it can grow much messier for reasonably sized shift units. The number of tri-state buffers scales quadratically as the number of bits in the ALU; more specifically a shifter for an  $N$ -bit ALU would require  $3N^2$  tri-states. That would be 768 tri-states for a 16-bit ALU and 3,072 tri-states for a 32-bit ALU.

In order to clarify the above circuit, we present the state of the circuit for each of the three shift options: no shift, left shift by 1, and right shift by 1. Note that for each diagram, each input line is connected to precisely one output line.

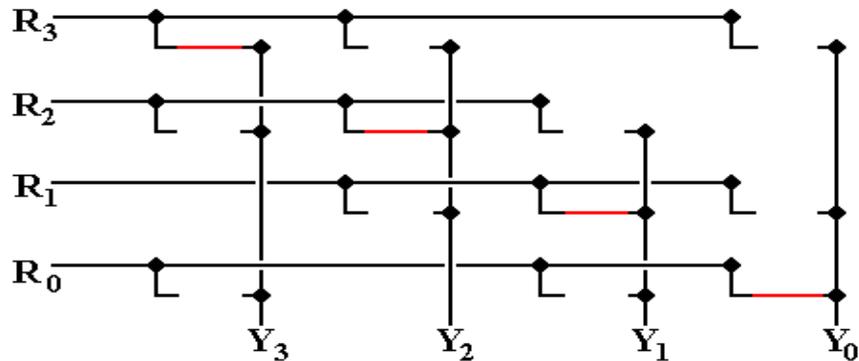
First the no shift option. The lines in red show the connections. Other wires are not connected.



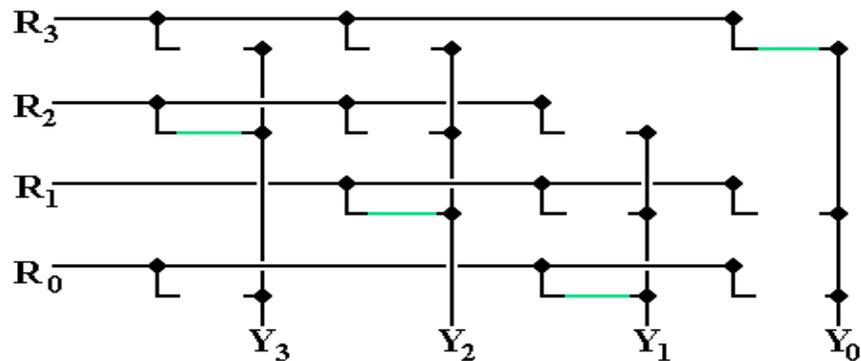Now the left shift option. The lines in green show the connections.



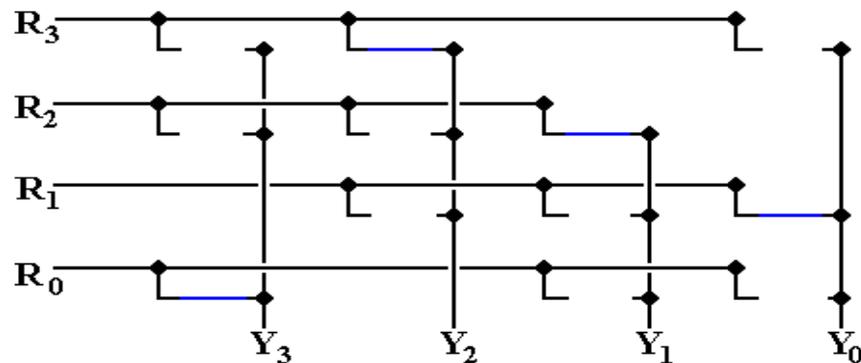And now the right shift option. The lines in blue show the connections.



### **Multiplication and Division**

We note immediately that multiplication of two  $N$ -bit integers yields a product with  $2N$  bits. For that reason, we shall discuss  $N$ -bit multiplication with a  $2N$ -bit product, and  $N$ -bit division with a  $2N$ -bit dividend, an  $N$ -bit divisor, an  $N$ -bit quotient, and  $N$ -bit remainder. This “doubling of the digits” is seen in decimal as well as binary multiplication.

Decimal:  $9,999 \bullet 9,999 = 99,980,001$   
 Binary  $1111 \bullet 1111 = 1110\ 0001$  ( $15 \bullet 15 = 225$ )

The most common implementations of multipliers call for two 16-bit numbers with a 32-bit product, and two 32-bit numbers with a 64-bit product.

We begin with a consideration of multiplication for unsigned positive integers. At one level, this is quite simple, as the “times table” is very small. Here it is.

A	B	A•B
0	0	0
0	1	0
1	0	0
1	1	1

One might note that this is exactly the truth table for the logical AND function, which is denoted by the same symbol as multiplication. This might suggest the use of the logical AND gate in a multiplier; the true circuits are even simpler. Consider a labeled example.

<u>1011</u>	the multiplicand, with decimal value 11
<u>1001</u>	the multiplier, with decimal value 9
1011	
0000	
0000	the four partial products
<u>1011</u>	
1100011	the product, with decimal value 99

Note that there are four partial products, one for each bit in the multiplier. Each partial product is the length of the multiplicand, and is either a copy of the multiplicand or all 0. The standard assumption is that the multiplicand and multiplier have equal length, each having the length of the standard integer in the architecture. All commercial designs allow different lengths for integer representations (8-bit, 16-bit, 32-bit, etc.), providing a number of distinct multiplication operations (8-bit by 8-bit, 16-bit by 16 bit).

Modern multiplication algorithms are based on shifting and adding. This allows one to use the minimum number of registers required to hold the operands and the results. The standard approach calls for setting up a result of  $2N$  bits, initialized to zero. The multiplier is then examined right to left. If the bit is 1, the multiplicand is added to the result. If not, nothing is added.

The next step is to shift the multiplicand left by one, and consider the next bit in the multiplier. We illustrate this algorithm with two 4-bit numbers and an 8-bit product.



Now the five-bit part of the dividend, **10010**, is compared to the four-bit divisor, **1011**, and subtracted from it. A “1” is written directly above the units column for the divisor.

$$\begin{array}{r} \phantom{1011} \underline{00001} \\ 1011 \ ) 10010011 \\ \phantom{1011} \underline{1011} \\ \phantom{1011} 0111 \end{array}$$

Next a 0 is “brought down”, the divisor shifted once more to the right, and compared. The divisor is smaller than the partial remainder. The subtraction is performed.

$$\begin{array}{r} \phantom{1011} \underline{000011} \\ 1011 \ ) 10010011 \\ \phantom{1011} \underline{1011} \\ \phantom{1011} 01110 \\ \phantom{1011} \underline{1011} \\ \phantom{1011} 0011 \end{array}$$

We now finish the division using the standard manual practice.

$$\begin{array}{r} \phantom{1011} \underline{00001101} \\ 1011 \ ) 10010011 \\ \phantom{1011} \underline{1011} \\ \phantom{1011} 01110 \\ \phantom{1011} \underline{1011} \\ \phantom{1011} 001111 \\ \phantom{1011} \underline{1011} \\ \phantom{1011} 100 \end{array}$$