

Chapter 6 – More Combinational Circuits

Chapter Overview

The previous chapter of this text focused on Boolean functions and the SSI (Small Scale Integration) circuits used to implement those functions. We shall find it convenient to define some higher-level components that contain the equivalent of a number of SSI components and function at a higher level, closer to the logical description of problems we want solved. These components we now investigate fall under the classification of MSI (Medium Scale Integration) chips. Specifically, we shall study the following:

1. Decoders and Encoders.
2. Multiplexers and Demultiplexers.
3. The Full Adder.
4. A Shift Unit Allowing for Multiple Right or Left Shifts.
5. An ALU (Arithmetic Logic Unit).
6. A MDU (Multiplication/Division Unit).

Beginning with this revision of the chapter, we shall study two variants of some chips: the active high (easier for some to understand) and the active low (as seen in most commercial chips). This change is motivated by the increasing use of circuit emulators in this course.

Codes and A Review of Binary Arithmetic

In our study of digital circuits, it is time to move to a discussion of MSI components. Many of these are closely tied to the idea of binary codes to represent unsigned integers. For this reason, we shall indulge in a brief review of unsigned binary numbers and illustrate our discussion with three-bit binary codes as examples.

The first thing to be noted is that codes have many uses besides those commonly called “secret codes”, which are more often than not secret ciphers. Commercial codes arose in the age of telegrams, in which one would be charged by the word – defined to be any grouping of five characters. Books of commercial codes were published and used to substitute five letter groupings for much longer phrases commonly occurring in commercial messages.

The use of codes in digital computers is based on the fact that the computer stores only binary numbers: 0’s and 1’s. Thus we interpret patterns of 0’s and 1’s as codes for other objects: ASCII code for characters, two’s-complement code for integers, etc. As we shall see later, the meaning of a collection of binary bits in a computer depends on the context in which the binary bits are fetched from the memory.

One commonly used pattern is that of **unsigned binary numbers**, in which the bit patterns represent non-negative integers. In order to understand these numbers, we must recall some arithmetic that we learned early in elementary school – positional notation.

Consider the decimal number 139. To be precise, this is not a number but a collection of symbols each used to represent a number. We know that the digit “1” represents the number 1, the digit “3” represents the number 3, and the digit “9” represents the number 9. The association of the character string “139” with the number 139 is based on **positional notation**, which states that $139 = 1 \cdot 100 + 3 \cdot 10 + 9 \cdot 1 = 1 \cdot 10^2 + 3 \cdot 10^1 + 9 \cdot 10^0$.

The above example assumes decimal (base 10) notation, which is the notation most commonly used by humans for representing integers. In our studies of digital computers, we must consider not only decimal numbers but also binary (base 2), octal (base 8) and hexadecimal (base 16). It is conventional to represent the base of every number system as a decimal number. Any other approach would lead to considerable confusion.

In a positional number system, the value of a string of digits is expressed in terms of powers of the base B . Consider the four-digit number, denoted in the abstract as $D_3D_2D_1D_0$. The value of this number is given by $D_3 \cdot B^3 + D_2 \cdot B^2 + D_1 \cdot B^1 + D_0 \cdot B^0$. For example, consider the number 1101. The value of this number depends on the base of the number system.

In decimal notation, we have $1 \cdot 10^3 + 1 \cdot 10^2 + 0 \cdot 10^1 + 1 \cdot 10^0 = 1 \cdot 1000 + 1 \cdot 100 + 0 \cdot 10 + 1 \cdot 1 = 1000 + 100 + 1 = 1101_{10}$.

In octal numbers (base 8), we have

$$\begin{aligned} 1101_8 &= 1 \cdot 8^3 + 1 \cdot 8^2 + 0 \cdot 8^1 + 1 \cdot 8^0 \\ &= 1 \cdot 512 + 1 \cdot 64 + 0 \cdot 8 + 1 \cdot 1 &= 577_{10}. \end{aligned}$$

In hexadecimal numbers (base 16), we have

$$\begin{aligned} 1101_{16} &= 1 \cdot 16^3 + 1 \cdot 16^2 + 0 \cdot 16^1 + 1 \cdot 16^0 \\ &= 1 \cdot 4096 + 1 \cdot 256 + 0 \cdot 16 + 1 \cdot 1 &= 4453_{10}. \end{aligned}$$

In binary numbers (base 2), we have

$$\begin{aligned} 1101_2 &= 1 \cdot 2^3 + 1 \cdot 2^2 + 0 \cdot 2^1 + 1 \cdot 2^0 \\ &= 1 \cdot 8 + 1 \cdot 4 + 0 \cdot 2 + 1 \cdot 1 &= 13_{10}. \end{aligned}$$

Common examples of encoders and decoders are based on either two-bit or three-bit arithmetic. Two bits can encode four numbers, 0 through 3 in unsigned binary. Three bits can encode eight numbers, 0 through 7 in unsigned binary. In general, N bits can encode 2^N different numbers, 0 through $2^N - 1$ in unsigned binary.


	Binary	Decimal
The two-bit codes are	00	0
	01	1
	10	2
	11	3
The three-bit codes are	000	0
	001	1
	010	2
	011	3
	100	4
	101	5
	110	6
	111	7

Multiplexers and Demultiplexers

A multiplexer has a number of inputs (usually a power of two), a number of control signals, and one output. A demultiplexer has one input signal, a number of control signals, and a number of outputs, also usually a power of two. We consider here a 2^N -to-1 multiplexer and a 1-to- 2^N demultiplexer.

Circuit	Inputs	Control Signals	Outputs
Multiplexer	2^N	N	1
Demultiplexer	1	N	2^N

 The action of each of these circuits is determined by the control signals. For a multiplexer, the output is the selected input. In a demultiplexer, the input is routed to the selected output. As examples, we show the diagrams for both a four-to-one multiplexer (MUX) and a one-to-four demultiplexer (DEMUX).




Note that each of the circuits has two control signals. For a multiplexer, the N control signals select which of the 2^N inputs will be passed to the output. For a demultiplexer, the N control signals select which of the 2^N outputs will be connected to the input.

Multiplexers

The output for a multiplexer can be represented as a Boolean function of the inputs and the control signals. As an example, we consider a 4-input multiplexer, with control signals labeled C_0 and C_1 and inputs labeled I_0 , I_1 , I_2 , and I_3 . The output can be described as a truth table or algebraically. Note that each of the truth tables and algebraic expression shows the input that is passed to the output. The truth table is an abbreviated form of the full version, which as a table for independent variables C_0 , C_1 , I_0 , I_1 , I_2 , and I_3 would have 64 rows.


C_1	C_0	M	
0	0	I_0	$M = C_1' \cdot C_0' \cdot I_0 + C_1' \cdot C_0 \cdot I_1 + C_1 \cdot C_0' \cdot I_2 + C_1 \cdot C_0 \cdot I_3$
0	1	I_1	
1	0	I_2	
1	1	I_3	

 Multiplexers are generally described as 2^N -to-1 devices. These multiplexers have 2^N inputs, one of which is connected to the single output line. The N control lines determine which of the inputs is connected to the output. Here is a circuit for a 4-to-1 multiplexer. Note that the inputs are labeled X_3 , X_2 , X_1 , and X_0 here and I_3 , I_2 , I_1 , and I_0 in the multiplexer equation.



Demultiplexer

Demultiplexers are generally described as 1-to- 2^N devices. These multiplexers have one input, which is connected to one of the 2^N output lines. The N control lines determine which of the output line is connected to the input. Here is a circuit for a 1-to-4 demultiplexer, which might be called “active high” in that the outputs not selected are all set to 0. Note that multiplexers do not have the problem of unselected outputs; a MUX has only one output.

 

Note that, for good measure, we have added an enable-high to the demultiplexer. When this enable is 0, all outputs are 0. When this enable is 1, the selected output gets the input, X . Remember, that X can have a value of either 0 or 1.

We shall return to demultiplexers after we have discussed decoders. At that time, we shall note a similarity between the decoders and demultiplexers, consider the use of a decoder as a demultiplexer, and investigate the possibility of an active-low demultiplexer.

We close our discussion of multiplexers and demultiplexers with the two theorems.

Theorem 1: Any Boolean function of N Boolean variables, $N > 0$, can be constructed by a multiplexer with 2^N inputs and N control lines, labeled $C_{N-1} \dots C_0$.

Proof: We give as a proof a method for constructing the function. We then give an example. The method is as follows:

1. Connect the N variables to the N control lines $C_{N-1} \dots C_0$. It is generally easier to connect the control lines in order of the variables listed; thus for $F(X, Y, Z)$ we would connect X to C_2 , Y to C_1 , and Z to C_0 . This is merely a convenience.
2. Write the multiplexer equation in terms of the input variables; thus for $F(X, Y, Z)$, we write the multiplexer equation as

$$\begin{aligned} \mathbf{M} = & \bar{X} \cdot \bar{Y} \cdot \bar{Z} \cdot \mathbf{I}_0 + \bar{X} \cdot \bar{Y} \cdot Z \cdot \mathbf{I}_1 + \bar{X} \cdot Y \cdot \bar{Z} \cdot \mathbf{I}_2 + \bar{X} \cdot Y \cdot Z \cdot \mathbf{I}_3 \\ & + X \cdot \bar{Y} \cdot \bar{Z} \cdot \mathbf{I}_4 + X \cdot \bar{Y} \cdot Z \cdot \mathbf{I}_5 + X \cdot Y \cdot \bar{Z} \cdot \mathbf{I}_6 + X \cdot Y \cdot Z \cdot \mathbf{I}_7 \end{aligned}$$

3. Write the Boolean function in Canonical Sum of Products form. If the variables have been properly associated with the control lines, the terms in the Canonical SOP should be in the same order as the terms in the multiplexer equation.
4. Match the function $F(X, Y, Z)$ to the multiplexer. If a product term appears in the Boolean function, set the input to 1. Otherwise set the input to 0.

Example: Consider the function $F2 = X \cdot Y + X \cdot Z + Y \cdot Z$, which we have identified as the carry-out of a full adder with inputs X , Y , and Z .

We begin by connecting the variables to control lines in the suggested order. Connect X to C_2 , Y to C_1 , and Z to C_0 ; thus $C_2 = X$, $C_1 = Y$, and $C_0 = Z$.

Writing the multiplexer equation in terms of the input variables, we get:

$$\begin{aligned} \mathbf{M} = & \bar{X} \cdot \bar{Y} \cdot \bar{Z} \cdot \mathbf{I}_0 + \bar{X} \cdot \bar{Y} \cdot Z \cdot \mathbf{I}_1 + \bar{X} \cdot Y \cdot \bar{Z} \cdot \mathbf{I}_2 + \bar{X} \cdot Y \cdot Z \cdot \mathbf{I}_3 \\ & + X \cdot \bar{Y} \cdot \bar{Z} \cdot \mathbf{I}_4 + X \cdot \bar{Y} \cdot Z \cdot \mathbf{I}_5 + X \cdot Y \cdot \bar{Z} \cdot \mathbf{I}_6 + X \cdot Y \cdot Z \cdot \mathbf{I}_7 \end{aligned}$$

We now write the Boolean function in Canonical Sum of Products form.


$$\begin{aligned} \mathbf{F2} &= X \cdot Y + X \cdot Z + Y \cdot Z \\ &= X \cdot Y \cdot (\bar{Z} + Z) + X \cdot (\bar{Y} + Y) \cdot Z + (\bar{X} + X) \cdot Y \cdot Z \\ &= X \cdot Y \cdot \bar{Z} + X \cdot Y \cdot Z + X \cdot \bar{Y} \cdot Z + X \cdot Y \cdot Z + \bar{X} \cdot Y \cdot Z + X \cdot Y \cdot Z \\ &= \bar{X} \cdot Y \cdot Z + X \cdot \bar{Y} \cdot Z + X \cdot Y \cdot \bar{Z} + X \cdot Y \cdot Z \end{aligned}$$

In the Σ -list form we say $F2 = \Sigma(3, 5, 6, 7)$.

The final step is to assign the inputs:

$$\begin{array}{llll} \mathbf{I}_0 = 0 & \mathbf{I}_1 = 0 & \mathbf{I}_2 = 0 & \mathbf{I}_3 = 1 \\ \mathbf{I}_4 = 0 & \mathbf{I}_5 = 1 & \mathbf{I}_6 = 1 & \mathbf{I}_7 = 1. \end{array}$$

 We now show the design, again using X_0 through X_7 as labels for inputs.



This figure suggests a simpler way to design with multiplexers using this theorem.

- 1) Force the expression into a canonical SOP expression.
- 2) Write the canonical SOP expression as a Σ list
- 3) Connect the multiplexer inputs corresponding to numbers in the list to 1.
- 4) Connect the other inputs to 0.

Above, the design shows the implementation of $F(X, Y, Z) = \Sigma(3, 5, 6, 7)$. Note that inputs 3, 5, 6, and 7 are connected to logic 1; the others are connected to logic 0.

There are also two ways to implement an expression in POS. For each method we force the expression into canonical POS. We can then do one of two things: convert to canonical SOP and implement as above, or use the POS list as a list of inputs to set to 0; thus

- 1) Connect the multiplexer inputs corresponding to numbers in the Π list to 0.
- 2) Connect the other inputs to 1.

Above, the design shows the implementation of the same function $F(X, Y, Z) = \Sigma(3, 5, 6, 7)$, now called $F(X, Y, Z) = \Pi(0, 1, 2, 4)$. Note that inputs 0, 1, 2, and 4 are connected to logic 1; the others are connected to logic 0.

We close the discussion of this theorem with a remark on logical complexity as opposed to physical complexity. The logical complexity of a circuit is most readily expressed in the number of logic gates in the circuit. An alternate measure would be the maximum number of gates between any input and the output; this would determine the time delay of the circuit.

What might be called the “physical complexity” of a circuit is best measured in the number of physical chips that we use. Consider our function $F_1(X, Y, Z) = \Sigma(1, 2, 4, 7)$. As we shall see later, direct implementation with basic gates requires three NOT gates, four 3-input AND gates, and a 4-input OR gate. This requires four chips: one 6-input NOT chip, two triple 3-input AND chips and one double 4-input OR chip.

As we shall see below, this may be fabricated from a 3-to-8 decoder and one double 4-input OR chip, for a total of two chips. We have just seen the fabrication with a 8-to-1 multiplexer, a total of one chip. Physically, the last design is the simplest.

For all of these designs we assume that the control inputs have been set in the correct order. We now consider another way to design with multiplexers. This method is a bit more complex, and thus should be used less often. In this author's view, it is less important. However, your author cannot resist the impulse to impart knowledge, so here it is.

Theorem 2: Any Boolean function of $(N + 1)$ Boolean variables, $N > 0$, can be constructed by a multiplexer with 2^N inputs and N control lines.

Proof: We give as a proof a method for constructing the function. We then give an example. The method is as follows:

1. Connect any N variables to the control lines. This leaves one variable unconnected.
2. Express the Boolean function in normal SOP form. Each term must have a literal for each of the N variables that are connected to the control lines and may contain the other one. Put another way, each of the 2^N product terms possible on the N variables attached to the control lines must be included in a term in this expression.
3. Connect the remaining variable, its complement, 0, or 1 to the 2^N input lines.
4. Match the terms.

Example:

Consider the function $F2 = A \bullet B + A \bullet C + B \bullet C$, which we have identified as the carry-out of a full adder with inputs A , B , and C . Arbitrarily, we connect A and B to the control lines. This implies that each of the terms in $F2$ must contain both A and B , either in complemented or plain form. To get this, we use some algebra to expand the last two terms.

$$\begin{aligned}
 F2 &= A \bullet B + A \bullet C + B \bullet C \\
 &= A \bullet B + A \bullet (B + B') \bullet C + (A + A') \bullet B \bullet C \\
 &= A \bullet B + A \bullet B \bullet C + A \bullet B' \bullet C + A \bullet B \bullet C + A' \bullet B \bullet C \\
 &= A \bullet B + A \bullet B \bullet C + A \bullet B \bullet C + A \bullet B' \bullet C + A' \bullet B \bullet C \\
 &= A \bullet B + A \bullet B \bullet C + A \bullet B' \bullet C + A' \bullet B \bullet C && \text{as } X + X = X \\
 &= A \bullet B \bullet (1 + C) + A \bullet B' \bullet C + A' \bullet B \bullet C \\
 &= A \bullet B + A \bullet B' \bullet C + A' \bullet B \bullet C && \text{as } 1 + C = 1 \text{ for all } C.
 \end{aligned}$$

Note that the form produced is not canonical as the first term is lacking a C . It is, however, in the required sum of products form. To complete the construction, we rewrite $F2$ and match it against the multiplexer equation for a 4-input multiplexer.

$$\begin{aligned}
 F2 &= A' \bullet B' \bullet 0 & + & A' \bullet B \bullet C & + & A \bullet B' \bullet C & + & A \bullet B \bullet 1 \\
 M &= C_1' \bullet C_0' \bullet I_0 & + & C_1' \bullet C_0 \bullet & + & C_1 \bullet C_0' \bullet I_2 & + & C_1 \bullet C_0 \bullet I_3
 \end{aligned}$$

The match-up is $C_1 = A$, $C_0 = B$, $I_0 = 0$, $I_1 = C$, $I_2 = C$, and $I_3 = 1$. With these inputs, the multiplexer has synthesized the function $F2$.

Decoders and Encoders


We now consider an important class of commercial circuits – encoders and decoders. These perform the functions suggested by the corresponding decimal-binary conversions. In conversion of a decimal number to binary, we obtain the binary equivalent of the number. An encoder has a number of inputs, usually a power of two, and a set of outputs giving the binary code for the “number” of the input.

Encoders

Consider a classic 2^N -to- N encoder. The inputs are labeled I_0, I_1, \dots, I_K , where $K = 2^N - 1$. The assumption is that only one of the inputs is active; in our way of thinking only one of the inputs is 1 and the rest are 0. Suppose input J is 1 and the rest are 0. The output of the circuit is the binary code for J . Suppose a 32-to-5 encoder with input 18 active. The output Z is the binary code 10010; $Z_4 = 1, Z_3 = 0, Z_2 = 0, Z_1 = 1, \text{ and } Z_0 = 0$.

Common encoders include 8-to-3, 16-to-4, and 32-to-5. One common exception to the rule of 2^N -to- N is a 10-to-4 encoder, which is used because decimal numbers are so common. Note that three binary bits are not sufficient to encode ten numbers, so we must use four bits and not produce the outputs 1010, 1011, 1100, 1101, 1110, or 1111.

 We now present a detailed discussion and a design of a 10-to-4 encoder. We begin with a diagram that might illustrate a possible use of an encoder.



In this example, the key pad has ten keys, one for each digit. When a key is pressed, the output line corresponding to that key goes to logic 1 (5 volts) and the other output lines stay at logic 0 (0 volts). Note that there are ten output lines from the key pad, one for each of the keys. These ten output lines form ten input lines into the 10-to-4 encoder.

The 10-to-4 encoder outputs a binary code indicating which of the keys has been pressed. In a complete design, we would require some way to indicate that no key has been pressed. For our discussion, it is sufficient to ignore this common case and assume that a key is active.

We first ask why we need four bits for the encoder. N bits will encode 2^N different inputs. As a result, to encode M different items, we need N bits with $2^{N-1} < M \leq 2^N$. To encode 10 inputs, we note that $2^3 < 10 \leq 2^4$, so we need 4 bits to encode 10 items.

We now present a table indicating the output of the encoder for each input. In this example, we assume that at any time exactly one input is active.

Input	Y_3	Y_2	Y_1	Y_0
X_0	0	0	0	0
X_1	0	0	0	1
X_2	0	0	1	0
X_3	0	0	1	1
X_4	0	1	0	0
X_5	0	1	0	1
X_6	0	1	1	0
X_7	0	1	1	1
X_8	1	0	0	0
X_9	1	0	0	1

In the table at left, we label the inputs X_0 through X_9 , inclusive. To produce the equations for the outputs, we reason as follows.

Y_3 is 1 when either $X_8 = 1$ or $X_9 = 1$.

Y_2 is 1 when $X_4 = 1$ or $X_5 = 1$ or $X_6 = 1$ or $X_7 = 1$.

Y_1 is 1 when $X_2 = 1$, $X_3 = 1$, $X_6 = 1$, or $X_7 = 1$.

Y_0 is 1 when $X_1 = 1$, $X_3 = 1$, $X_5 = 1$, $X_7 = 1$, or $X_9 = 1$.

These observations lead to the following equations, used to design the encoder.


$$Y_3 = X_8 + X_9$$

$$Y_2 = X_4 + X_5 + X_6 + X_7$$

$$Y_1 = X_2 + X_3 + X_6 + X_7$$

$$Y_0 = X_1 + X_3 + X_5 + X_7 + X_9$$

 Here is the circuit for the 10-to-4 encoder.



The student will note that input X_0 is not connected to an output. This gives rise to the following problem for the circuit: how does one differentiate between X_0 being active and no input being active. That might be a problem for real encoder design.

The most straightforward modification of the circuit would be to create the logical OR of the ten inputs and pass that signal as a “key pressed” signal. We mention this only to show that some applications must handle this case; we shall not consider it further in this course.

Another issue with encoders is what to do if two or more inputs are active. For ‘plain’ encoders the output is not always correct; for example, in the above circuit with inputs X_3 and X_5 active would output $Y_3 = 0$, $Y_2 = 1$, $Y_1 = 1$, and $Y_0 = 1$.

Priority encoders are designed to avoid the problem of multiple inputs by implementing a priority order on the inputs and producing the output for the input that has priority. For example, in a 32-to-5 priority encoder, having inputs 18 and 29 active would produce either the binary code 10010 (for 18) or 11101 (for 29), depending on the priority policy, and not the output 11111 that a plain encoder would produce.

Decoders

An N -to- 2^N decoder does just the opposite, taking an N bit binary code and activating the output labeled with the corresponding number. Consider a 4-to-16 decoder with outputs labeled Z_0, Z_1, \dots, Z_{15} . Suppose the input is $I_3 = 1$, $I_2 = 0$, $I_1 = 0$, and $I_0 = 1$ for the binary code 1001. Then output Z_9 is active and the other outputs are not active.

Again, the main exception to the N -to- 2^N rule for decoders is the 4-to-10 decoder, which is a common circuit. Note that it takes 4 bits to encode 10 items, as 3 bits will encode only 8. This author’s preference would be to use a 4-to-16 decoder and ignore some of the outputs, but this author does not establish commercial practice. The main advantage is that the 4-to-10 decoder chip would have 6 fewer pins than a 4-to-16 decoder; a 16-pin chip is standard and cheaper to manufacture than a 22-pin chip.

Another issue is whether the signals are **active high** or **active low**. Our examples have been constructed for active high circuits. Consider the 4-to-16 decoder as an example. If the input code is 1001, then the output Z_9 is a logic 1 (+5 volts) and all other outputs are logic 0 (0 volts). This approach is active high. In real commercial circuits, we often have outputs as active low, in which case the above decoder would have output Z_9 as a logic 0 (0 volts) and all other inputs as logic 1 (+5 volts). This reflects an issue with design using real TTL circuits or with standard circuit emulators, such as MultiSim or Multi-Media Logic.

Decoders have N inputs and 2^N outputs. We consider a 3-to-8 decoder; thus $N = 3$. The design that we present will assume that the decoder is active high; again that the selected output becomes logic 1 (5 volts) and the others remain at logic 0 (ground or 0 volts).

The decoder is based on the association of binary numbers to decimal numbers, as is shown in the figure at right. Since this is a 3-to-8 decoder, we have three inputs, labeled X_2, X_1 , and X_0 ; and eight outputs, labeled $Y_7, Y_6, Y_5, Y_4, Y_3, Y_2, Y_1$, and Y_0 .


The observation that leads to the design of the decoder is the obvious one that the values of X_2, X_1 , and X_0 determine the output selected. For this part of the discussion, I choose to ignore the enable input. We introduce the Enable output in a later discussion.

Decimal	Binary
0	000
1	001
2	010
3	011
4	100
5	101
6	110
7	111

The following Boolean equations determine the 3-to-8 decoder.

$$\begin{array}{ll} Y_0 = \bar{X}_2 \cdot \bar{X}_1 \cdot \bar{X}_0 & Y_4 = X_2 \cdot \bar{X}_1 \cdot \bar{X}_0 \\ Y_1 = \bar{X}_2 \cdot \bar{X}_1 \cdot X_0 & Y_5 = X_2 \cdot \bar{X}_1 \cdot X_0 \\ Y_2 = \bar{X}_2 \cdot X_1 \cdot \bar{X}_0 & Y_6 = X_2 \cdot X_1 \cdot \bar{X}_0 \\ Y_3 = \bar{X}_2 \cdot X_1 \cdot X_0 & Y_7 = X_2 \cdot X_1 \cdot X_0 \end{array}$$

 Here is the circuit diagram for the 3-to-8 active-high decoder.



The Enable Input


We now consider another important input to the decoder chip. This is the enable input. If the decoder enable signal is active high, then the decoder is active when enable is 1 and not active when enable = 0. We shall consider enabled-high decoders here.

The enable input allows the decoder to be either enabled or disabled. For an active high decoder that is enabled high (Enable = 1 activates it) we have the following.

- Enable = 0 All outputs of the decoder are 0
- Enable = 1 The selected output of the decoder is 1, all other outputs are 0.


One way to express the effect of the enable input is to use a modified truth table.

Enable	X_1	X_0	Y_0	Y_1	Y_2	Y_3
0	d	d	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 

Thus, all outputs are 0 when the enable input is 0. This is true without regard to the inputs. When the enable input is 1, the outputs correspond to the inputs.

 
Here is a circuit diagram for a 2-to-4 decoder that is enabled high and active high.



Note that the Enable input is passed as an input to all four of the AND gates used to produce the output of the decoder. As a result, when Enable = 0, all of the outputs are 0; the decoder is not active.

When Enable = 1 in the above circuit, the other two inputs X_1 and X_0 will determine the one of the four outputs is set to 1; the others remaining 0. This is exactly how the active-high decoder should function.

 The following example illustrates the use of the enable input for decoders. We use two two-to-four decoders to construct a single three-to-eight decoder. The way to do this is to use one of the inputs, conventionally the high-order bit, as an enable signal. This way one of the two-to-four decoders will be enabled and one will not be. Here is the circuit.



Suppose the three-to-eight decoder is enabled. Under this assumption, the input I_2 selects the two-to-four decoder that is active. If $I_2 = 0$, then the top decoder is active and the bottom decoder is not active (all its outputs are 0). If $I_2 = 1$, then the bottom decoder is active and the top decoder is not active (all its outputs are 0). In either case, the inputs I_1 and I_0 are passed to both two-to-four decoders.

When $I_2 = 0$, the inputs I_1 and I_0 select which of outputs Y_0, Y_1, Y_2, Y_3 in the top two-to-four decoder is active and thus which of Z_0, Z_1, Z_2, Z_3 is active.

When $I_2 = 1$, the inputs I_1 and I_0 select which of outputs Y_0, Y_1, Y_2, Y_3 in the bottom two-to-four decoder is active and thus which of Z_4, Z_5, Z_6, Z_7 is active. Thus we have constructed the equivalent of a three-to-eight decoder.

The Active-Low, Enabled-Low Decoder

We now examine a decoder designed according to standard commercial practice. This decoder is active-low and enabled-low.

The enable input allows the decoder to be either enabled or disabled. For a decoder that is enabled low (Enable = 0 activates it) we have the following:

Enable = 1 None of the outputs of the decoder are active.

Enable = 0 Only the selected output is active; all others are inactive.


For a decoder that is enabled-low and active-low, we have the following:

Enable = 1 All outputs are 1; no output is active.

Enable = 0 Only the selected output has value 0 (active);
all others have value 1 (inactive).

One way to express the effect of the enable input is to use a modified truth table. Here we examine a 2-to-4 decoder that is enabled-low and active-low.


Enable	X ₁	X ₀	Y ₀	Y ₁	Y ₂	Y ₃
1	d	d	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

 


We may immediately deduce the decoder equations from the truth table just above. Here they are.

$$\begin{aligned}
 Y_0 &= \bar{E} + X_1 + X_0 & Y_2 &= \bar{E} + \bar{X}_1 + X_0 \\
 Y_1 &= \bar{E} + X_1 + \bar{X}_0 & Y_3 &= \bar{E} + \bar{X}_1 + \bar{X}_0
 \end{aligned}$$

 Here is the circuit diagram for a 2-to-4 decoder that is active low and enabled low.



We now repeat an earlier design, this time with decoders that are enabled–low. We use two two–to–four decoders (active low and enabled low) to construct a single three–to–eight decoder, that is also active low and enabled low. The way to do this is to use one of the inputs, conventionally the high–order bit, as an enable signal. This way one of the 2–to–4 decoders will be enabled and one will not be. Here is the circuit.

 

Suppose that the 3–to–8 decoder is disabled; $\overline{E} = 1$. Then, each of the 2–to–4 decoders is also disabled and all outputs are logic 1. This is as it should be.

Suppose the 3–to–8 decoder is disabled; $\overline{E} = 0$. Under this assumption, the input I_2 selects the 2–to–4 decoder that is active. If $I_2 = 0$, then the top decoder is active (with its Enable set to 0) and the bottom decoder is not active (with its Enable set to 1). If $I_2 = 1$, then the bottom decoder is active (its Enable = 0) and the top decoder is not active (its Enable = 1). In either case, the inputs I_1 and I_0 are passed to both 2–to–4 decoders.


When $I_2 = 0$, the inputs I_1 and I_0 select which of outputs Y_0, Y_1, Y_2 , or Y_3 in the top 2–to–4 decoder is active and thus which of Z_0, Z_1, Z_2 , or Z_3 is active.

When $I_2 = 1$, the inputs I_1 and I_0 select which of outputs Y_0, Y_1, Y_2 , or Y_3 in the bottom 2–to–4 decoder is active and thus which of Z_4, Z_5, Z_6 , or Z_7 is active. Thus we have constructed the equivalent of a 3–to–8 decoder.

There is an equivalence between decoders and demultiplexers that many students notice. Consider a 1-to- 2^N demultiplexer with N control signals, under the assumption that the selected output copies the input and the other outputs are set to the logic value considered inactive. The demultiplexer may be considered either as “active high”, with the inactive outputs set to logic 0, or “active low”, with the inactive outputs set to logic 1

Consider the “active high” demultiplexer. We then set the input (labeled “Enable” in the diagram) to logic 1 and note that the output selected by the control signals is logic 1 while the other outputs are logic 0. When the input (“Enable”) is set to logic 0, all of the outputs are logic 0. We have converted the demultiplexer into an active-high decoder.

 
The following figure shows a 1-to-4 demultiplexer used as a 2-to-4 decoder.



Note that the input to the circuit acting as a decoder is labeled X_1 and X_0 . This input is placed into the control inputs of the demultiplexer, indicating which output should receive the input, set to the decoder enable signal. When Enable = 0, all of the outputs are 0, as required for the decoder.

When Enable = 1, the $X_1 X_0$ input selects which output becomes 1 while the other outputs remain at 0. This makes the DEMUX so configured to be functionally equivalent to a 2-to-4 decoder.

 We now note a confusing usage in commercial chips, as seen in the Multi-Media Logic tool. The following chips are labeled demultiplexers; the one on the left called a 2-to-4 DEMUX and the one on the right called a 3-to-8 DEMUX.



In reality, each of these is an active-low, enabled-low decoder. In each, if $\overline{E} = 1$, all of the outputs are logic 1. In each, if $\overline{E} = 0$, the selected output is logic 0 and the rest are logic 1.

It is easy to see that each of the above may be used as an “active low” demultiplexer. Think of the \overline{E} input as input to the demultiplexer. What we have is as follows:

If $\overline{E} = 1$, all outputs are logic 1 (inactive).

If $\overline{E} = 0$, the selected output is logic 0 and the other outputs are logic 1.


In either case, the selected output has the value of the input.

Implementation of SOP expressions with decoders

We now consider the use of decoders as elements in a circuit. We first discuss active-high decoders for this design, although they are rarely used in commercial circuits. For such encoders, the design calls for use with OR gates to implement a function expressed in canonical SOP form.

We now give two examples of circuit design with decoders. Recall two functions specified by truth tables.

A	B	C	F1	F2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

We use an active-high decoder to implement these two functions.

Each of the two functions is represented in the truth table in a way that can easily be converted into canonical SOP form. F1 can be seen as the sum of canonical product terms 1, 2, 4, and 7. F2 can be seen as the sum of the canonical product terms 3, 5, 6, and 7. In the standard notation, we say $F1 = \Sigma(1, 2, 4, 7)$ and $F2 = \Sigma(3, 5, 6, 7)$.

The circuit to the right of the truth table shows the use of an active-high positive logic 3-to-8 decoder and an OR gate to synthesize each of the functions F1 and F2. The method for each function is the same. First represent the function in the canonical SOP list form and then connect each of the indicated outputs from the decoder to the OR gate for the function.

To synthesize $F1 = \Sigma(1, 2, 4, 7)$ we connect the outputs 1, 2, 4, and 7 from the decoder to the OR gate for F1. The output of this OR gate is F1.

Basis of the Designs


The design above is quite straightforward. Start with an active-high decoder and the Σ -list canonical representation of the function. Attach the outputs listed in the Σ -list to an OR gate. Your author would like, at this moment, to develop the logical basis of this strategy.

In the discussion below we shall consider design with both Active-High decoders and Active-Low decoders. It is hoped that this intuitive discussion will assist the reader to understand not only decoders themselves but also their use in the generation of arbitrary Boolean functions.


As always in our design examples, we select a function that would better be implemented by a much simpler circuit. The goal here is to present the method, not develop a clever design. The function to be implemented is one of the two that we have been discussing at some length in this and previous chapters: $F2 = \Sigma(3, 5, 6, 7) = \Pi(0, 1, 2, 4)$.

This function displays the unusual symmetry that there are 4 terms in both its SOP and POS expressions. All of our designs will use some sort of 4-input gate to combine the output of some sort of 3-to-8 decoder.

 
We begin by characterizing a number of basic gates. For the purpose of illustration, we examine 4-input gates. What is said is true for any number of inputs to these gates.



 
We now consider an active high decoder. For this and other examples, we assume that the decoder has been enabled; else all of its outputs are 0. An active high decoder outputs logic 1 for its selected output and logic 0 for the outputs not selected. For F2, we have:



 
Seeking a gate that outputs 1 if at least one of its inputs is 1, we are led to the OR gate.



 
Seeking a gate that outputs 1 only if all its inputs are 0, we are led to the NOR gate.



 
We now consider an active low decoder. For this and other examples, we assume that the decoder has been enabled; else all of its outputs are 1. An active high decoder outputs logic 0 for its selected output and logic 1 for the outputs not selected. For F_2 , we have:



 Looking for a gate that outputs 0 if all of its inputs are logic 1 and outputs logic 1 if at least one of its inputs is logic 0, we find the NAND gate.



 Looking for a gate that outputs 1 if and only if all of its inputs are 1, we find the AND gate.



Implementation of POS Expressions with Decoders

We have a number of options, the first of which is the most common. Just convert the expression to Sum of Products and continue.


Thus, if we are given $F_2(A, B, C) = \Pi(0, 1, 2, 4)$, we just convert the expression to $F_2(A, B, C) = \Sigma(3, 5, 6, 7)$ and continue with our work. Remember that the numbers in a canonical expression on N variables run from (0 through $2^N - 1$). The number is in the Σ -list if and only if it is not in the Π -list. The discussions above actually indicate how to construct the circuits directly from a canonical expression.

We note here that almost all commercially available decoders are active-low. Those in our lab are active-low. It is that fact that is one of the reasons for this long discussion.

Design Summary: Decoder Type and Expression


Active High, SOP Attach the specified outputs as input to an OR gate.

 Example: $F_2(A, B, C) = \Sigma(3, 5, 6, 7)$




Active High, POS Attach the specified outputs as input to a NOR gate

 Example: $F_2(A, B, C) = \Pi(0, 1, 2, 4)$




Active Low, SOP Attach the specified outputs as input to a NAND gate

 Example: $F_2(A, B, C) = \Sigma(3, 5, 6, 7)$



Active Low, POS Attach the specified outputs as input to an AND gate.

 
Example: $F_2(A, B, C) = \Pi(0, 1, 2, 4)$




Interlude: More Designs with Multi-Media Logic.

The first design shows two experiments with a 2-to-4 enabled-low, active-low decoder, which Multi-Media Logic labels as a “2:4 DEMUX”. In the top figure, we have $\overline{E} = 0$ and the selected output is set to logic 0 (seen by the LED being off). In the bottom figure, we have $\overline{E} = 1$, and none of the outputs are active. Each output is logic 1, as seen by the corresponding LED being illuminated.

 Often, experiments such as this set are the only way to determine the real behavior of a circuit element.



 Here is an implementation of our two functions $F1 = \Pi(0, 3, 5, 6)$ and $F2 = \Pi(0, 1, 2, 4)$ that uses an active high 3-to-8 decoder and two 4-input AND gates.



As we shall see in the section immediately following, these two functions ($F1$ and $F2$) have more common names that correspond to their standard usage in computers.

Design of a Full Adder

We now investigate the design of a full adder. A full-adder is specified by its truth table.


A	B	C	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A full adder circuit adds two bits (A and B) with a carry-in C. It produces two outputs the Sum and the Carry out to the next higher stage. Here we elect to translate the truth table to two Sum of Products expressions and implement the Sum and Carry using AND-OR logic.


$$\text{SUM} = A' \cdot B' \cdot C + A' \cdot B \cdot C' + A \cdot B' \cdot C' + A \cdot B \cdot C$$

$$\text{CARRY} = A \cdot B + A \cdot C + B \cdot C \text{ (this has been simplified).}$$

 Here is one design of a Full-Adder using the basic Boolean gates.



As an aside, we show a more conventional variant of the full adder circuit, one that is designed to address the “fan-out” problem. Consider the input labeled A in either circuit. It must be generated by another circuit element that is capable of delivering input to only a limited amount of gates. In the first circuit, the source of the signal A must drive five gates: the NOT gate producing A' and the AND gates producing $A \cdot B' \cdot C'$, $A \cdot B \cdot C$, $A \cdot B$, and $A \cdot C$. The circuit below is a common variant in which each of the A, B, and C inputs is driving only one gate – the first NOT gate of the double inverter pair. Such a design provides for a standard input load for the circuit and facilitates its use in design.

 

Gate Delays and Timing Analyses


At this point, we move on to creating a “ripple carry” adder, which is a simple collection of a number of full adders to generate the sum of two multi-bit integers. In order to undertake this design, we must first do a rough timing analysis of the full adder.

Consider the three basic gates from which a full adder is built. We normally do not consider the time delay for producing the output, but consider the circuit only after all transients have disappeared. However, there are occasions upon which we must consider the fact that the output of a given logic gate does not change immediately with the input, but only after a short time delay, called the “gate delay”.

Each gate introduces a delay and produces its output only after the delay. This delay is unique to the gate type and method of manufacture; thus an AND gate would display a gate delay different from that of a NOT gate. For simplicity, we just assume that all gates have the same delay, normally in the range 1 – 5 nanoseconds. We may note that the gates used in commercial microprocessors are etched onto the CPU chip and have gate delays that are considerably less, probably on the order of 100 picoseconds (0.10 nanoseconds).


In order to explain, consider three basic gates, each of which has its input change at $T = 0$.

$T = -1$ (before any changes)

 


We begin our analysis at a time called $T = -1$, and assume that the inputs have been stable for some time. At this time, the gate outputs are exactly what we expect.

$T = 0$ (when the input changes)

 

At $T = 0$, the inputs to each gate suddenly change. Note that the outputs of the gates have not yet changed, as the change has yet to propagate through each gate.

 $T = 1$ (one gate delay after the change)



At $T = 1$, by definition one gate delay after each input has changed, the outputs of each of the three gates finally reflects the changed inputs and the circuits again display the expected results. This is an example of the effect of gate delays – the changes in input gradually propagate through the circuit, with the output of a gate at $T = K$ depending on its input at the previous time $T = K - 1$.

Before the Input Changes

We now consider a timing analysis of the first version of the full adder (the one without the double not gates). Suppose at $T = 0$, the input changes from $A = 0, B = 0, C = 0$ to $A = 1, B = 0, C = 1$. We begin at $T = -1$, at which time the inputs have been stable for some time, so that all values in the circuits follow what would be expected from the Boolean equations for the SOP expressions of the Sum and Carry-Out.

 


Figure: The Situation before Any Input Change

The Input Changes

At $T = 0$ the input changes suddenly to $A = 1$, $B = 0$, $C = 1$. The situation is shown below. The new inputs are shown in **RED**, but note that none of the gate outputs (shown in **BLUE**) have yet changed. The change has not propagated through the gates and the circuit might be considered to be in a logically inconsistent state.

 


Figure: The Circuit at $T = 0$, the Instance of Input Change

Author's note: At this point, the only way to avoid confusion is to show both the previous value and current value of a changed input. The gate outputs, shown in blue, still depend on the old values and have not reacted to the new values.

After One Gate Delay

After one gate delay, the output of the gates that receive the input directly have changed, but the outputs of the gates one or more steps removed from the input have not changed. Again, the changed values are shown in **RED**, while the unchanged values are shown in **BLUE**.

Note the notation **OLD → NEW**, used in an attempt to avoid confusion in understanding the input to the AND gates, which are still responding to the status at $T = 0$.

 


Figure: The Full Adder after One Gate Delay

Note the output of the top AND gate. At $T = 0$, the value of C has changed to 1, but the value of A' and B' are still 1, so we have $A' = 1$, $B' = 1$, and $C = 1$. The output of $A' \cdot B' \cdot C$ at $T = 1$ depends on these values, which have changed from $A' = 1$, $B' = 1$, and $C = 0$; thus the value of $A' \cdot B' \cdot C$ changes from 0 to 1. We note that the value will change again.

After Two Gate Delays, the Carry-Out is Correct


 


Figure: The Full Adder after Two Gate Delays

After two gate delays, the effect of the input change has moved through all of the AND gates and the OR gate for the generation of the Carry-Out, which is now correct. Note that the SUM output has changed to 1, a result of the values of $A' \cdot B' \cdot C$ and $A \cdot B' \cdot C'$ at $T = 1$.

After Three Gate Delays, the Output is Stable

 After three gate delays, the output has changed to reflect the new input.




The progress of the change in the circuit is summarized in the table below.

T	A	B	C	A'	B'	C'	A'B'C	A'BC'	AB'C'	ABC	S	AB	AC	BC	CO
-1	0	0	0	1	1	1	0	0	0	0	0	0	0	0	0
0	1	0	1	1	1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	1	0	1	0	1	0	0	0	1	0	0
2	1	0	1	0	1	0	0	0	0	0	1	0	1	0	1
3	1	0	1	0	1	0	0	0	0	0	0	0	1	0	1

Ripple Carry Adders

The circuit above shows a full adder that takes two one-bit numbers and a one-bit carry-in and produces a one-bit sum and a one-bit carry-out. One bit adders might be cute, but our design will require a 32-bit adder/subtractor. Let's extend this design.

 The first step in the extension is to make a 32-bit ripple-carry adder. The significance of the term "ripple carry" will become obvious soon. The design of such an adder would be rather messy, so we here present a 4-bit ripple-carry adder. Such an adder is made from four full adders. The circuit, shown below, adds two four bit numbers $A_3A_2A_1A_0$ and $B_3B_2B_1B_0$.



A 32-bit ripple-carry adder will be made from 32 full adders. The name "ripple carry" arises from a timing analysis of the circuit, which we now undertake. Consider the first circuit showing a full adder. We count the number of gate levels required for each of the two outputs: we have two levels for the carry and three for the sum. The circuit shown has four full adders, labeled from right to left as FA₀, FA₁, FA₂, and FA₃. A 32-bit ripple carry adder would have 32 full adders, labeled from right to left as FA₀ through FA₃₁. Note that the input for full adder FA_K is the triple A_K, B_K, and C_K; its output is S_K and C_{K+1}. For $0 \leq K \leq 31$, the output C_{K+1} from full adder FA_K is an input to the next full adder FA_{K+1}. It is this fact that gives rise to the name "ripple-carry" as full adder FA_{K+1} cannot produce a correct output until some time after full adder FA_K has provided the correct value of C_{K+1} for use as input.

Note that FA₀ has C₀ ≡ 0, as the carry-in input is grounded. This effectively reduces the full adder to a half adder. The reason for keeping FA₀ as a full adder will become apparent soon.

Let FA₀ be the full adder taking in A₀, B₀, and C₀ (C₀ = 0) to produce the sum S₀ and carry-out C₁. If all input is at T = 0, FA₀ produces C₁ at T = 2 and S₀ at T = 3. But FA₁ cannot produce correct output until C₁ is correctly set by FA₀. Thus FA₁ produces C₂ at T = 4 and S₁ at T = 5. In general, one can show the following.

Full adder FA_K gets its input correct at time T = 2•K.


Full adder FA_K produces a correct carry-out at time T = 2•K + 2.

Full adder FA_K produces a correct sum at time T = 2•K + 3.


The correct answer "ripples" through the adder as the carry bits become correct.

Before we develop the 32-bit ripple-carry adder/subtractor, we must note that no modern computer uses a ripple-carry adder, as such devices are far too slow. We are talking about producing a 32-bit sum after 65 gate delays, approximately 130 nanoseconds. Real adders use a trick called “carry-look-ahead” in which the carry into higher order adders is computed in a more complex, but much more time-efficient manner.

We now consider the construction of a subtractor, again using a 4-bit unit for illustration. We use a feature of two’s-complement arithmetic that mimics true arithmetic in that subtraction can be implemented as addition of the negative: $A - B = A + (-B)$. But recall that negation in the two’s complement system is achieved by taking the one’s-complement (bitwise logical NOT) and adding 1, so $A - B = A + \overline{B} + 1$. This suggests a design for a subtractor, which we develop only for a single bit unit.

 

 This is interesting, but we want an adder/subtractor. Such a circuit is achieved by recalling an interesting property of the XOR function: $0 \oplus B = B$ and $1 \oplus B = \overline{B}$. This observation allows us to design an adder/subtractor controlled by the signal $\overline{\text{ADD}}/\text{SUB}$.



When $\overline{\text{ADD}}/\text{SUB} = 0$, this circuit adds the two 4-bit integers A and B. When $\overline{\text{ADD}}/\text{SUB} = 1$, this subtracts the 4-bit integer B from the 4-bit integer A. Thus we have the desired circuit, which can easily be extended to thirty two bits. Again, a real adder/subtractor will be fabricated using look-ahead technology, but the above circuit is logically correct.

Arithmetic Overflow – “Busting the Arithmetic”

We continue our examination of computer arithmetic to consider one more topic – **overflow**.

Arithmetic overflow occurs under a number of cases:

- 1) when two positive numbers are added and the result is negative
- 2) when two negative numbers are added and the result is positive
- 3) when a shift operation changes the sign bit of the result.

In mathematics, the sum of two negative numbers is always negative and the sum of two positive numbers is always positive. The overflow problem is an artifact of the limits on the range of integers and real numbers as stored in computers. We shall consider only overflows arising from integer addition.

We consider only two’s-complement arithmetic. The textbook considers only 32-bit numbers, but we use 16-bit numbers as allowing simpler examples. For two’s-complement arithmetic, the range of storable integers is as follows:

$$\begin{array}{llll} \text{16-bit} & -2^{15} \text{ to } 2^{15} - 1 & \text{or} & -32768 \text{ to } 32767 \\ \text{32-bit} & -2^{31} \text{ to } 2^{31} - 1 & \text{or} & -2147483648 \text{ to } 2147483647 \end{array}$$

The bits in an integer are numbered from left (most significant) to right (least significant), with the most significant bit having the highest number*. The bits are numbered 31 to 0 for 32-bit numbers, 15 to 0 for 16 bit numbers, and 7 to 0 for 8-bit numbers. In the standard integer notation, the most significant (left-most) bit is the sign bit; for 32-bit arithmetic bit 31 is the sign bit, and for 16-bit arithmetic the sign bit is bit 15.

Overflow in addition occurs when two numbers, each with a sign bit of 0, are added and the sum has a sign bit of 1 or when two numbers, each with a sign bit of 1, are added and the sum has a sign bit of 0. For simplicity, we consider 16-bit addition. As an example, consider the sum $24576 + 24576$ in both decimal and binary. Note that $24576 = 16384 + 8192 = 2^{14} + 2^{13}$.

$$\begin{array}{r} 24576 \qquad 0110\ 0000\ 0000\ 0000 \\ 24576 \qquad 0110\ 0000\ 0000\ 0000 \\ -16384 \qquad 1100\ 0000\ 0000\ 0000 \end{array}$$

Note that, as unsigned addition, the binary value is correct. However, in 16-bit arithmetic, bit 15 is the sign bit. We have two positive numbers (bit 15 is 0) giving rise to a negative sum (bit 15 is 1). This is an example of overflow.

In fact, $24576 + 24576 = 49152 = 32768 + 16384$. The overflow is due to the fact that the number 49152 is too large to be represented as a 16-bit signed integer.

***NOTE:** This is not the notation used by IBM for its mainframe and enterprise computers. In the IBM notation, the most significant bit (often the sign bit) is bit 0 and the least significant bit has the highest number; bit 7 for an 8-bit integer.

Common Notation (8-bit entry)

Bit #	7	6	5 – 1	0
	Sign	MSB		LSB

IBM Mainframe Notation


Bit #	0	1	2 – 6	7
	Sign	MSB		LSB

We now consider 16-bit addition. As inputs we have two 16-bit numbers A and B

$$A = A_{15}A_{14}A_{13}A_{12}A_{11}A_{10}A_9A_8A_7A_6A_5A_4A_3A_2A_1A_0$$

$$B = B_{15}B_{14}B_{13}B_{12}B_{11}B_{10}B_9B_8B_7B_6B_5B_4B_3B_2B_1B_0$$

 For each number, bit 15 is the sign bit, bit 14 is the bit for $2^{14} = 16384$, bit 13 is the bit for $2^{13} = 8192$, etc. Conceptually, a 16-bit adder comprises sixteen one-bit full adders, each taking in a carry bit from the lower order adder and producing both a sum bit and a carry-out bit. The following figure shows the three high order full adders for the three high order bits.



Overflow occurs in two cases

When $A_{15} = 0$, $B_{15} = 0$, and $S_{15} = 1$ Two positive numbers sum to a negative number

When $A_{15} = 1$, $B_{15} = 1$, and $S_{15} = 0$ Two negative numbers sum to a positive number

To understand overflow, we need only to consider the full-adder used to add the two sign bits; in this case we consider the full adder for bit 15.

A_{15}	B_{15}	C_{15}	S_{15}	C_{16}	Overflow
0	0	0	0	0	No
0	0	1	1	0	<u>YES</u>
0	1	0	1	0	Not possible
0	1	1	0	1	Not possible
1	0	0	1	0	Not possible
1	0	1	0	1	Not possible
1	1	0	0	1	<u>YES</u>
1	1	1	1	1	No

It is easy to prove that overflow is not possible when adding numbers of opposite signs. When adding two valid 16 bit numbers, overflow can occur only when the magnitude of the sum is greater than the magnitude of either of the two input numbers – this can occur only when the two numbers have the same sign. Consider the two rows $A_{15} = 0$, $B_{15} = 0$, $C_{15} = 1$, $S_{15} = 1$ and $A_{15} = 1$, $B_{15} = 1$, $C_{15} = 0$, $S_{15} = 0$.

These are the only two cases in which overflow occurs. Closer inspection of this full-adder table gives rise to a simpler method for identifying the overflow cases. Only in these two cases of overflow is $C_{16} \neq C_{15}$. For all other cases we have $C_{16} = C_{15}$. So, our overflow detector is a circuit that detects when $C_{16} \neq C_{15}$. The Exclusive OR gate is exactly what we need; $C_{16} \oplus C_{15} = 1$ if and only if $C_{16} \neq C_{15}$. Thus, the signal is generated by

$$\text{Overflow} = C_{16} \oplus C_{15}, \text{ or}$$

$$\text{Overflow} = C_{32} \oplus C_{31} \text{ for 32 bit numbers.}$$

Saturation Arithmetic

We now discuss a type of integer arithmetic in which overflow cannot occur. We consider 8-bit integers in both unsigned and two's-complement form. The range of integers representable in 8-bits is as follows:

Unsigned integers	0	to	255
Two's-Complement	-128	to	127

Saturation arithmetic is most commonly used in computer graphics, where color values may be conveniently represented as a RGB triple of 8-bit integers, one integer for each of the Red, Green, and Blue intensities of the color. In such a situation, we want the addition operator to saturate at its maximum value rather than overflow. This avoids some rather bizarre visual effects in the graphics display, such as the appearance of black spots in a white region.

The rule for saturation arithmetic is quite simple. If the value computed is not in the range representable for the data type, adjust it to the range by either setting it to the minimum or maximum value as appropriate.

Consider saturated 8-bit unsigned arithmetic. All results must be in the range $[0, 255]$, that is – at least 0 and not greater than 255.

128	+	64	=	192	as in standard arithmetic
128	+	128	=	255	in standard arithmetic this overflows as $256 > 255$. in saturation arithmetic this saturates at 255.
32	-	16	=	16	as in standard arithmetic
32	-	48	=	0	in standard arithmetic this causes an error.

The following table summarizes the difference between standard and saturation arithmetic.

Type of Arithmetic	Result Greater Than Maximum Number Representable	Result Smaller Than Minimum Number Representable
Standard Arithmetic	Error	Error
Saturation Arithmetic	Set the result to the maximum number representable	Set the result to the minimum number representable

Saturation arithmetic is used mostly in graphics cards, also called “graphical processing units”. The ALU designed for this text will not provide for saturation arithmetic.

Multiplication and Division

Here we shall study circuits to perform integer multiplication and division. We shall spend some time considering circuits to perform these operations on unsigned positive integers, and then sketch out the design of realistic circuits that operate on integers in two's-complement form. Due to the complexity of these circuits, they are not normally included in the ALU, but are placed in a related circuit called the MDU (Multiplication & Division Unit).

We note immediately that multiplication of two N -bit integers yields a product with $2N$ bits. For that reason, we shall discuss N -bit multiplication with a $2N$ -bit product, and N -bit division with a $2N$ -bit dividend, an N -bit divisor, an N -bit quotient, and N -bit remainder. This "doubling of the digits" is seen in decimal as well as binary multiplication.

Decimal: $9,999 \bullet 9,999 = 99,980,001$
 Binary $1111 \bullet 1111 = 1110\ 0001$ ($15 \bullet 15 = 225$)

The computer designed for this course will yield a 64-bit product of two 32-bit integers. The division will call for a 64-bit dividend, with 32-bit divisors, quotient, and remainder.

We begin with a consideration of multiplication for unsigned positive integers. At one level, this is quite simple, as the "times table" is very small. Here it is.

A	B	A•B
0	0	0
0	1	0
1	0	0
1	1	1

One might note that this is exactly the truth table for the logical AND function, which is denoted by the same symbol as multiplication. This might suggest the use of the logical AND gate in a multiplier; the true circuits are even simpler. Consider a labeled example.

<u>1011</u>	the multiplicand, with decimal value 11
<u>1001</u>	the multiplier, with decimal value 9
1011	
0000	
0000	the four partial products
<u>1011</u>	
1100011	the product, with decimal value 99

Note that there are four partial products, one for each bit in the multiplier. Each partial product is the length of the multiplicand, and is either a copy of the multiplicand or all 0. The standard assumption is that the multiplicand and multiplier have equal length, each having the length of the standard integer in the architecture. All commercial designs allow different lengths for integer representations (8-bit, 16-bit, 32-bit, etc.), providing a number of distinct multiplication operations (8-bit by 8-bit, 16-bit by 16-bit).

This textbook will focus on two distinct integer sizes: 4-bit unsigned integers to introduce the basic ideas of multiplication and division, and 32-bit signed two's-complement integers for the MDU as used in the design implemented in later chapters.

The above example is based on human experience with multiplication. A straightforward implementation would require four temporary registers, one for each of the partial products. As we shall quickly see, this is not necessary.

Consider the following problem, first solved in the traditional way with a slight change.

1011	Multiplicand = decimal 11
<u>0111</u>	Multiplier = decimal 7
1011	This is decimal 11
10110	This is $2 \cdot 11 =$ decimal 22
101100	This is $4 \cdot 11 =$ decimal 44
<u>0000000</u>	
01001101	$64 + 8 + 4 + 1 = 77$

Modern multiplication algorithms are based on shifting and adding. This allows one to use the minimum number of registers required to hold the operands and the results.

For this example, label the multiplier bits as $M_3M_2M_1M_0$; $M_3 = 0$, $M_2 = 1$, $M_1 = 1$, $M_0 = 1$. For 4-bit multiplication, we initialize the register set used for the product to eight 0's.

At the start, the situation is as follows.	Multiplicand	1011
	Results	00000000
$M_0 = 1$, add multiplicand to results	Multiplicand	1011
	Results	00001011
Shift the results register set right	Multiplicand	1011
	Results	00001011
$M_1 = 1$, add multiplicand to results	Multiplicand	1011
	Results	00100001
Shift the results register set right	Multiplicand	1011
	Results	00100001
$M_2 = 1$, add multiplicand to results	Multiplicand	1011
	Results	01001101
Shift the results register set right	Multiplicand	1011
	Results	01001101
$M_3 = 0$, do not add.	Multiplicand	1011
	Results	01001101


For the more general discussion of the algorithm and its implementation in hardware, we use the register names from the Multiply/Divide Unit that will be the prototype for that used in the computer we shall design. There are three registers: X, Y, and Z.

At the beginning: X contains the multiplicand and Z contains the multiplier.
Y is initialized to all zeroes.

At the end The register pair (Y, Z) contains the product.
Register X is not altered.

For this chapter, each of the three registers will be assumed to have four bits. In the design discussed later, each will be a 32-bit register. The example used will be the multiplication of 1011 (decimal 11) by 1101 (decimal 13) to get the product 1000 1111 (decimal 143).

 Here is the basic circuit diagram for the multiplier.




Here is the formal algorithm.

 
1. Initialize $C = 0$, $Y = 0$, $X = \text{multiplicand}$, $Z = \text{multiplier}$, $\text{Count} = N$.
2. At each step, examine Z_0 .
If $Z_0 = 1$, then add X and Y to put the sum in Y and set the carry bit C .
3. Right shift the register pair (Y, Z) , with $C \rightarrow Y_{N-1}$ and $Y_0 \rightarrow Z_{N-1}$. Z_0 is lost.
4. Decrement the count. If count = 0, stop. If not, go to step 2.

We now illustrate the algorithm with the example specified just above.


At the start of the multiplication, the registers are initialized as follows:
 $X = 1011$, $Y = 0000$, $Z = 1101$, and $C = 0$.




$Z_0 = 1$, so there is an addition.

 

Then there is a right shift.

 

 
Now $Z_0 = 0$, so there is no addition. The next step is another right shift.




$Z_0 = 1$, so there is an addition.

$$\begin{array}{r} 1011 \\ 0010 \\ \hline 01101 \end{array}$$

 Here, the Y register gets the 4-bit sum 1101, and the carry bit is set to $C = 0$.




Then, there is the third right shift.

 


$Z_0 = 1$, so there is an addition.

$$\begin{array}{r} 1011 \\ 0110 \\ \hline 10001 \end{array}$$

 Here, the Y register gets the 4-bit sum 0001, and the carry bit is set to $C = 1$.



 The final shift gives the product 1000 1111 (decimal 143) in the (Y, Z) register pair.



One of the advantages of two's-complement arithmetic is that such numbers can be handled as unsigned integers for the purpose of addition and subtraction. Unfortunately, the unsigned multiplication algorithm will not work for multiplication of signed integers. The algorithm most commonly implemented for two's-complement multiplication is called **Booth's algorithm**, developed by Andrew Donald Booth of Birkbeck College in London England in 1951. We shall not cover that algorithm in this text.


The Machine Division Algorithm for Unsigned Integers

Here again we shall use the register notation taken from the CDP1855, the multiplication and division chip that will form the basis for our MDU. There are three registers: X, Y, and Z. Recall that division for N-bit integers will involve a dividend of 2N bits, with a divisor, quotient, and remainder, each of N bits. Here is the standard for register usage.

At the beginning, the register pair (Y, Z) will hold the 2N-bit dividend, and the register X will hold the N-bit divisor.


At the end the register Z will hold the N-bit quotient, the register Y will hold the N-bit remainder, and the register X will hold the N-bit divisor (not changed).

 Here is the flow chart for the standard algorithm for unsigned division.



Note the key operation, which is $Y \leftarrow Y - X$. If the new value is not less than zero, a 1 is placed in the least significant bit of register Z. If the new value is negative, the value X is added back in order to restore the old value of Y. For this reason, the algorithm is called “**restoring division**”.

 Before giving an example of the algorithm, we must attend to an apparent difference between this algorithm and the mathematics on which it is based. The key operation is standard two’s-complement subtraction; take the two’s-complement of X and add it to Y. This seems to involve three registers (X, Y, and Z) as shown in the figure below.



As (Y, Z) are being considered as a single 2N-bit register, one might ask what is so special about the more significant N bits. The answer is a trick of two’s-complement arithmetic.

The basic mathematics calls for two $2N$ -bit registers: the $2N$ -bit register pair (Y, Z) and the X register extended to $2N$ bits by padding the value with N bits to the right. For example, consider the 4-bit example that will be discussed later in this chapter.

$$\begin{aligned} X &= \mathbf{0111} && \text{(Decimal 7)} \\ Y &= \mathbf{0010} \\ Z &= \mathbf{1001} && \text{(Y, Z), as an 8-bit number, have decimal value 41.} \end{aligned}$$

The algorithm defined above seems to call for the following situation.

0010	1001
0111	

The precise mathematical definition calls for this situation.

0010	1001
0111	0000

The precise mathematical procedure calls for subtracting the $2N$ -bit (here 8 bit) value at bottom from the $2N$ -bit (here 8 bit) value in the (Y, Z) register pair. To see why the first scheme works, we should consider the two's-complement of the extended X register.

For this specific example, we have the following.

$$\begin{aligned} \text{The } X \text{ register proper} & && \mathbf{0111} \\ \text{The one's-complement} & && \mathbf{1000} \\ \text{The two's-complement} & && \mathbf{1001} \\ \text{The extended } X \text{ register} & && \mathbf{0111 \ 0000} \\ \text{The one's-complement} & && \mathbf{1000 \ 1111} \\ \text{The two's-complement} & && \mathbf{1001 \ 0000} \end{aligned}$$

Adding the two's-complement of the extended X register, possibly denoted as $(X, 0)$, has the identical effect to adding the two's-complement of X to Y and not changing Z . This is precisely what the machine algorithm calls for.

To place this illustrative argument on slightly more solid ground, we present the sketch of a theoretical demonstration. Let X have N bits, $X_{N-1} \dots X_0$, and the extended X register have $2N$ bits: the original X register with N 0's appended to the right.

In taking the two's-complement of the extended X register, we begin with the following.

$$\mathbf{X_{N-1} X_{N-2} \dots X_2 X_1 X_0 0000..00}$$

The first step is to take the one's-complement, giving the following results.

$$\mathbf{\bar{X}_{N-1} \bar{X}_{N-2} \dots \bar{X}_2 \bar{X}_1 \bar{X}_0 1111..11}$$


The next step is to add 1 to this $2N$ -bit number. This causes all of the N bits to the right with value 1 to be changed to 0, and a 1 to be carried into the X_0 position.

$$\mathbf{\bar{X}_{N-1} \bar{X}_{N-2} \dots \bar{X}_2 \bar{X}_1 \bar{X}_0 \ 0000..00}$$

↖ Carry-in = 1

This is precisely the same as taking the two's-complement of X and appending the zeroes.

 In our illustration of the division algorithm, we shall take a shortcut that is not available to a standard ALU. The first subtraction, $Y \leftarrow Y - X$, is tentative. If the result is negative, the subtraction is undone by a restoring addition. Our illustration will use the rule as follows. If $Y < X$, then set $Z_0 = 0$, else set $Z_0 = 1$ and set $Y \leftarrow Y - X$. Here is the procedure.



Here is the computation $(0010, 1001)$ divided by 0111 . In decimal $41 / 7 = 5$, remainder 6.

Start with	(Y,Z)	0010 1001	
	X	0111	
Shift left	(Y,Z)	0101 0010	
	X	0111	X is bigger. Set $Z_0 = 0$.
Shift left	(Y,Z)	1010 0100	
	-X	<u>1001</u>	2's-comp of 0111 is 1001
		0011 0100	New value of Y
		0011 0101	Set $Z_0 = 1$.
Shift left	(Y,Z)	0110 1010	
	X	0111	X is bigger. Set $Z_0 = 0$.
Shift left	(Y,Z)	1101 0100	
	-X	<u>1001</u>	2's-comp of 0111 is 1001
		0110 0100	New value of Y
		0110 0101	Set $Z_0 = 1$.

At the end, we have $Z = 0101$ (the quotient is 5) and $Y = 0110$ (the remainder is 6). The value in the X register has not changed. I just display $-X$ in the example because I have difficulty with binary subtraction, much preferring to add the complement.

The Shifter

This section focuses on a common implementation of a **shift unit**, which is a circuit for achieving multiple shifts of a number of useful types. There are several types of shifters; we shall study the simpler one that uses $\log_2 N$ stages to achieve shifts by N places.

We shall first discuss the logical bases for the shifting operations and then design a sequence of shifters, each more capable than the last, in order to arrive at the final design. Along the way, we note that the main problem will be the complexity of the drawings.

Types of Shifts


In general, there are two types of shifts – left shifts and right shifts. These names correspond roughly to the way in which we would illustrate these shifts by drawing diagrams. Each of the two shift types comes in three varieties: logical, circular, and arithmetic.

The basic definition of each shift type is in terms of shifting by one place. We should note that multiple shifts are easily defined; shifting by N places must be equivalent to N single shifts. For convenience in designing a barrel shifter, we normally think in terms of shifting by $N = 2^k$, so that a shift by 13 places is a shift by 1 place, followed by a shift by 4 places, and then a shift by 8 places, as $13 = 1 + 4 + 8$.

We shall illustrate the shift types by considering them as applied to an eight-bit shift register, with contents labeled as $R_7 R_6 R_5 R_4 R_3 R_2 R_1 R_0$. We use 1001 0110 as an example.

Logical Shifts

 Logical shifts just move bits in the indicated direction, padding out with 0's. Shifts can be by any count, but shifts by more than the size of the register leave it all 0's.



For left shifting an N -bit register by 1 place

$$R_{J+1} \leftarrow R_J \quad \text{for } 0 \leq J < (N - 1)$$

$$R_0 \leftarrow 0, R_{(N-1)} \text{ is lost}$$


As an example of a shift of an 8-bit register
1001 0110 becomes 0010 1100

For right shifts by 1 place

$$R_{J+1} \rightarrow R_J \quad \text{for } 0 \leq J < (N - 1)$$

$$R_{(N-1)} \leftarrow 0, R_0 \text{ is lost}$$

 As an example of a 8-bit register shift
1001 0110 becomes 0100 1011



Left shift by 2 places: 1001 0110 becomes 0101 1000

Right shift by 2 places: 1001 0110 becomes 0010 0101

Note that shifting either left or right by eight or more places produces the result 0000 0000, so that the shift count will normally be in the range 0 through 7 inclusive.

The general rule for an N-bit register is that the shift count is usually in the range from 0 to $(N - 1)$ inclusive, a modulo-N non-negative number.

Arithmetic Shifts

Arithmetic shifts are identical to logical shifts except that the sign bits are preserved. Arithmetic shifting is normally defined only for right shifts.


For right shifts by 1 place

$$R_{J+1} \rightarrow R_J \quad \text{for } 0 \leq J < (N - 1)$$

$$R_{(N-1)} \rightarrow R_{(N-1)}, R_0 \text{ is lost}$$

As an example of an 8-bit register

1001 0110 becomes 1100 1011

 

The purpose of arithmetic shifts is to cause the right shift to become equivalent to division by two on two's-complement integers. We use 8-bit two's-complement arithmetic to illustrate the correspondence of shifting to multiplication and division. The range of this representation is from -128 to 127 inclusive.

Consider the number 52, represented as 0011 0100 in binary. Taking the two's-complement of this binary pattern, we find that the representation of -52 is 1100 1100.

We first apply successive arithmetic right shifts to both 52 and -52 .

00110100	52	11001100	-52
00011010	26	11100110	-26
00001101	13	11110011	-13
00000110	6	11111001	-7
00000011	3	11111100	-4
00000001	1	11111110	-2
00000000	0	11111111	-1


We now apply successive logical left shifts to the same two numbers.

00110100	52	11001100	-52
01101000	104	10011000	-104
11010000	-48	00110000	48
10100000	-96	01100000	96
01000000	64	11000000	-64

Note that this corresponds to multiplication by two whenever the sign bit stays the same.

Circular Shifts

 Circular shifts are identical to logical shifts except that bits “shifted off” one end are put at the other end, thus making the shift appear as a circle.



For left shifts by 1 place

$$R_{J+1} \leftarrow R_J \quad \text{for } 0 \leq J < (N-1)$$

$$R_0 \leftarrow R_{(N-1)}, \text{ nothing is lost}$$

As an example for an 8-bit shift

1001 0110 becomes 0010 1101


For right shifts by 1 place

$$R_{J+1} \rightarrow R_J \quad \text{for } 0 \leq J < (N-1)$$

$$R_{(N-1)} \leftarrow R_0$$

As an example of an 8-bit shift

1001 0110 becomes 0100 1011

 

Circular shifts are quite often used when writing code for device drivers. These drivers assign bits in a word as logical flags. Suppose that bits 3 and 2 of an 8-bit register contain a device select. We would right shift by two to get the bits into position and do a logical AND. Note that the circular shift does not lose information, as do the logical and arithmetic shifts.


Example: Let R = 0010 0101
 Right shift by 2 0100 1001
 AND 0000 0011 0000 0001 The selected device is 01.

Logical Left Shift


We begin our study of barrel shifters by presenting a very simple logical left shift circuit. As this author had to draw the circuit, it is presented as a four-bit shifter taking input $X_3X_2X_1X_0$ and outputting $Y_3Y_2Y_1Y_0$. This shifter is controlled by a signal named “SHIFT”.

If SHIFT = 0, the circuit is a copy.

 If SHIFT = 1, the circuit performs a left shift by one position.



 The basic element in this circuit is the shifter comprising two AND gates and an OR gate. The SHIFT control signal here is designated by S. There are two inputs




When $S = 0$, the input labeled IN_0 is passed to the output; when $S = 1$, the input labeled IN_1 is passed to the output. In the above circuit, we have the following connections:

- | | |
|-----------------------|----------------------------------|
| For $1 \leq N \leq 3$ | IN_0 is connected to X_N |
| | IN_1 is connected to X_{N-1} |
| For $N = 0$ | IN_0 is connected to X_0 |
| | IN_1 is connected to 0. |

In order to simplify our drawings, we use the symbol at the right to represent this simple shift/pass-through circuit. Note that the input S is output by the element as input.

 
We now present the simple left shifter diagram using our new circuit element.



The reason for the unusual alignment of the input will become obvious in the next discussion. Note that each element passes the SHIFT control signal to the next one. This is a convention used in the diagram to avoid drawing too many crossing lines.

Logical Left Shifter for Multiple Shifts

 We now present a shifter that will shift left by 0, 1, 2, or 3 places. The amount of the shift is controlled by the binary number S_1S_0 .



The shift is implemented in two stages, the first stage shifting by either 0 or 1, and the second stage shifting by either 0 or 2. This is basically a barrel shifter. The rules are


Signals		Action	Top Unit	Bottom Unit
$S_1 = 0$	$S_0 = 0$	No shift	No shift	No shift
$S_1 = 0$	$S_0 = 1$	Left shift one place	Shift by 1	No shift
$S_1 = 1$	$S_0 = 0$	Left shift two places	No shift	Shift by 2
$S_1 = 1$	$S_0 = 1$	Left shift three places	Shift by 1	Shift by 2

Allowing Circular Shifts

We now make a modification to allow selection between circular and logical shifts.

The control signal is C . If $C = 0$, the shift is logical. If $C = 1$ the shift is circular.

 One should note that even this simple shifter is associated with a circuit diagram that is increasingly hard to read.




The Two-Level 4-Bit Barrel Shifter

Another Implementation of A Left Shifter

We now present an implementation of a four-bit logical left shifter with 4-to-1 multiplexers.

 
Each output has a selection of four inputs, depending on the shift count. As above, C is the circulate control, with $C = 0$ for logical shifts and $C = 1$ for circular shifts. The shift count is specified by the binary number S_1S_0 , which is passed on by each multiplexer to the next one.



The Multiplexer-Based 4-Bit Barrel Shifter

Another Look at the 4-bit Shifter

 Our presentation of the barrel shifter will be based on the design that uses multiple levels of two-input shift units. The representation of this design, as shown above, works well for 4-bit shifters, but will become complex for a 32-bit shifter. For that reason, we show two simpler representations of the two-level four-bit barrel shifter.




Simpler Representations of the Two-Level Four-Bit Barrel Shifter

The design on the left shows the barrel shifter with each level of four shift units grouped into a single block labeled by its functionality. The figure on the right is drawn in the simplest style possible. This is the representation that we shall use.


A 32-bit Left Shifter

The figure on the right shows the general 32-bit left shifter as we shall draw such figures in order to minimize complexity. Note that it comprises five shifting levels, one each for shifts by 1, 2, 4, 8, and 16 bits. Each level is controlled by one bit of the five bit shift-count register. In a more general CPU design, this shift count register will be a part of the Instruction Register (IR). Note the control signal C, which continues to stand for Circular: C = 0 for a logical shift and C = 1 for a circular shift.

 


Logical Right Shift

As before, we begin with a basic AND/OR/NOT circuit implementing the logical right shift. Note that this is almost a mirror-image of the logical left shifter.

 
Right Shift: Logical, Arithmetic, and Circular

We now add two control signals, A for Arithmetic Shift and C for Circular Shift. Neither of these will have effect if $S = 0$, calling for no shift. When $S = 1$, the following holds

 - $A = 1$ $C = 1$ Circular right shift. This is an arbitrary decision, but the signals A and C should not be asserted simultaneously.
 $A = 1$ $C = 0$ Arithmetic right shift
 $A = 0$ $C = 0$ Logical right shift



 
In order to understand the above circuit, consider the input to the left AND gate corresponding to the Y_3 output. This gate is active when $S = 1$, indicating a shift. The operative part of the circuit, providing input when $S = 1$ is shown below.



From the above diagram we derive the truth table shown below. The student should understand that the action for the condition $A = 1$ and $C = 1$ was decided by which decision would yield the neater drawing, not by any deep consideration of architectural details.

A	C	Input
0	0	0
0	1	X_0
1	0	X_3
1	1	X_0

 The above circuit, while logically correct, “misses the forest for the trees” in that it overlooks an obvious simplification in the circuitry. What we have in the first try at the circuit for Y_3 input is an OR gate feeding another OR gate. This can be simplified.



We now trace the output of the revised and simplified circuit. When $S = 0$, there is no shift.

If $S = 0$ then $Y_3 = X_3$ (no shift), as expected.


If $S = 1$ and $C = 1$ then $Y_3 = X_0$ – for a circular shift

If $S = 1$, $C = 0$, and $A = 1$ then $Y_3 = X_3$ (copy the sign bit) for an arithmetic shift.


If $S = 1$, $C = 0$, and $A = 0$ then $Y_3 = 0$, for a logical right shift.

Again, the precedence of $C = 1$ over $A = 1$ is an arbitrary design decision

 Here is the shift-by-one level slightly redrawn to facilitate readability.




 A barrel shifter for right shifts by two is a bit more complex.




In the diagram above, each AND gate has been labeled with the input to which it corresponds. Again, all we really need to worry about is the complexity.

 Here is the two-level barrel shifter capable of shifting right by 0, 1, 2, or 3 places.



 Shown below is the two-level simplification of the above circuit.




Here is the version of the shifter that we shall use in future work. There are a number of control inputs to this circuit that determine the shifting of X_{31-0} to produce Y_{31-0} .

The shift count is a five-bit binary number, ranging in value from 0 through 31 inclusive.

There are three control signals:

- L / \overline{R} the shift direction: 0 for right shift and 1 for left shift
- A** the arithmetic shift flag, this applies only to right shifts.
If $A = 1$, we have an arithmetic shift (if $L / \overline{R} = 0$)
- C** the circular shift flag. If $C = 1$ we have a circular shift.

 Recall that we have arbitrarily decided to do a circular shift if both $A = 1$ and $C = 1$. The only requirement for this circuit is that when both shift signals are asserted, only one is done.




Commercial Chips


This section of the chapter will discuss some commercial MSI chips that once were used to implement ALUs and MDUs. While these units are no longer in use, they seem to form the logical basis for the modern ALU/MDU designs, and so will be studied. The chips to be studied are the SN74181 ALU and the CDP1855 MDU.

In order to emphasize the point above, we examine two pictures: one a labeled picture of a Pentium CPU (taken in 1993), and the other a picture of a PDP-11 CPU (vintage 1980's).

 Here is the labeled picture of the Pentium CPU. The ALU and MDU are contained in the block labeled “Superscalar Integer Execution Units”.



 Here is a picture of the PDP-11 CPU, which contains several SN74121 ALU chips.



What one should notice is that the entire Pentium CPU chip would easily fit within one of the gold squares to the upper left of the PDP-11 CPU board. The Pentium CPU is much smaller, very much faster, and much more powerful. The MSI chips we shall discuss are physically too big for modern hardware; their only relevance is logical design.

The SN74181 ALU Chip

This chip was discussed in Chapter 1 (pages 50–52) as an example of a MSI chip. That chapter includes a picture of the chip, dimensional drawings, and a circuit diagram. As this chip has influenced more modern designs, we shall discuss its functionality.

Here is the function table for the SN74181, assuming active-high inputs and outputs. Note that the output is determined by the logic mode bit, M , and the selectors $S_3S_2S_1S_0$.

Mode Select Inputs				Active High Inputs and Outputs	
S_3	S_2	S_1	S_0	Logic Mode ($M = 1$)	Arithmetic ($M = 0, C_{in} = 1$)
0	0	0	0	A'	A
0	0	0	1	$(A + B)'$	$A + B$
0	0	1	0	$A' \bullet B$	$A + B'$
0	0	1	1	Logical 0	Minus 1
0	1	0	0	$(A \bullet B)'$	A plus $A \bullet B'$
0	1	0	1	B'	$(A + B)$ plus $A \bullet B'$
0	1	1	0	$A \oplus B$	A minus B minus 1
0	1	1	1	$A \bullet B'$	$A \bullet B'$ minus 1
1	0	0	0	$A' + B$	A plus $A \bullet B$
1	0	0	1	$(A \oplus B)'$	A plus B
1	0	1	0	B	$(A + B')$ plus $A \bullet B$
1	0	1	1	$A \bullet B$	$A \bullet B$ minus 1
1	1	0	0	Logical 1	A plus A ($2A$)
1	1	0	1	$A + B'$	$(A + B)$ plus A
1	1	1	0	$A + B$	$(A + B')$ plus A
1	1	1	1	A	A minus 1

The vast array of functions available is probably a result of the design chosen. The goal seems to have been to create a simple design that would result in the desired functionality. The “extra functions” were probably the result of the simplicity of the design.

The control unit of a design based on the SN74181 would probably issue control signals for only a small subset of the possible functions. The design for the Boz-7 computer and later designs will use an ALU designed by the instructor. While the Boz-7 ALU is probably not as good as the SN74181, it is considerably easier to explain.

The CDP1855 MDU Chip

The CDP1855 is a CMOS 8-bit multiply/divide unit. These chips can be grouped in twos or fours to provide either 16-bit or 32-bit functionality.

Each CDP1855 has number of 8-bit registers, four of which concern us directly. These are the Control Register, and the three data registers: X , Y , and Z .

For multiplication, the 8-bit multiplicand and multiplier are placed in registers X and Z , with the 16-bit product found in the 16-bit register pair (Y, Z).

For division, the 16-bit dividend is placed in the 16-bit register pair (Y, Z) and the 8-bit divisor is placed in the 8-bit register X . After division, the 8-bit quotient is found in the 8-bit register Z , and the 8-bit remainder is found in 8-bit register Y .

The interesting parts of the Control Register are bits 5 and 4, and bits 1 and 0.

Bits 1 and 0 select the operation to be performed.

Bit 1	Bit 0	Operation
0	0	No operation
0	1	Multiply
1	0	Divide
1	1	Illegal

A realistic use of the CDP1855 would specify that input 11 here would be mapped to either 01 (multiply dominates) or 10 (divide dominates).

Bits 5 and 4 determine the number of CDP1855 chips being used in this particular MDU implementation. This setting determines the internal clock rates for each CDP1855.

Bit 5	Bit 4	Number of CDP1855 Chips in MDU
1	1	Four
1	0	Three
0	1	Two
0	0	One

One important feature for using the MDU is to note the relative lengths of the numbers involved. Consider a “32-bit unit”. Here are the actual lengths.

For multiplication the multiplicand and multiplier are each 32 bits in length, and the product is 64 bits in length.

For division the dividend is 64 bits in length, and each of the dividend, quotient, and remainder is 32 bits in length.

In a load/store RISC design, such as used by this author’s design, all arithmetic is done between registers. This author’s design calls for integers stored in two’s-complement form in 32-bit registers.

The solution for the 64-bit product and dividend is one that this author has borrowed from the assembly language for IBM mainframe computers, such as the z/10. It may be much more common than that. 64-bit integers will be stored in (even, odd) register pairs. For example, a 64-bit dividend stored in the register pair denoted by 6 would have the high order 32 bits stored in register 6 and the low order 32 bits stored in register 7.

The rationale behind the use of the (even, odd) register pair design is that it facilitates the design of the control unit. It appears obvious that the register pair should be of the form (R, R + 1), such as (4, 5). If the first register is an even number, one may just set the last bit to 1 and effectively add 1 to the number.

Register 6 110
Register 7 111.

Solved Problems

We now present some solved problems.


PROBLEM

1. Given a function represented by the truth table

X	Y	Z	F(X, Y, Z)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Implement this function using an 8-to-1 multiplexer and no other logic gates.

 
ANSWER: We use an eight-to-one multiplexer with three control lines C_2 , C_1 , and C_0 . Because we list X, Y, Z in that order in the function, we set $C_2 = X$, $C_1 = Y$, and $C_0 = Z$. Note that all inputs must be specified – either connected to logic 1 or logic 0.



The next two questions concern the function represented by $F(A, B, C) = \sum(0, 2, 3, 5, 6, 7)$.


3. Implement this function using an 8-to-1 multiplexer.

Answer:

 

 4. Implement this function using a 3-to-8 active-high decoder and a single NOR gate.


ANSWER: This function can be written as $F(A, B, C) = \prod(1, 4)$, that is it has the value 0 only for the rows 0 and 4 in the truth table: $A = 0, B = 0, C = 1$, and $A = 1, B = 0, C = 0$.



The next two questions focus on a Boolean function $F(W, X, Y, Z) = \Sigma(0, 3, 5, 8, A, B, C)$

- 5 Use an active-high 4-to-16 decoder and OR gates to implement this function.
 6 Use a 16-to-1 multiplexer to implement this function.

 ANSWER: Here are the two circuits. A 7-input OR gate would be acceptable.



- 7 An **active-low** decoder is one in which the selected output goes to zero and the other outputs remain at 1. Here is the description of an **enabled-low, active-low** 2-to-4 decoder. Implement this decoder using only AND, OR, and NOT gates.

Enable = 0	X1 = 0	X0 = 0	Y0 = 0	Y1 = 1	Y2 = 1	Y3 = 1
Enable = 0	X1 = 0	X0 = 1	Y0 = 1	Y1 = 0	Y2 = 1	Y3 = 1
Enable = 0	X1 = 1	X0 = 0	Y0 = 1	Y1 = 1	Y2 = 0	Y3 = 1
Enable = 0	X1 = 1	X0 = 1	Y0 = 1	Y1 = 1	Y2 = 1	Y3 = 0
Enable = 1	X1 = d	X0 = d	Y0 = 1	Y1 = 1	Y2 = 1	Y3 = 1

The circuit must have three inputs (Enable, X1, and X0) and four outputs.

ANSWER: The easiest way to do this is first ignore the Enable and draw the truth table. Basically, we have four truth tables. Lets examine them as a group and then individually.

X1	X0	Y0	Y1	Y2	Y3
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

Examining the four functions represented in the truth table, we see that each has exactly one zero and three one's in its column. This should immediately suggest POS (Product of Sums) formulations for each function. Let's look at the first function: Y0.

X1	X0	Y0	Sum Term
0	0	0	$X1 + X0$
0	1	1	
1	0	1	
1	1	1	

As an aside, note that the truth table for Y0 is exactly the truth table for the expression $(X1 + X0)$. This is the reason for making the association of the sum term to the row.

Here are the other three truth tables.

X1	X0	Y1	Sum Term
0	0	1	
0	1	0	$X1 + X0'$
1	0	1	
1	1	1	

X1	X0	Y2	Sum Term
0	0	1	
0	1	1	
1	0	0	$X1' + X0$
1	1	1	

X1	X0	Y3	Sum Term
0	0	1	
0	1	1	
1	0	1	
1	1	0	$X1' + X0'$

Without the enable input, we have the four equations.

$$Y_0 = X_1 + X_0$$

$$Y_1 = X_1 + X_0'$$

$$Y_2 = X_1' + X_0$$

$$Y_3 = X_1' + X_0'$$

Now, all we need is a way for the Enable signal to force all four of these to 1 when $E = 1$. This is easily done with an OR gate.


$$Y_0 = E + X_1 + X_0$$

$$Y_1 = E + X_1 + X_0'$$


$$Y_2 = E + X_1' + X_0$$

$$Y_3 = E + X_1' + X_0'$$

 We now show a circuit that implements these four Boolean functions.



 
We now investigate whether or not there is another implementation of this circuit. To do this, we look at using either AND or OR gates to implement this circuit, and postulate a new signal, called A , that is related to the Enable signal. We look at the two basic possibilities.



The rules of the game are simple. Either $A = 0$ means enabled or $A = 1$ means enabled. Either 1 or 0 means “select me”. The requirement on the two circuits is quite simple also: for one value of A , both outputs are the same, and for another value of A , one output is 1 and the other is 0. Once we have this, we can determine what A must be.

For the OR gates, a value of $A = 1$ makes all outputs equal 1. Thus the “select me” value must be 0 and $A = 0$ must be the enable signal. For the AND gates, a value of $A = 0$ makes all outputs equal 0. Thus the “select me” value must be 1 and $A = 1$ must be the enable.

 The statement of the problem requires that the “select me” signal be 0, so the AND gates must be changed to NAND gates or followed by a NOT gate. The new circuits are:




For the OR gate circuits on the left,

$A = 0 \Rightarrow$ the “selected” output is 0 and the other is 1
 $A = 1 \Rightarrow$ all outputs are 1.

For the NAND (AND followed by NOT) gate circuits on the right.

$A = 0 \Rightarrow$ all outputs are 1
 $A = 1 \Rightarrow$ the “selected” output is 0 and the other is 1.

 Use of the OR gate strategy, as on the left, gives rise to the circuit shown above. Use of the NAND gate strategy, as on the right, gives rise to the other valid implementation.



- 8 Consider a computer in which all integers are stored as 8 bits.
- What is the range of integer values that can be stored in two's-complement form; i.e. the most negative integer and the most positive integer.
 - What is the range of integer values that can be stored for unsigned arithmetic.
 - Perform the following sums assuming 8-bit binary arithmetic. Indicate the answer as "Overflow" if the sum cannot be represented.
 - $120 + 130$ (assuming unsigned arithmetic)
 - $120 + 130$ (assuming saturation arithmetic)
 - $140 + 150$ (assuming unsigned arithmetic)
 - $140 + 150$ (assuming saturation arithmetic)

NOTE: You can answer this without doing any binary arithmetic.

a) The range for signed 8-bit integers is given as follows:

Two's-complement - 128 through 127 inclusive.

b) The range for signed 8-bit integers is given as follows:

Unsigned arithmetic 0 through 255 inclusive.

c) $120 + 130 = 250$

$120 + 130 = 250$

$140 + 150 = \text{OVERFLOW}$

$140 + 150 = 255$ (Saturation)

PROBLEMS FOR SOLUTION

1. Design and implement a 2-to-4 decoder using only AND, OR, and NOT gates.
2. Design and implement a 4-to-1 multiplexer using only AND, OR, and NOT gates.

The next few problems are based on the following truth table.

A	B	C	F(A, B, C)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

3. Use a 3-to-8 decoder and a single 5-input OR gate to realize this function.
In other words, use these gates to design a circuit for this function.
4. Use a 3-to-8 decoder and a single 3-input NOR gate to realize this function.
5. Use an 8-to-1 multiplexer to realize this function.
6. An enabled-low active-high decoder is one for which all outputs are inactive (equal logic 0) when Enable = 1 and for which only the selected output is active (equal logic 1) when Enable = 0. Use a 1-to-4 demultiplexer to realize this circuit.