

# **Multiplexers and Demultiplexers: Description and Design Issues**

**Edward L. Bosworth, Ph.D.**  
**TSYS School of Computer Science**  
**Columbus State University**  
**Columbus, GA 31907**

# Multiplexers and Demultiplexers

## Multiplexer – MUX


Associates One of Many Inputs to a Single Output

## Demultiplexer – DEMUX

Associates One Input with One of Many Outputs

Circuit	Inputs	Control Signals	Outputs
Multiplexer	$2^N$	N	1
Demultiplexer	1	N	$2^N$

## Sample: 4-to-1 MUX and 1-to-4 DEMUX

 

My Notation: X for Input  
C for Control Signals  
Y for Output

# The Multiplexer Equation Illustrated for a 4-to-1 MUX

Truth table

Denote the multiplexer output by **M**

$C_1$	$C_0$	<b>M</b>
0	0	$X_0$
0	1	$X_1$
1	0	$X_2$
1	1	$X_3$


Equation Form

$$\mathbf{M} = \overline{C_1} \cdot \overline{C_0} \cdot X_0 + \overline{C_1} \cdot C_0 \cdot X_1 + C_1 \cdot \overline{C_0} \cdot X_2 + C_1 \cdot C_0 \cdot X_3$$

Here is another form of the equation that is better when X is used as an input.

$$\mathbf{M} = \overline{C_0} \cdot \overline{C_1} \cdot I_0 + \overline{C_0} \cdot C_1 \cdot I_1 + C_0 \cdot \overline{C_1} \cdot I_2 + C_0 \cdot C_1 \cdot I_3$$

## Build a 4-to-1 MUX

 


But what about an enable input for a multiplexer?

What does it mean for the output of the MUX to be 0?
 
## Multiplexer Attached to a Bus Line

To control a multiplexer's connection to a common bus, we use a tri-state buffer and not an enable input to the MUX. Here I use "E" as the tri-state control.




When  $E = 1$ , the selected MUX input is placed on the bus.

When  $E = 0$ , the MUX is detached from the bus; another source feeds the bus.

## A 1-to-4 DEMUX

$C_1$	$C_0$	Selected Output
0	0	$Y_0 = X$ Other outputs 0
0	1	$Y_1 = X$ Other outputs 0
1	0	$Y_2 = X$ Other outputs 0
1	1	$Y_3 = X$ Other outputs 0

# Build a 1-to-4 DEMUX With an Enable

 

If Enable = 0, all outputs are 0.



# Using A $2^N$ -to-1 MUX for a Boolean Function of N Boolean Variables

**Theorem 1:** Any Boolean function of N Boolean variables,  $N > 0$ , can be constructed by a multiplexer with  $2^N$  inputs (usually labeled  $I_K, I_{K-1}, \dots, I_1, I_0$ ) and N control lines, labeled  $C_{N-1} \dots C_0$ .

**Method:** Express the Boolean function of N Boolean variables in Canonical Sum of Products and then match the desired function to the Multiplexer Equation for a  $2^N$ -to-1 MUX.

**Example:**  $F2(X, Y, Z) = X \bullet Y + X \bullet Z + Y \bullet Z$

**Step 1:** This is a function of three Boolean variables. We must use a  $2^3$ -to-1 MUX, also called a 8-to-1 MUX.

## Using A $2^N$ -to-1 MUX (page 2)

**Step 2:** Convert  $F2(X, Y, Z) = X \bullet Y + X \bullet Z + Y \bullet Z$  to Canonical SOP.  
Every product term must have a literal for each variable.  
A literal is either the variable or its complement.

$$\begin{aligned} F2 &= X \bullet Y + X \bullet Z + Y \bullet Z \\ &= X \bullet Y \bullet (\bar{Z} + Z) + X \bullet (\bar{Y} + Y) \bullet Z + (\bar{X} + X) \bullet Y \bullet Z \\ &= X \bullet Y \bullet \bar{Z} + X \bullet Y \bullet Z + X \bullet \bar{Y} \bullet Z + X \bullet Y \bullet Z + \bar{X} \bullet Y \bullet Z + X \bullet Y \bullet Z \\ &= \bar{X} \bullet Y \bullet Z + X \bullet \bar{Y} \bullet Z + X \bullet Y \bullet \bar{Z} + X \bullet Y \bullet Z \end{aligned}$$

Note that all four terms have a literal for each of the three variables X, Y, and Z.

## Using A $2^N$ -to-1 MUX (page 3)

**Step 3:** Convert the function to a form with all  $2^N$  product terms.  
Here we convert F2 to have all eight possible product terms.

$$\begin{aligned} F(X, Y, Z) &= \bar{X} \cdot Y \cdot Z + X \cdot \bar{Y} \cdot Z + X \cdot Y \cdot \bar{Z} + X \cdot Y \cdot Z \\ &= \bar{X} \cdot \bar{Y} \cdot \bar{Z} \cdot 0 + \bar{X} \cdot \bar{Y} \cdot Z \cdot 0 + \bar{X} \cdot Y \cdot \bar{Z} \cdot 0 + \bar{X} \cdot Y \cdot Z \cdot 1 \\ &\quad + X \cdot \bar{Y} \cdot \bar{Z} \cdot 0 + X \cdot \bar{Y} \cdot Z \cdot 1 + X \cdot Y \cdot \bar{Z} \cdot 1 + X \cdot Y \cdot Z \cdot 1 \end{aligned}$$

## Using A $2^N$ -to-1 MUX (page 4)

**Step 4:** Write the Multiplexer Equation for an 8-to-1 MUX.

$$\begin{aligned} M = & \bar{C}_2 \cdot \bar{C}_1 \cdot \bar{C}_0 \cdot I_0 + \bar{C}_2 \cdot \bar{C}_1 \cdot C_0 \cdot I_1 + \bar{C}_2 \cdot C_1 \cdot \bar{C}_0 \cdot I_2 + \bar{C}_2 \cdot C_1 \cdot C_0 \cdot I_3 \\ & + C_2 \cdot \bar{C}_1 \cdot \bar{C}_0 \cdot I_4 + C_2 \cdot \bar{C}_1 \cdot C_0 \cdot I_5 + C_2 \cdot C_1 \cdot \bar{C}_0 \cdot I_6 + C_2 \cdot C_1 \cdot C_0 \cdot I_7 \end{aligned}$$

**Step 5:** Rewrite the equation with  $C_2 = X$ ,  $C_1 = Y$ , and  $C_0 = Z$ .

$$\begin{aligned} M = & \bar{X} \cdot \bar{Y} \cdot \bar{Z} \cdot I_0 + \bar{X} \cdot \bar{Y} \cdot Z \cdot I_1 + \bar{X} \cdot Y \cdot \bar{Z} \cdot I_2 + \bar{X} \cdot Y \cdot Z \cdot I_3 \\ & + X \cdot \bar{Y} \cdot \bar{Z} \cdot I_4 + X \cdot \bar{Y} \cdot Z \cdot I_5 + X \cdot Y \cdot \bar{Z} \cdot I_6 + X \cdot Y \cdot Z \cdot I_7 \end{aligned}$$


**NOTE:** Here I use  $I_0, I_1, \dots, I_7$  as the MUX inputs because I am using  $X$  to denote one of the Boolean variables.

## Using A $2^N$ -to-1 MUX (page 5)

**Step 6:** Match the two expressions

$$F(X, Y, Z) = \bar{X} \cdot \bar{Y} \cdot \bar{Z} \cdot 0 + \bar{X} \cdot \bar{Y} \cdot Z \cdot 0 + \bar{X} \cdot Y \cdot \bar{Z} \cdot 0 + \bar{X} \cdot Y \cdot Z \cdot 1 \\ + X \cdot \bar{Y} \cdot \bar{Z} \cdot 0 + X \cdot \bar{Y} \cdot Z \cdot 1 + X \cdot Y \cdot \bar{Z} \cdot 1 + X \cdot Y \cdot Z \cdot 1$$
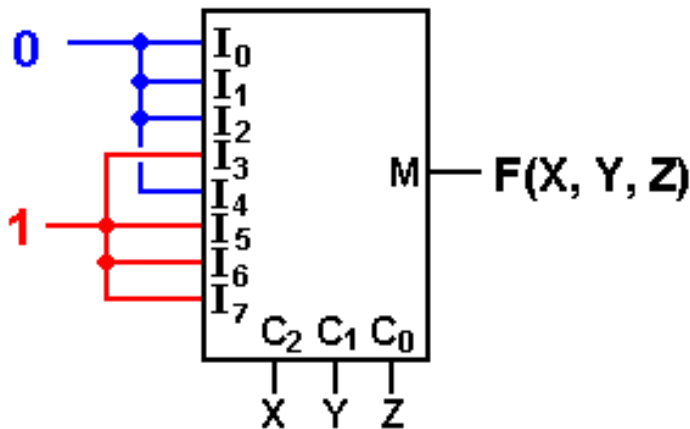
$$M = \bar{X} \cdot \bar{Y} \cdot \bar{Z} \cdot I_0 + \bar{X} \cdot \bar{Y} \cdot Z \cdot I_1 + \bar{X} \cdot Y \cdot \bar{Z} \cdot I_2 + \bar{X} \cdot Y \cdot Z \cdot I_3 \\ + X \cdot \bar{Y} \cdot \bar{Z} \cdot I_4 + X \cdot \bar{Y} \cdot Z \cdot I_5 + X \cdot Y \cdot \bar{Z} \cdot I_6 + X \cdot Y \cdot Z \cdot I_7$$



$$\begin{array}{cccc} I_0 = 0 & I_1 = 0 & I_2 = 0 & I_3 = 1 \\ I_4 = 0 & I_5 = 1 & I_6 = 1 & I_7 = 1 \end{array}$$


with  $C_2 = X$ ,  $C_1 = Y$ , and  $C_0 = Z$ .

## Using A $2^N$ -to-1 MUX (Using either a $\Sigma$ list or a $\Pi$ list)

For a  $\Sigma$  list, connect the listed inputs to 1 and the others to 0.

For a  $\Pi$  list, connect the listed inputs to 0 and the others to 1.

 
$$F(X, Y, Z) = \Sigma(3, 5, 6, 7) = \Pi(0, 1, 2, 4)$$



We try this with a common circuit emulator, such as Multi-Media Logic, and find that we need to think a bit more.
 
## An Eight-to-One MUX in Multi-Media

Here is the circuit element selected in the Multi-Media Logic tool.




This is an 8-to-1 MUX with inputs labeled 7 through 0, or equivalently  $X_7$  through  $X_0$ . This is expected.

The selector (control) lines are as expected; 2 through 0.

In my notes, I use M for the output of the Multiplexer. This figure uses the symbol Y (not a problem) and notes that real multiplexers also output the complement.

The only issue here is the enable. Note that the MUX is enabled low; this signal must be set to ground in order for the multiplexer to function as advertised.
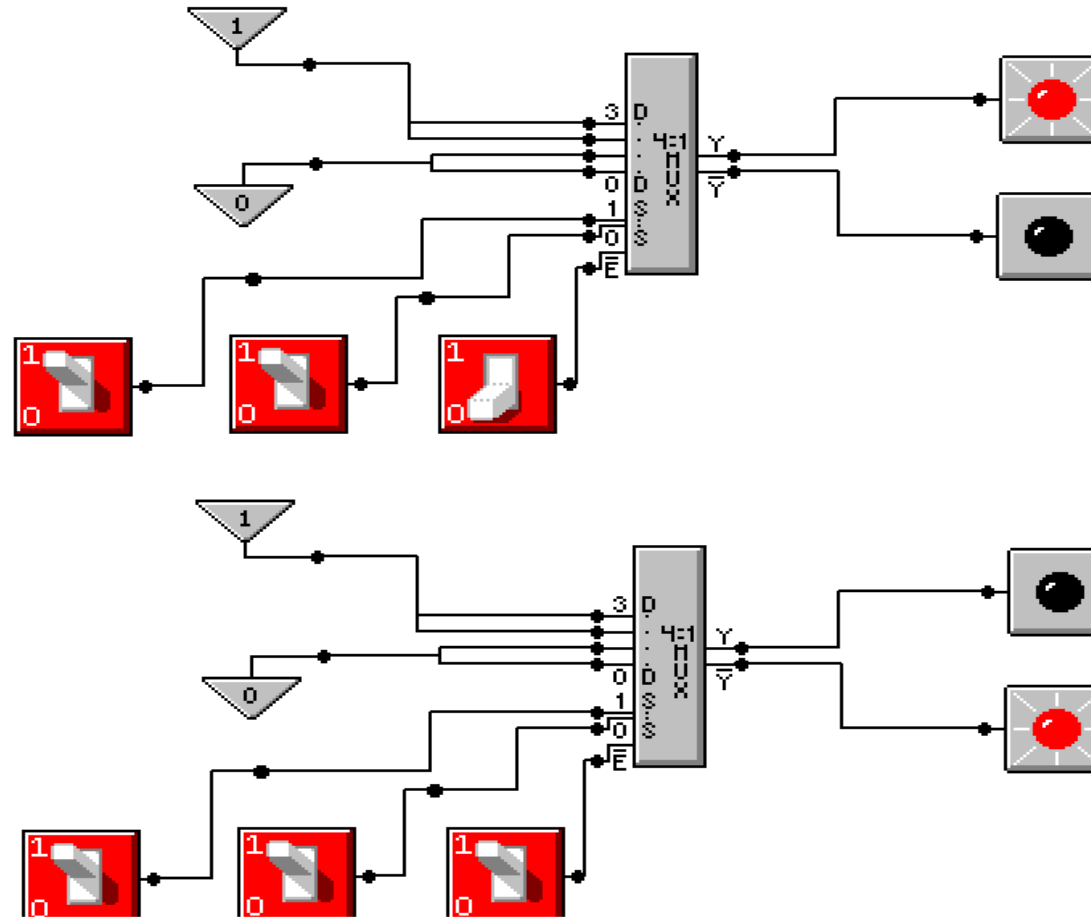
# Commercial Multiplexer: Enabled and Not Enabled




At top, the output is  $X_3$ . At bottom, the output is 0.


 
# Carry-Out of a Full Adder

Here is a screen shot of my implementation of  $F(X, Y, Z) = \Sigma(3, 5, 6, 7)$ .



NOTE: Show simulation here.

## Gray Codes: Minimal Effort Testing

Consider the above circuit with three basic inputs  $S_2, S_1, S_0$ .

How can one test all possible inputs with minimum switching?

One good answer is to use Gray Codes for input. Here are the 2-bit and 3-bit codes.

00	000
01	001
11	011
10	010
	110
	111
	101
	100

To generate an  $(N + 1)$ -bit code set from an  $N$ -bit code set.

1. Write out the  $N$ -bit codes with 0 as a prefix, then
2. Write out the  $N$ -bit codes in reverse with 1 as a prefix.

00, 01, 11, 10 becomes 000, 001, 011, 010, 110, 111, 101, and 100

## Testing the Carry-Out Circuit

If the Enable switch is set to 1, the output is always 0.  $Y' = 1$ .


Set the Enable switch to 0 and generate the following sequence.

Start with $S_2 = 0, S_1 = 0, S_0 = 0$ .	0 0 0
Click $S_0$ to get	0 0 1
Click $S_1$ to get	0 1 1
Click $S_0$ to get	0 1 0
Click $S_2$ to get	1 1 0
Click $S_0$ to get	1 1 1
Click $S_1$ to get	1 0 1
Click $S_0$ to get	1 0 0
 
## Where are the Decoders?

One will note that the Multi-Media Logic tool does not provide a decoder circuit.

Fortunately, a 1-to- $2^N$  demultiplexer can be made into an N-to- $2^N$  decoder.




Look at the circuit to the left. The control signals  $C_1, C_0$  select the output to receive the input  $X$ . This is exactly equivalent to a decoder.

In the circuit at right, the selected output gets the input, now called “Enable”. For the demultiplexers we use, the other outputs get a logic 1.

We can fabricate an active low decoder.
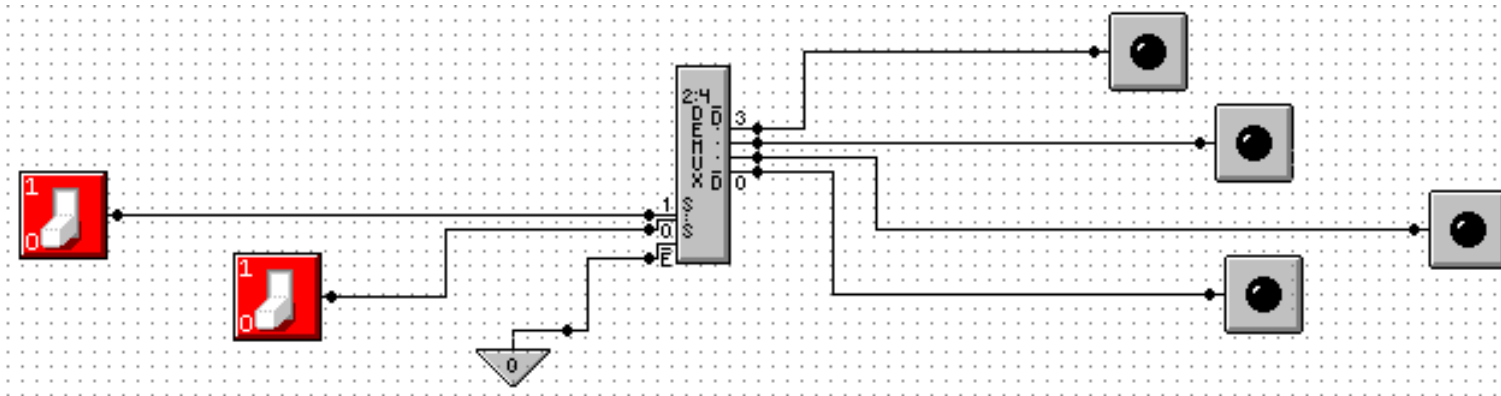
## The MUX as an Active-Low Decoder

Here is the 2-to-4 Demultiplexer as an 2-to-4 active low decoder.



Here is an answer to one of the homework problems: use a 2-to-4 decoder for XOR. The function is either  $\Sigma(1, 2)$  or  $\Pi(0, 3)$ .

