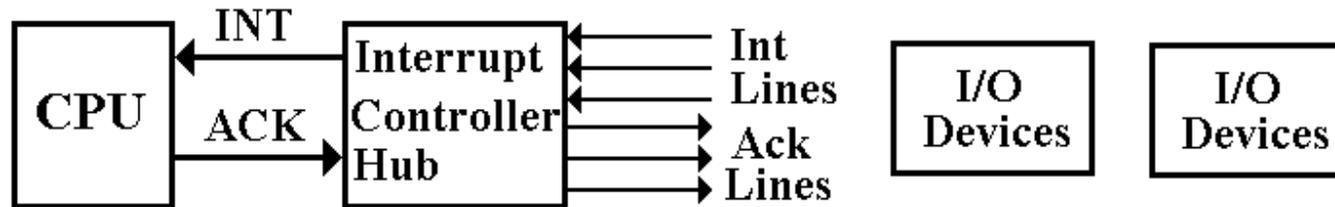


# Structure of an Interrupt Handler

I/O devices and their controllers fall into three major classes.

1. Program Controlled
2. Interrupt Driven
3. Direct Memory Access

Of these classes, only the latter two can generate interrupts. Here we focus on how the CPU processes the interrupts associated with such devices.



This lecture focuses on what I call the “Interrupt Controller Hub”.

This hub processes interrupts from multiple devices and sends a single INT signal to the CPU when an interrupt is recognized.

The CPU sends a single ACK signal back to the hub, which sends it to the appropriate device.

## Interrupt Priority and CPU Priority

We follow the design of the PDP-11, developed by the Digital Equipment Corporation (now defunct) in discussing an interrupt structure.

We begin with the idea of a CPU execution priority. This is specified by a 3-bit number in the program status register (PSR). Here is the structure that we shall use.

Bits	15 – 8	7	6	5	4	3	2	1	0
Use	Other Uses	N	Z	V	C	I	CPU Priority		

We postulate a 16-bit program status register with the following bits:

N, Z, V, & C	Status of the previous arithmetic operation (Always included in the PSR, so we use these too)
I	Interrupts enabled. When I = 0, the CPU ignores any interrupt.
Priority	A 3-bit unsigned integer representing the CPU execution priority.

# The I Bit and CPU Execution Priority

These four bits are used in processing interrupts.

## Disabling Interrupts ( $I = 0$ )

This should be done very seldom. Only the Operating System can set the I bit.

There are certain times in processing an interrupt during which another interrupt cannot be processed. During these short times, the CPU sets  $I = 0$ .

## CPU Priority

Normal programming practice allows for multiple interrupt priorities and nested interrupts. A high priority device, such as a disk, can take precedence over the processing of an interrupt for a low priority device, such as a keyboard.

To manage devices at various priorities, each interrupt is processed as follows.

1. A device interrupts with priority K.
2. The CPU sets  $I = 0$  and saves various registers.
3. The CPU sets its priority to K (the same number), sets  $I = 1$ , and then begins execution of the interrupt handler.

Devices with higher priorities can now interrupt and have their interrupts handled.

## More on CPU Priority

We follow the PDP-11 convention.

Priority = 0                      All user programs execute at this level.

Priority = 1, 2, 3              Various Operating System Utilities operate at these levels.  
We generally ignore these levels.

Priority = 4, 5, 6, 7          Interrupt handlers operate at these levels.

The CPU will acknowledge and process an interrupt only if the priority of the interrupting device is higher than the CPU execution priority.

For this reason, almost all interrupt handlers are written to execute with a CPU priority exactly equal to the device priority.

The convention is that all hardware devices are assigned one of four interrupt levels: 4, 5, 6, and 7.

Priority 4              is the lowest hardware priority, reserved for the keyboard, etc.

Priority 7              is the highest hardware priority, reserved for disks, etc.

# Vectored Interrupts

How does the CPU identify the device that asserted the interrupt and begin execution of its interrupt handler? More on this later, but for now:


1. The device sends its “vector”, which is an address of a data structure. This is most often an address in low memory, say addresses 0 – 1023.
2. The data structure at the specified address contains the following.
  - a) The address of the interrupt handler associated with the device.
  - b) The CPU execution priority for the interrupt handler.

The interrupt handling sequence can be elaborated.

1. Clear the Interrupt Enabled bit (set  $I = 0$ ) to block other interrupts.
2. Store the essential registers, so that the user program can be restarted later.
3. Load the PSR with the execution priority and load the PC with the address.
4. Set  $I = 1$  to allow nested interrupts and start execution of the handler.
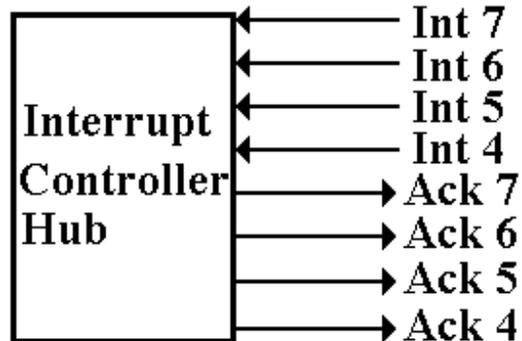
## Interrupt Lines and Assertion Levels

The structure of the interrupt lines on our computer is as follows:




We have four interrupt lines, one for each of the four priority levels. Each is paired with an acknowledge line for the same priority.

Interrupts are **asserted low**; that is, the signal goes to 0 when the device interrupts.

Acknowledgements are **asserted high**; that is, the signal goes to logic 1 to acknowledge.
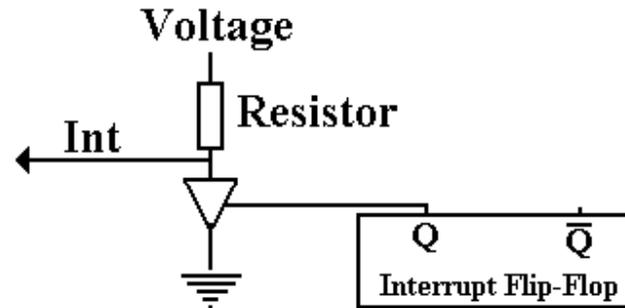
## Mechanism for Asserting an Interrupt

Each interrupt line is attached to a “pull down” resistor.




When the device asserts an interrupt, it sets its Interrupt Flip-Flop. Thus  $Q = 1$ . This enables the tri-state, which becomes a closed switch with very low resistance.

With the tri-state enabled, all the voltage drop is across the resistor so that the voltage on the Interrupt Line becomes 0. The interrupt is asserted.

With the tri-state disabled, it becomes an open switch, a line with very high resistance. All the voltage drop is across the tri-state, so the Interrupt Line stays at voltage.
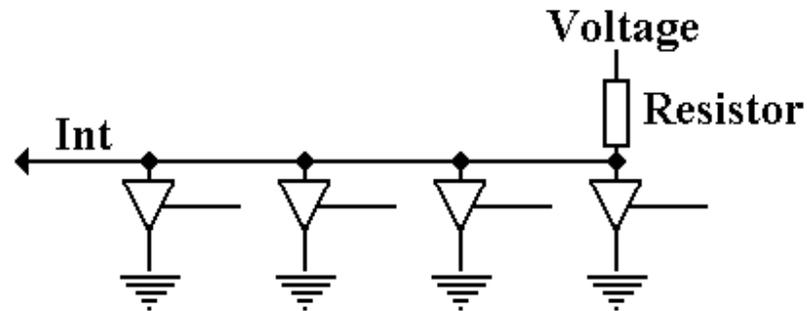
## Multiple Devices on One Line

By design, Interrupts are active low in order to facilitate attaching multiple interrupting devices on a single interrupt line.



Here we see four devices attached to a single line.

If no device is interrupting, we have  $\text{Int} = \text{Logic } 1$


If any one device is interrupting, we have  $\text{Int} = \text{Logic } 0$ . The interrupt is asserted.

If more than one device is interrupting, we still have  $\text{Int} = \text{Logic } 0$ .

The devices cannot interfere with each other.

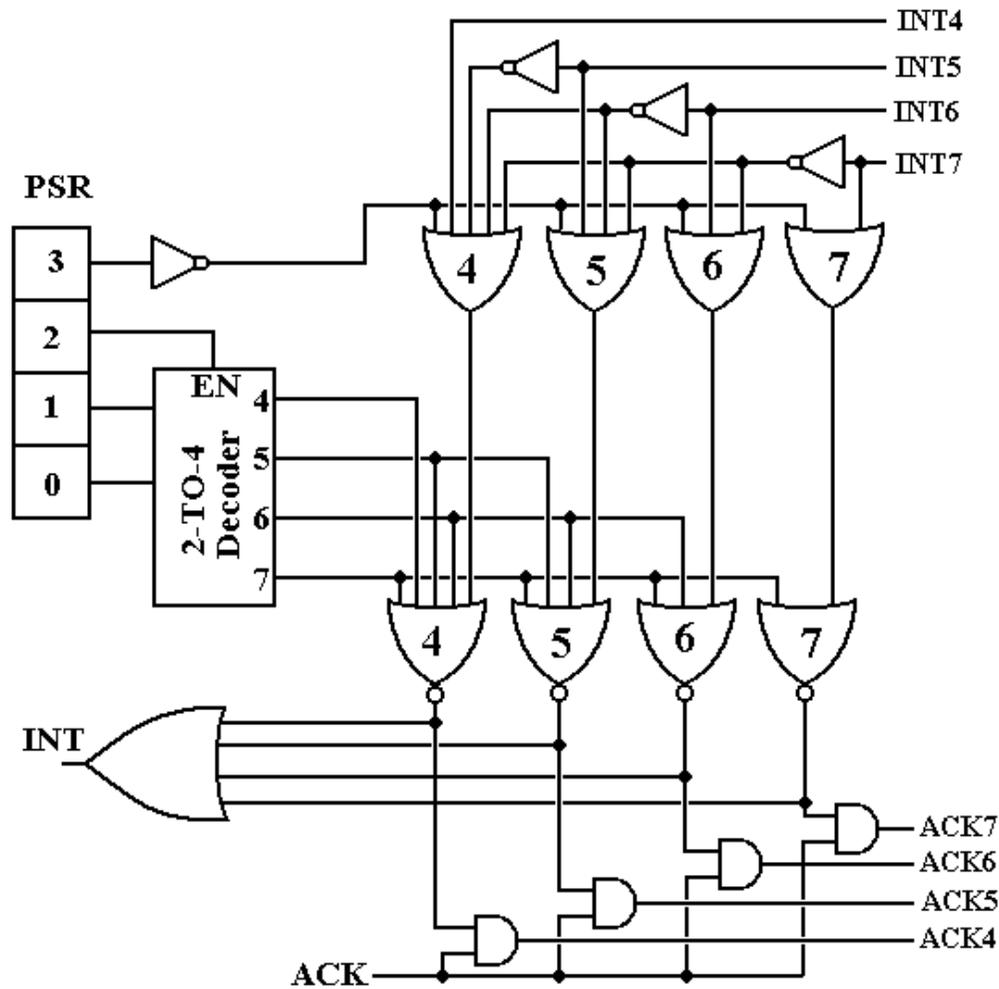
# The Big Picture

Here is the entire circuit for the controller hub.



# The Hub: Part 1

Look first at the output of the PSR.

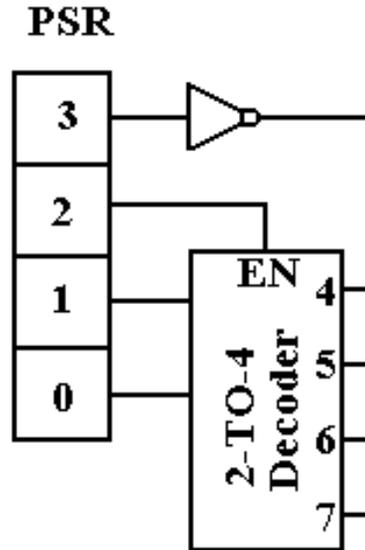


If  $PSR_3 = 0$ , the output of the not gate is 1. We see later how this disables interrupts.

If  $PSR_2 = 0$ , the CPU execution priority is less than 4. This is less than the priority of any I/O device.

If  $PSR_2 = 1$ , the output of the 2-to-4 decoder indicated the CPU execution priority, which must be in the range 4 to 7 inclusive.
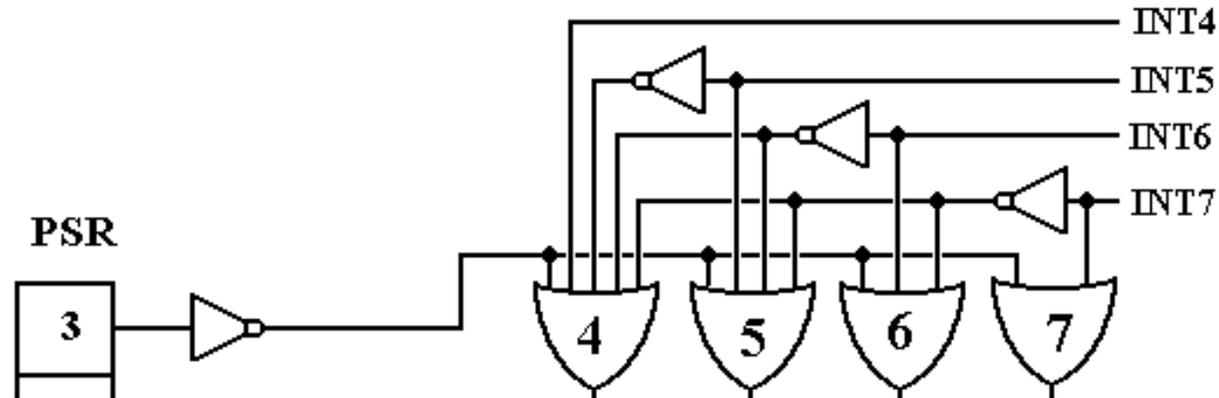
## The Hub: Part 2

Remember that interrupts are asserted low. This circuit has at most one of its outputs equal to 0. The rest are 1. Possibly all are logic 1.



If  $PSR_3 = 0$ , the input from the left is logic 1, and the output of each of the four OR gates is also 1. No interrupt is recognized.


If all of Int4, Int5, Int6 and Int7 are logic 1 there is no interrupt being asserted.

The output of each of the four OR gates is also 1 and no interrupt is recognized.

Suppose  $Int7 = 1$  and  $Int6 = 0$ . The output of OR gate 7 is 1. The output of OR gate 6 is logic 0. Since the negation of Int6 goes into OR gates 4 and 5, the output of each of those gates is 1. Thus only one gate has a logic 0 output.
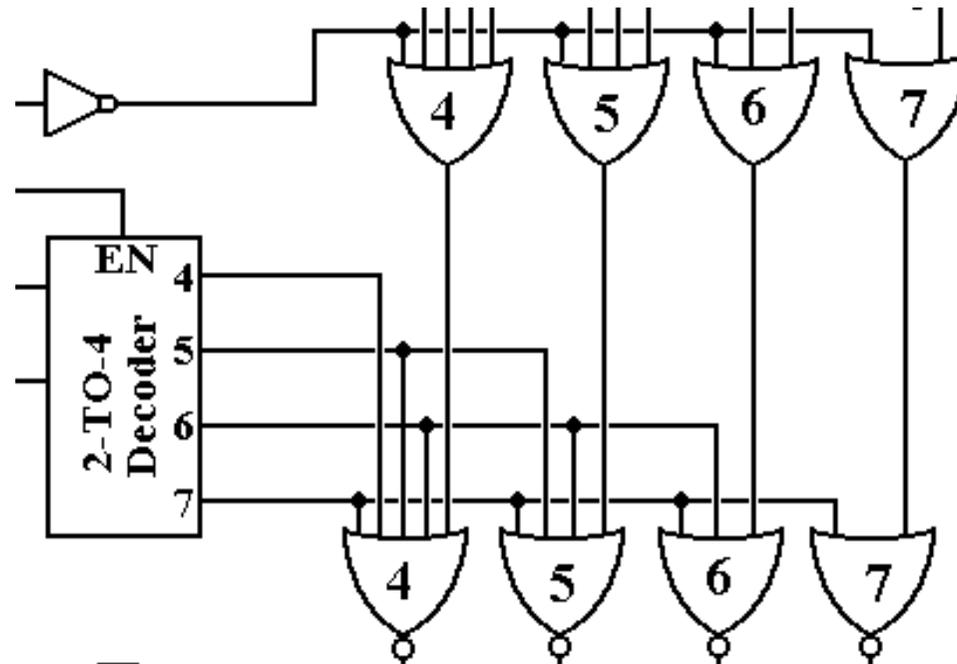
## The Hub: Part 3

At this point, either all of the OR gates at the top are outputting a logic 1, or exactly one has output of logic 0.




The NOR gates at the bottom are a key point of converting the active low device interrupt to an active high acknowledgement signal.

If all OR gates output a logic 1, each of the NOR gates will output a logic 0. No acknowledgement will be generated.
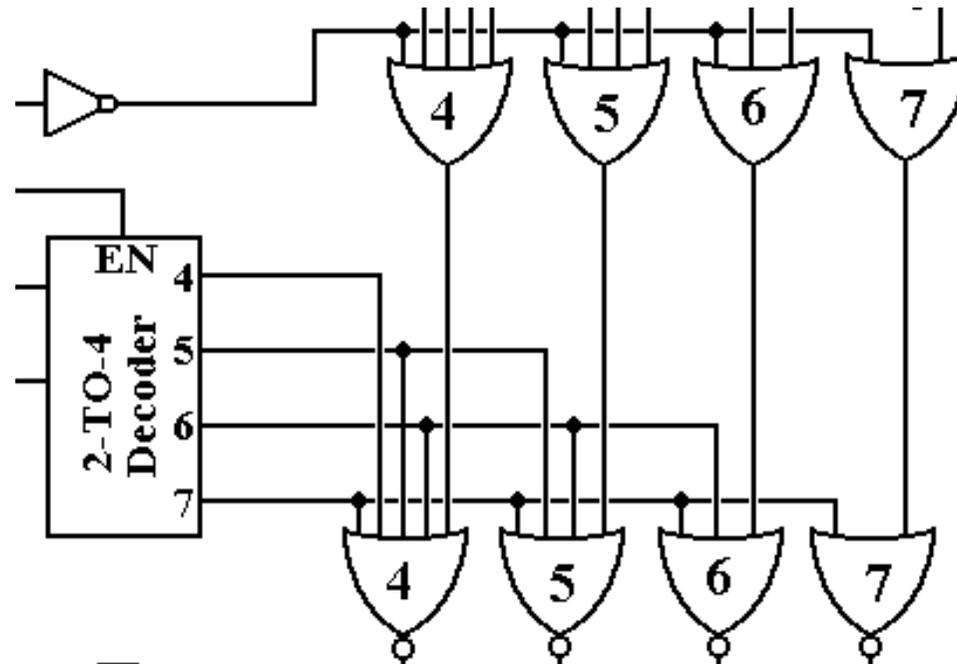
## The Hub: Part 4

We now consider what happens when exactly one of the OR gates at the top has an output of logic 0. Say that OR gate 5 has an output of logic 0.




Each of NOR gates 4, 6, and 7 will have an output of 0.

NOR gate 5 will have an output of logic 1 if and only if all of its inputs are 0. Look at the decoder. This will occur only if the CPU priority is less than 5.


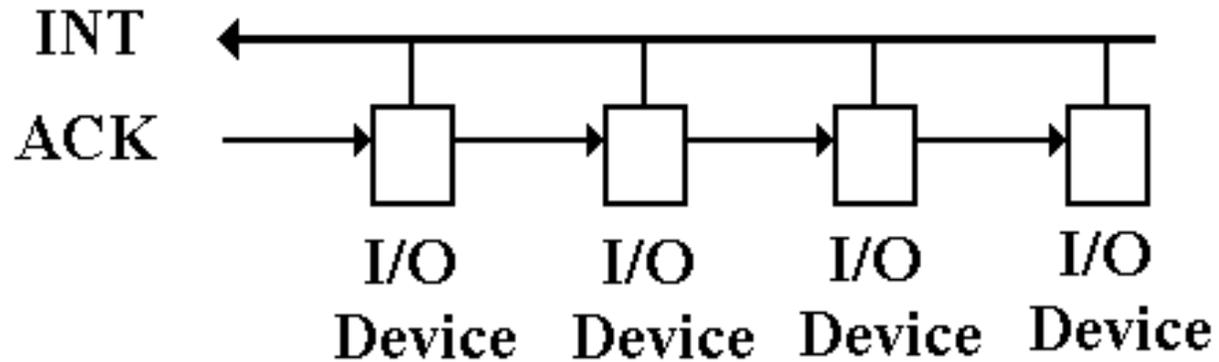
## Daisy Chaining

In daisy chaining, the ACK is passed from device to device until it hits a device that has asserted an interrupt.



If the I/O device has not asserted an interrupt, it passes the ACK to the next “downstream” I/O device.

Priority rank is by physical proximity to the CPU.

## Daisy Chaining (Part 2)

The ACK is passed down the line to the first I/O device attached.

If that device has not raised an interrupt, it passes the ACK to the next device.

When a device that asserted an interrupt gets the ACK, it captures it and does not pass it.

