

Chapter 6 – Basics of the Memory System

We now give an overview of RAM – **R**andom **A**ccess **M**emory. This is the memory called “primary memory” or “core memory”. The term “core” is a reference to an earlier memory technology in which magnetic cores were used for the computer’s memory. This discussion will pull material from a number of chapters in the textbook.

Primary computer memory is best considered as an array of addressable units. Addressable units are the smallest units of memory that have independent addresses. In a byte-addressable memory unit, each byte (8 bits) has an independent address, although the computer often groups the bytes into larger units (words, long words, etc.) and retrieves that group. Most modern computers manipulate integers as 32-bit (4-byte) entities, so retrieve the integers four bytes at a time.

In this author’s opinion, byte addressing in computers became important as the result of the use of 8-bit character codes. Many applications involve the movement of large numbers of characters (coded as ASCII or EBCDIC) and thus profit from the ability to address single characters. Some computers, such as the CDC-6400, CDC-7600, and all Cray models, use word addressing. This is a result of a design decision made when considering the main goal of such computers – large computations involving integers and floating point numbers. The word size in these computers is 60 bits (why not 64? – I don’t know), yielding good precision for numeric simulations such as fluid flow and weather prediction.

Memory as a Linear Array

Consider a byte-addressable memory with N bytes of memory. As stated above, such a memory can be considered to be the logical equivalent of a C++ array, declared as

```
byte memory[N] ; // Address ranges from 0 through (N - 1)
```

The computer on which these notes were written has 512 MB of main memory, now only an average size but once unimaginably large. $512 \text{ MB} = 512 \cdot 2^{20} \text{ bytes} = 2^{29} \text{ bytes}$ and the memory is byte-addressable, so $N = 512 \cdot 1048576 = 536,870,912$.

The term “**random access**” used when discussing computer memory implies that memory can be accessed at random with no performance penalty. While this may not be exactly true in these days of virtual memory, the key idea is simple – that the time to access an item in memory does not depend on the address given. In this regard, it is similar to an array in which the time to access an entry does not depend on the index. A magnetic tape is a typical **sequential access device** – in order to get to an entry one must read over all previous entries.

There are two major types of random-access computer memory. These are: **RAM** (Read-Write Memory) and **ROM** (Read-Only Memory). The usage of the term “RAM” for the type of random access memory that might well be called “RWM” has a long history and will be continued in this course. The basic reason is probably that the terms “RAM” and “ROM” can easily be pronounced; try pronouncing “RWM”. Keep in mind that both RAM and ROM are random access memory.

Of course, there is no such thing as a pure Read-Only memory; at some time it must be possible to put data in the memory by writing to it, otherwise there will be no data in the memory to be read. The term “Read-Only” usually refers to the method for access by the CPU. All variants of ROM share the feature that their contents cannot be changed by normal CPU write operations. All variants of RAM (really Read-Write Memory) share the feature that their contents can be changed by normal CPU write operations. Some forms of ROM have their contents set at time of manufacture, other types called **PROM** (Programmable ROM), can have contents changed by special devices called PROM Programmers.

Pure ROM is more commonly found in devices, such as keyboards, that are manufactured in volume, where the cost of developing the chip can be amortized over a large production volume. PROM, like ROM, can be programmed only once. PROM is cheaper than ROM for small production runs, and provides considerable flexibility for design. There are several varieties of **EPROM** (Erasable PROM), in which the contents can be erased and rewritten many times. There are very handy for research and development for a product that will eventually be manufactured with a PROM, in that they allow for quick design changes.

We now introduce a new term, “**shadow RAM**”. This is an old concept, going back to the early days of MS-DOS (say, the 1980’s). Most computers have special code hardwired into ROM. This includes the BIOS (Basic Input / Output System), some device handlers, and the start-up, or “boot” code. Use of code directly from the ROM introduces a performance penalty, as ROM (access time about 125 to 250 nanoseconds) is usually slower than RAM (access time 60 to 100 nanoseconds). As a part of the start-up process, the ROM code is copied into a special area of RAM, called the **shadow RAM**, as it shadows the ROM code. The original ROM code is not used again until the machine is restarted.

The Memory Bus


The Central Processing Unit (CPU) is connected to the memory by a high-speed dedicated point-to-point bus. All memory busses have the following lines in common:

1. **Control lines.** There are at least two, as mentioned in Chapter 3 of these notes. The **Select#** signal is asserted low to activate the memory and the **R/W#** signal indicates the operation if the memory unit is activated.
2. **Address lines.** A modern computer will have either 32 or 64 address lines on the memory bus, corresponding to the largest memory that the design will accommodate.
3. **Data Lines.** This is a number of lines with data bits either being written to the memory or being read from it. There will be at least 8 data lines to allow transfer of one byte at a time. Many modern busses have a “**data bus width**” of 64 bits; they can transfer eight bytes or 64 bits at one time. This feature supports cache memory, which is to be discussed more fully in a future chapter of this text.
4. **Bus clock.** If present, this signal makes the bus to be a **synchronous bus**. Busses without clock signals are **asynchronous busses**. There is a special class of RAM designed to function with a synchronous bus. We investigate this very soon.

Modern computers use a synchronous memory bus, operating at 133 MHz or higher. The bus clock frequency is usually a fraction of the system bus; say a 250 MHz memory bus clock derived from a 2 GHz (2,000 MHz) system clock.


Memory Registers

Memory is connected through the memory bus to the CPU via two main registers, the **MAR** (Memory Address Register) and the **MBR** (Memory Buffer Register). The latter register is often called the **MDR** (Memory Data Register). The number of bits in the MAR matches the number of address lines on the memory bus, and the number of bits in the MBR matches the number of data lines on the memory bus. These registers should be considered as the CPU's interface to the memory bus; they are logically part of the CPU.

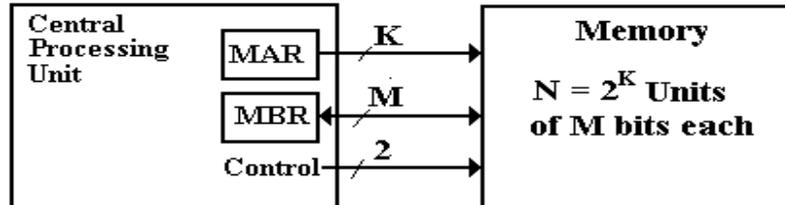

Memory Timings

There are two ways to specify memory speed: access time and the memory clock speed. We define each, though the access time measure is less used these days. Basically the two measures convey the same information and can be converted one to the other. The memory access time is defined in terms of reading data from the memory. It is the time between the address becoming stable in the MAR and the data becoming available in the MBR. In modern memories this time can range from 5 nanoseconds (billionths of a second) to 150 nanoseconds, depending on the technology used to implement the memory. More on this will be said very soon.

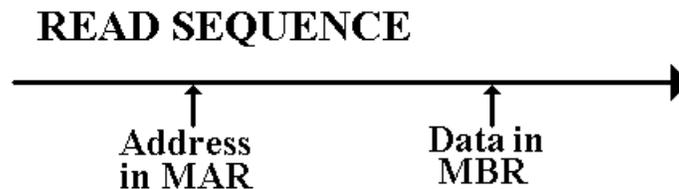

When the memory speed is specified in terms of the memory clock speed, it implies an upper limit to the effective memory access time. The speed of a modern memory bus is usually quoted in MHz (megahertz), as in 167 MHz. The actual unit is inverse seconds (sec^{-1}), so that 167 MHz might be read as "167 million per second". The bus clock period is the inverse of its frequency; in this case we have a frequency of $1.67 \cdot 10^8 \text{ sec}^{-1}$, for a clock period of $\tau = 1.0 / (1.67 \cdot 10^8 \text{ sec}^{-1}) = 0.6 \cdot 10^{-8} \text{ sec} = 6.0 \text{ nanoseconds}$.

Memory Control

Just to be complete, here are the values for the two memory control signals.

Select#	R/W#	Action
1	0	Memory contents are not changed or accessed. Nothing happens.
1	1	
0	0	CPU writes data to the memory.
0	1	CPU reads data from the memory.

Registers and Flip-Flops

One basic division of memory that is occasionally useful is the distinction between registers and memory. Each stores data; the basic difference lies in the logical association with the CPU. Most registers are considered to be part of the CPU, and the CPU has only a few dozen registers. Memory is considered as separate from the CPU, even if some memory is often placed on the CPU chip. The real difference is seen in how assembly language handles each of the two.


Although we have yet to give a formal definition of a flip-flop, we can now give an intuitive one. A flip-flop is a “bit box”; it stores a single binary bit. By $Q(t)$, we denote the state of the flip-flop at the present time, or present tick of the clock; either $Q(t) = 0$ or $Q(t) = 1$. The student will note that throughout this textbook we make the assumption that all circuit elements function correctly, so that any binary device is assumed to have only two states.

A flip-flop must have an output; this is called either Q or $Q(t)$. This output indicates the current state of the flip-flop, and as such is either a binary 0 or a binary 1. We shall see that, as a result of the way in which they are constructed, all flip-flops also output $\overline{Q(t)}$, the complement of the current state. Each flip-flop also has, as input, signals that specify how the next state, $Q(t + 1)$, is to relate to the present state, $Q(t)$. The flip-flop is a synchronous sequential circuit element.


The Clock

The most fundamental characteristic of synchronous sequential circuits is a system clock. This is an electronic circuit that produces a repetitive train of logic 1 and logic 0 at a regular rate, called the **clock frequency**. Most computer systems have a number of clocks, usually operating at related frequencies; for example – 2 GHz, 1GHz, 500MHz, and 125MHz. The inverse of the clock frequency is the **clock cycle time**. As an example, we consider a clock with a frequency of 2 GHz ($2 \cdot 10^9$ Hertz). The cycle time is $1.0 / (2 \cdot 10^9)$ seconds, or $0.5 \cdot 10^{-9}$ seconds = 0.500 nanoseconds = 500 picoseconds.


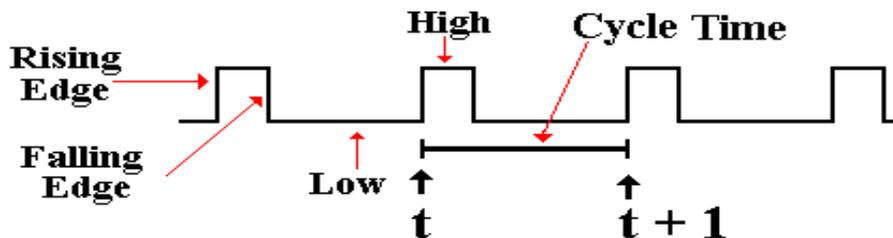
Synchronous sequential circuits are sequential circuits that use a **clock input** to order events. The following figure illustrates some of the terms commonly used for a clock.




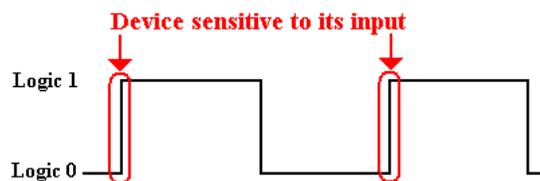
The **clock input** is very important to the concept of a sequential circuit. At each “tick” of the clock the output of a sequential circuit is determined by its input and by its state. We now provide a common definition of a “**clock tick**” – it occurs at the **rising edge** of each pulse. By definition, a flip-flop is sensitive to its input only on the rising edge of the system clock.



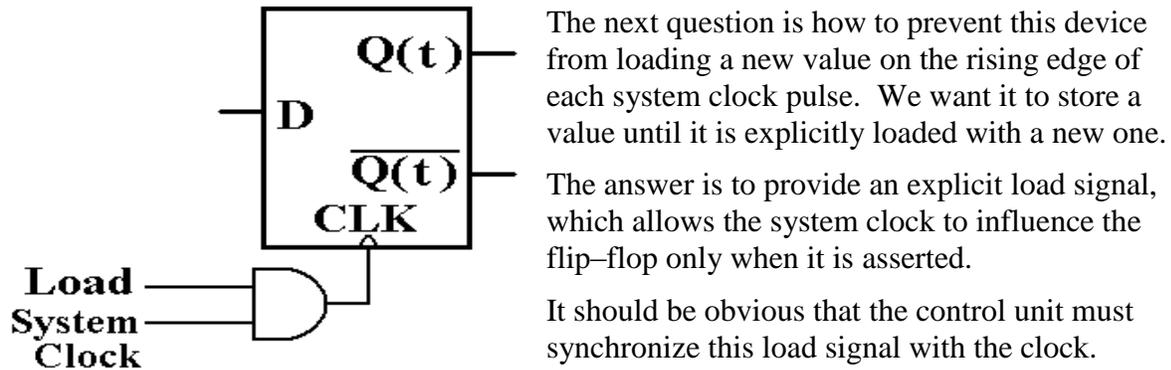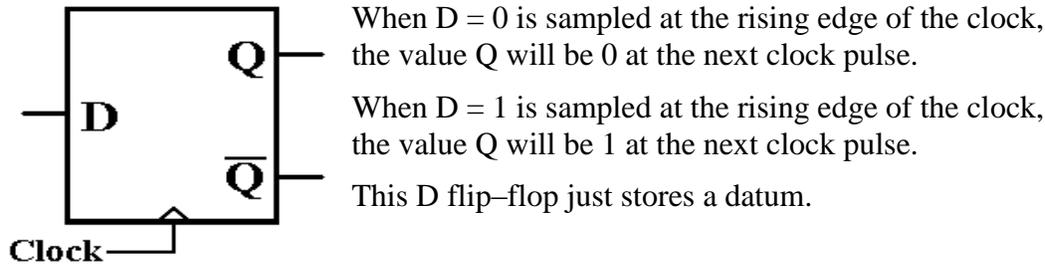There are four primary types of flip-flop: SR (Set Reset), JK, D (Data) and T (Toggle). We concern ourselves with only two: the D and the T. The D flip-flop just stores whatever input it had at the last clock pulse sent to it. Here is one standard representation of a D flip-flop.




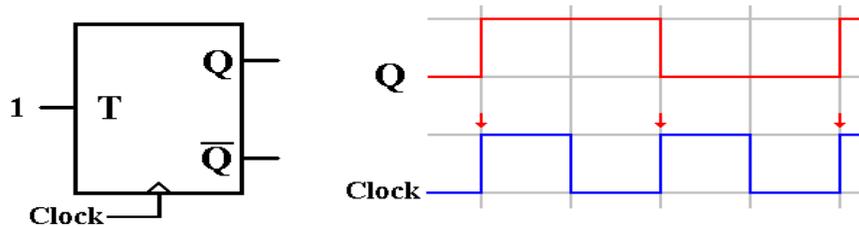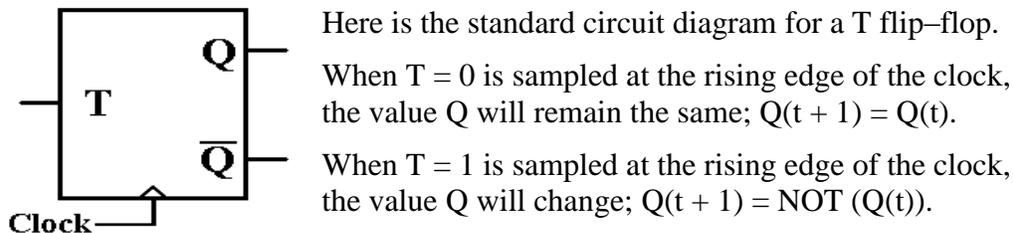The **T flip-flop** is one that retains its state when $T = 0$ and changes it when $T = 1$.



In this circuit, the input is kept at $T = 1$. This causes the value of the output to change at every rising edge of the clock. This causes the output to resemble the system clock, but at half of the frequency. This circuit is a frequency divider.

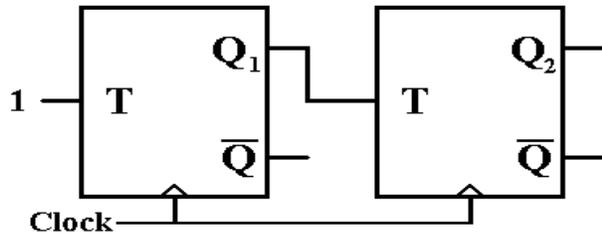
The next circuit suggests the general strategy for a frequency divider.



The circuit at left shows two T flip-flops, in which the output of T_1 is the input to T_2 .

When the output of T_1 goes high, T_2 changes at the rise of the next clock pulse.


Here is the timing for this circuit.

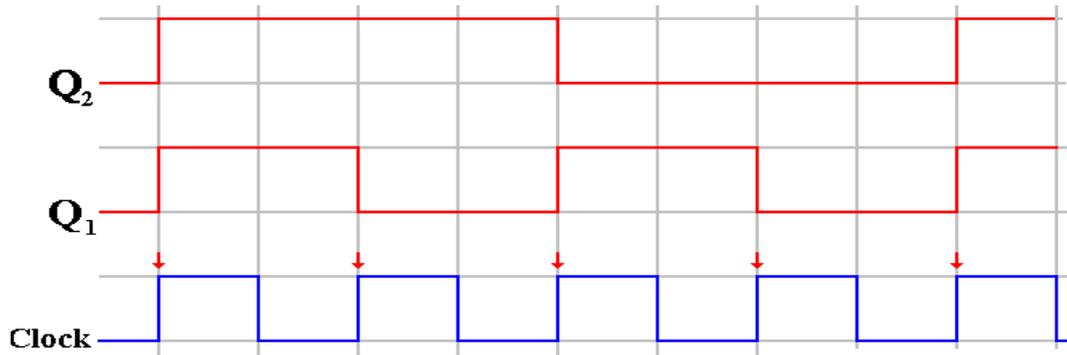

Note that Q_1 is a clock signal at half the frequency of the system clock, and Q_2 is another clock signal at one quarter the frequency of the system clock. This can be extended to produce frequency division by any power of two. Frequency division by other integer values can be achieved by variants of shift registers, not studied in this course.

The Basic Memory Unit

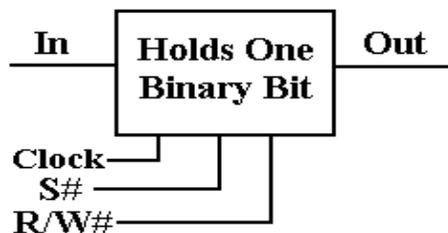All computer memory is ultimately fabricated from basic memory units. Each of these devices stores one binary bit. A register to store an 8-bit byte will have eight basic units. Here is a somewhat simplified block diagram of a basic memory unit.




There are two data lines: Input (a bit to be stored in the memory) and Output (a bit read from the memory).

There are two basic control lines. $S\#$ is asserted low to select the unit, and $R/W\#$ indicates whether it is to be read or written to. The Clock is added to be complete.

At present, there are three technologies available for main RAM. These are magnetic core memory, static RAM (SRAM) and dynamic RAM (DRAM). Magnetic core memory was much used from the mid 1950's through the 1980's, slowly being replaced by semiconductor memory, of which SRAM and DRAM are the primary examples.

At present, magnetic core memory is considered obsolete, though it may be making a comeback as MRAM (Magnetic RAM). Recent product offerings appear promising, though not cost competitive with semiconductor memory. For the moment, the only echo of magnetic core memory is the occasional tendency to call primary memory "core memory"

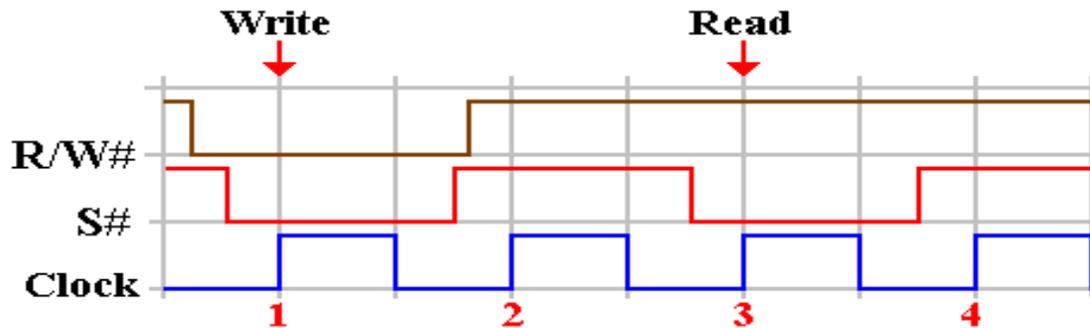Here is a timing diagram for such a memory cell, showing a write to memory, followed by an idle cycle, then a read from memory. Note the relative timings of the two control signals $S\#$ and $R/W\#$. The important point is that each has its proper value at the rising edge of the clock. Here they are shown changing values at some vague time before the clock rising edge.




At the rising edge of clock pulse 1, we have $R/W\# = 0$ (indicating a write to memory) and $S\# = 0$ (indicating the memory unit is selected). The memory is written at clock pulse 1.

At the rising edge of clock pulse 2, $S\# = 1$ and the memory is inactive. The value of $R/W\#$ is not important as the memory is not doing anything.

At the rising edge of clock pulse 3, $R/W\# = 1$ (indicating a read from memory) and $S\# = 0$. The memory is read and the value sent to another device, possibly the CPU.

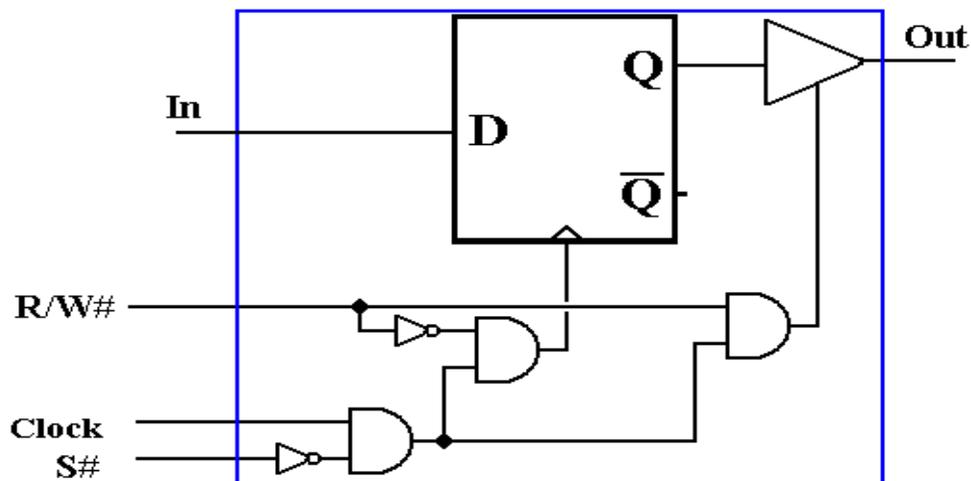As indicated above, there are two primary variants of semiconductor read/write memory. The first to be considered is SRAM (Static RAM) in which the basic memory cell is essentially a D flip-flop. The control of this unit uses the conventions of the above timing diagram.



When $S\# = 1$, the memory unit is not active. It has a present state, holding one bit. That bit value (0 or 1) is maintained, but is not read. The unit is disconnected from the output line.

When $S\# = 0$ and $R/W\# = 0$, the flip-flop is loaded on the rising edge of the clock. Note that the input to the flip-flop is always attached to whatever bus line that provides the input. This input is stored only when the control signals indicate.


When $S\# = 0$ and $R/W\# = 1$, the flip-flop is connected to the output when the clock is high. The value is transferred to whatever bus connects the memory unit to the other units.

The Physical View of Memory

We now examine two design choices that produce easy-to-manufacture solutions that offer acceptable performance at reasonable price. The basic performance of DRAM chips has not changed since the early 1990s'; the basic access time is in the 50 to 80 nanosecond range, with 70 nanoseconds being typical. The first design option is to change the structure of the main DRAM memory. We shall note a few design ideas that can lead to a much faster memory. The second design option is to build a memory hierarchy, using various levels of cache memory, offering faster access to main memory. As mentioned above, the cache memory will be faster SRAM, while the main memory will be slower DRAM.

In a multi-level memory that uses cache memory, the goal in designing the primary memory is to have a design that keeps up with the cache closest to it, and not necessarily the CPU. All modern computer memory is built from a collection of memory chips. These chips are usually organized into modules. In a byte-addressable memory, each memory module will have eight memory chips, for reasons to be explained. The use of memory modules allows an efficiency boost due to the process called "**memory interleaving**".


Suppose a computer with byte-addressable memory, a 32-bit address space, and 256 MB (2^{28} bytes) of memory. Such a computer is based on this author's personal computer, with the memory size altered to a power of 2 to make for an easier example. The addresses in the MAR can be viewed as 32-bit unsigned integers, with high order bit A_{31} and low order bit A_0 . Putting aside issues of virtual addressing (important for operating systems), we specify that only 28-bit addresses are valid and thus a valid address has the following form.

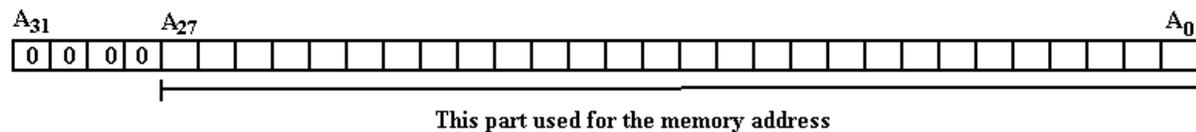

The memory of all modern computers comprises a number of modules, which are combined to cover the range of acceptable addresses. Suppose, in our example, that the basic memory chips are 4Mb (megabit) chips, grouped to form 4MB modules. The 256 MB memory would be built from 64 modules and the address space divided as follows:

- 6 bits to select the memory module as $2^6 = 64$, and
- 22 bits to select the byte within the module as $2^{22} = 4 \bullet 2^{20} = 4M$.

The question is which bits select the module and which are sent to the module. Two options commonly used are **high-order memory interleaving** and **low-order memory interleaving**. Other options exist, but the resulting designs would be truly bizarre. We shall consider only low-order memory interleaving in which the low-order address bits are used to select the module and the higher-order bits select the byte within the module. The advantage of low-order interleaving over high-order interleaving will be seen when we consider the principle of locality. Memory tends to be accessed sequentially by address.

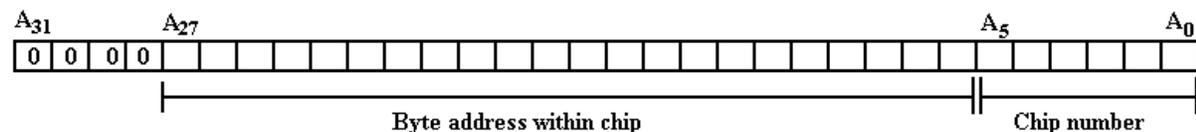

This low-order interleaving has a number of performance-related advantages. These are due to the fact that consecutive bytes are stored in different modules, thus byte 0 is in chip 0, byte 1 is in chip 1, etc. In our example

- Module 0 contains bytes 0, 64, 128, 192, etc., and
- Module 1 contains bytes 1, 65, 129, 193, etc., and
- Module 63 contains bytes 63, 127, 191, 255, etc.

Suppose that the computer has a 64 bit–data bus from the memory to the CPU. With the above low-order interleaved memory it would be possible to read or write eight bytes at a time, thus giving rise to a memory that is close to 8 times faster. Note that there are two constraints on the memory performance increase for such an arrangement.


- 1) The number of chips in the memory – here it is 64.
- 2) The width of the data bus – here it is 8, or 64 bits.

In this design, the chip count matches the bus width; it is a balanced design.

To anticipate a later discussion, consider the above memory as connected to a cache memory that transfers data to and from the main memory in 64–bit blocks. When the CPU first accesses an address, all of the words (bytes, for a byte addressable memory) in that block are copied into the cache. Given the fact that there is a 64–bit data bus between the main DRAM and the cache, the cache can be very efficiently loaded. We shall have a great deal to say about cache memory later in this chapter.


There is a significant speed advantage to low–order interleaving that is best illustrated with a smaller number of memory modules. Consider the above scheme, but with an eight–way low–order interleaved memory. The memory modules are identified by the low–order three bits of the address: A_2 , A_1 , A_0 . The modules can be numbered 0 through 7. Suppose that the memory is fabricated from chips with 80 nanosecond cycle time. Unlike the access time, which measures the delay from the address assertion to the data being loaded in the data buffer, the **cycle time** represents the minimum time between independent accesses to the memory. The cycle time has two major components: access time and recharge time. The recharge time represents the time required to reset the memory after a read operation. The precise meaning of this will become clear when we discuss DRAM.

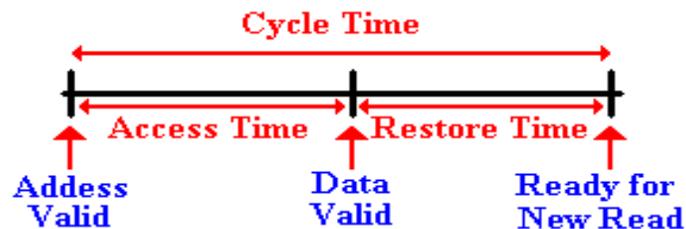Here is a timeline showing the access time and cycle time for a DRAM element. Here, the timings are specified for memory READ operations.



Suppose that this is an 8–chip module with the 80 nanosecond cycle time. The maximum data rate for reading memory would be one byte every 80 nanoseconds. In terms of frequency this would connect to a 12.5 MHz data bus. Recall that even a slow CPU (2 GHz) can issue one memory READ request every nanosecond. This memory is about 80 times too slow.

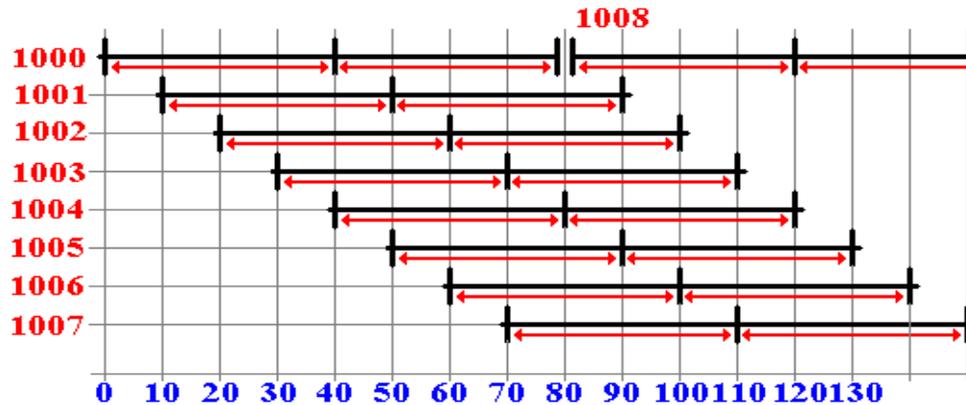We now implement the 8-way low order interleaving, using the memory with a cycle time of 80 nanoseconds and an access time of 40 nanoseconds (a bit fast). Suppose that the CPU reads in sequence the bytes from address 1000 through 1008. As is seen in the diagram below, the CPU can issue a READ command every 10 nanoseconds.



- At $T = 0$, the CPU issues a READ command for address 1000 in module 0.
- At $T = 10$, the CPU issues a READ command for address 1001 in module 1.
- At $T = 20$, the CPU issues a READ command for address 1002 in module 2.
- At $T = 30$, the CPU issues a READ command for address 1003 in module 3.
- At $T = 40$, the CPU issues a READ command for address 1004 in module 4.
Note that the data for address 1000 are ready to be transferred to the CPU.
- At $T = 50$, the CPU issues a READ command for address 1005 in module 5.
The data for address 1001 can be transferred to the CPU.
- At $T = 60$, the CPU issues a READ command for address 1006 in module 6.
The data for address 1002 can be transferred to the CPU.
- At $T = 70$, the CPU issues a READ command for address 1007 in module 7.
The data for address 1003 can be transferred to the CPU.
- At $T = 80$ module 0 has completed its cycle time and can accept a read from address 1008.
The data for address 1004 can be transferred to the CPU.

Here we have stumbled upon another timing issue, which we might as well discuss now. Note that the first value to be read is not ready for transfer until after 40 nanoseconds, the access time. After that one value can be transferred every ten nanoseconds.

This is an example of the two measures: latency and bandwidth. The **latency** for a memory is the time delay between the first request and the first value being ready for transfer; here it is forty nanoseconds. The **bandwidth** represents the transfer rate, once the steady state transfer has begun. For this byte-addressable memory, the bandwidth would be one byte every ten nanoseconds, or 100 MB per second.


Low-order memory interleaving was one of the earliest tricks to be tried in order to increase memory performance. It is not the only trick.

Selecting the Memory Word

In this paragraph, we use the term “word” to indicate the smallest addressable unit of primary memory. For most modern computers, this would be an eight-bit byte. We now revisit the mechanism by which the individual word (addressable unit) is selected.

Recall from our discussion of data formats that an N -bit unsigned binary number can represent a decimal number in the range from 0 through $2^N - 1$ inclusive. As examples, an 8-bit unsigned binary number can range from 0 through 255, a 12-bit can range from 0 through 4095, a 20-bit can range from 0 through 1,048,575 ($2^{20} = 1,048,576$), and a 32 bit number from 0 through 4,294,967,295 ($2^{32} = 4,294,967,296$).

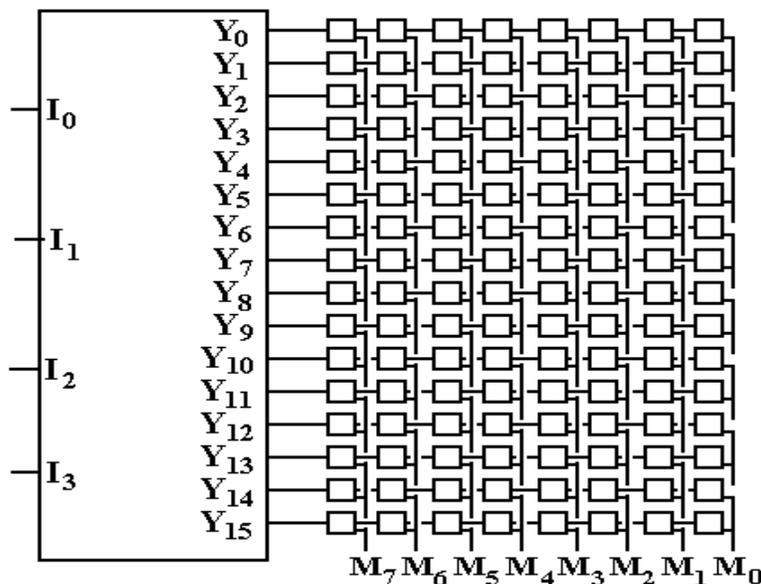Recall also our earlier discussion of decoders. A typical decoder is an N -to- 2^N device, basically converting the unsigned binary code to its decimal equivalent. The example for this discussion will be a 4-to-16 decoder. While rather small, it is large enough to make the point. When used as a decoder for memory addresses, such a device is called an **address decoder**.



Suppose that the 4-bit address 1011 is issued to the memory. The decoder output Y_{11} is asserted and the eight memory elements associated with that address are activated. Eight bits are either transferred to the selected byte or read from the byte. Note that the structure of the decoder is the reason that memory size is given in powers of 2; 1KB = 2^{10} bytes, etc.

While the above is a perfectly good implementation of a 16-word memory, the single decoder scheme does not scale well. Consider a memory that is rather small by today's standards. A 64MB memory would require a 26-to-67,108,864 decoder, as $64 \text{ MB} = 64 \cdot 1048576 \text{ bytes} = 26 \cdot 2^{20} \text{ bytes} = 2^{26} \text{ bytes}$. While such a decoder could be built, it would be rather large and unacceptably slow. Memories with fewer addressable units have smaller address decoders, which tend to be faster.

When we revisit SRAM in the chapter on the memory hierarchy, we shall comment on the fact that the cache memories tend to be small. This is partly due to the fact that address decoding for small memories is faster. A standard Pentium has a split L1 cache (note error in Williams' text on page 125), with two 16 KB caches each requiring a 14-to-16,384 decoder. As we shall see, even this is probably implemented as two 7-to-128 decoders.

Capacitors and DRAM

While it is quite possible to fabricate a computer using SRAM (Static RAM, comprising flip-flops), there are several drawbacks to such a design. The biggest problem is cost, SRAM tends to cost more than some other options. It is also physically bigger than DRAM, the principle alternative. Here are the trade-offs.

SRAM is physically bigger, more costly, but about ten times faster.

DRAM is physically smaller, cheaper, and slower.

Note that memory options, such as mercury delay lines, that are bigger, more costly, and slower have quickly become obsolete. If the memory is slower, it must have some other advantage (such as being cheaper) in order to be selected for a commercial product.


We are faced with an apparent choice that we do not care for. We can either have SRAM (faster and more expensive) or DRAM (slower and cheaper). Fortunately, there is a design trick that allows the design to approximate the speed of SRAM at the cost of DRAM. This is the trick called “cache memory”, discussed later in our chapter on the memory hierarchy.

DRAM (Dynamic RAM) employs a **capacitor** as its key storage element. A capacitor is a device that stores electronic charge. The flow of electronic charge is called “**current**”. There are many uses for capacitors in alternating current circuits and radios; our interest here is focused on its ability to store charge.

Introductory physics courses often discuss electric charge and current in terms borrowed from water flow in pipes. There is a very familiar hydraulic analog of a capacitor; it is the tank on a standard flush toilet. During normal operation, the tank holds water that can be released as a significant flow into the toilet bowl. The tank is then slowly refilled by a current of water through the feed lines. Another example is seen in the electronic flashes found on most cameras and many cell phones. The battery charges the capacitor with a small current. When the capacitor is charged it may be quickly discharged to illuminate the flash bulb.

All toilet tanks leak water; the seal on the tank is not perfect. At intervals, the float mechanism detects the low water level and initiates a refilling operation. There is an analogous operation for the capacitor in the DRAM; it is called “**refresh**” which occurs during the **refresh cycle**.

The basic mechanism is simple. Each capacitor can hold a charge up to a fixed maximum, determined by a measure called its **capacitance**. While the charge on a capacitor is hard to measure directly, it is easy to measure indirectly. Capacitance is defined as the charge stored per unit voltage. If the capacitor has capacitance **C**, stores a charge **Q**, and has a voltage **V**, then $C = Q/V$ by definition. Since the capacitance of the DRAM memory cell is known, measuring the voltage across the capacitor can determine the charge stored.

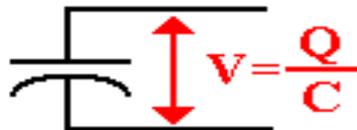


Since the DRAM cell is a binary unit, there are only two values stored: 0 volts (no charge) and full voltage (full charge). The refresh cycle measures the voltage across the capacitor in every memory cell. If above a certain value, it must have been fully charged at some point and lost its charge. The refresh circuitry then applies full voltage to the memory cell and brings the charge back up to full value. Below a given value, the charge is taken as zero, and nothing is done.

All modern memory is implemented as a series of modules, each of which comprises either eight or nine memory chips of considerable capacity. Each module now has the refresh logic built into it, so that the CPU does not need to manage the DRAM.


Another DRAM Organization

The apparently simple memory organization shown a few pages back calls for a single large decoder. As mentioned at the time, this large decoder would present problems both in size and time delays. One way to solve this problem is to treat the memory as a two-dimensional array, with row and column indices. This reduces the problem of an N to 2^N decoder to two $(N/2)$ to $2^{(N/2)}$ decoders; as in one 26-to-67,108,864 decoder vs. two 13-to-8,192 decoders.

There is a bit of a problem with this organization, but that is easily solved. Consider the figure presented a few pages back. It shows a 16-by-8 memory. A 64 MB memory in that style would be implemented as a singly dimensioned array of 67,108,864 entries of 8 bits each. How can this be represented as a number of square arrays, each 8,192 by 8,192, requiring two 13-to-8,192 decoders? The answer is to have a 67,108,864 byte (64MB) memory module comprising eight 67,108,864 bit (64 Mb) memory chips, along with the control circuitry required to manage the memory refresh. The figure below, copied from an earlier chapter in this textbook, shows the arrangement of such a module. Note that there are nine chips in this module: one controller chip and eight memory chips.

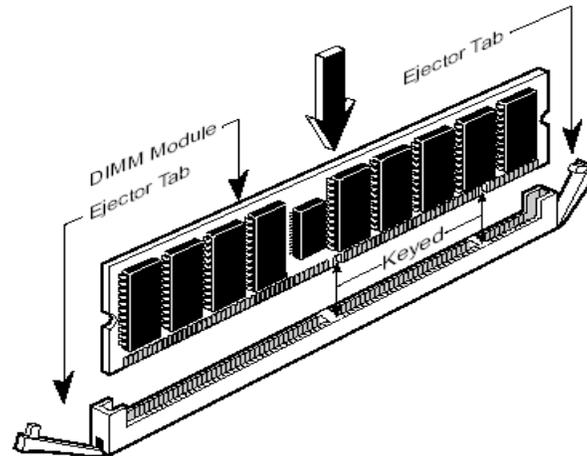


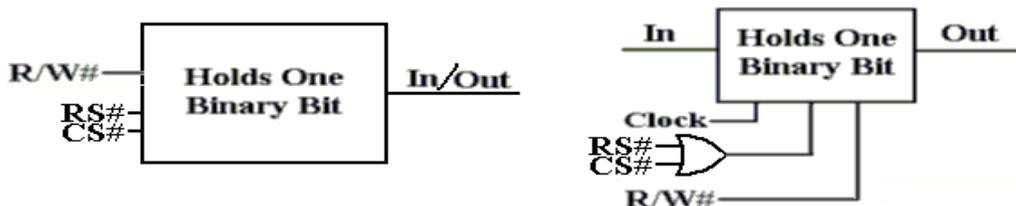In order to use this modular array of single bit chips, we must modify the basic memory cell to accept two select signals, a row select and a column select. This is done easily.




The figure at the left shows the new logical depiction of the memory cell, with its two select signals. The figure at right shows the modification of the simple memory cell to accommodate this design. If $RS\# = 0$ and $CS\# = 0$, then the cell is selected; otherwise not.

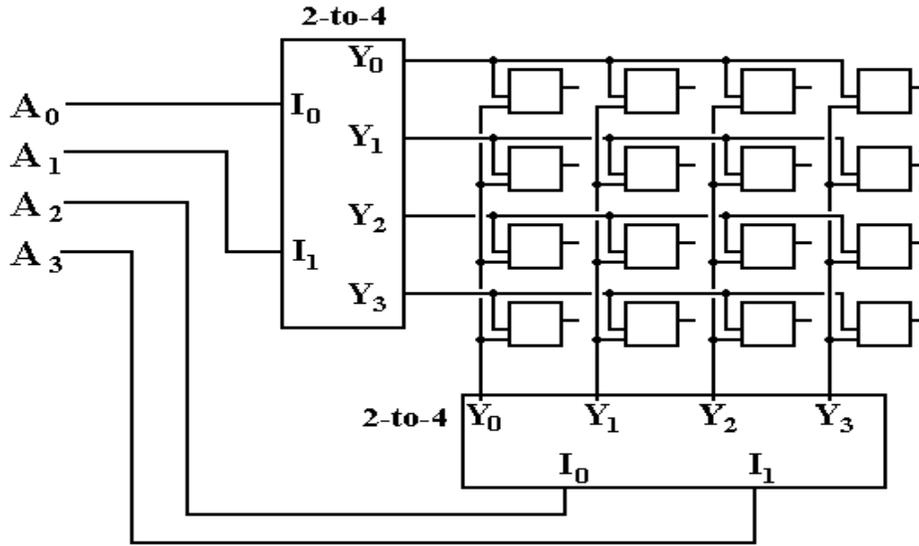Here is a diagram of a 16-bit memory array, organized in the two-dimensional structure. Note that the R/W# and memory cell I/O lines have been omitted for the sake of clarity.



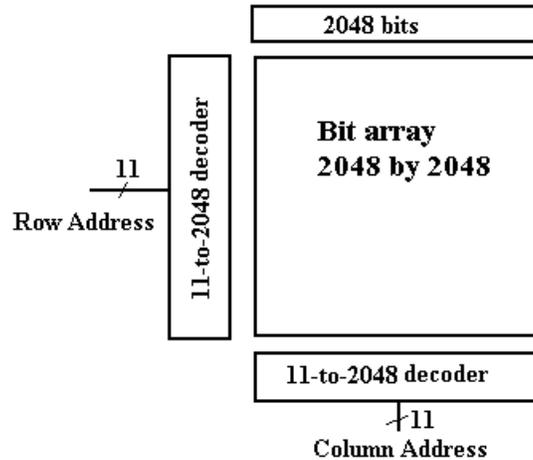
Imagine a 4 MB (megabyte) memory module. It would hold eight 4 Mb (megabit) memory chips, each organized as a 2,048 by 2,048 array of single bits. Note the 2048 bit array at the top of the square array. This will be explained shortly. There are two 11-to-2048 decoders.



We now come to a standard modification that at first seems to be a step back. After describing this modification, we show that it does not lead to a decrease in memory performance. The modification is a result of an attempt to reduce the pin count of the memory chip.

Each chip is attached to a mounting board through a series of pins. For a memory chip, there would be one pin for the bit input/output, pins for the address lines, pins for the power and ground lines, and pins for the control lines.

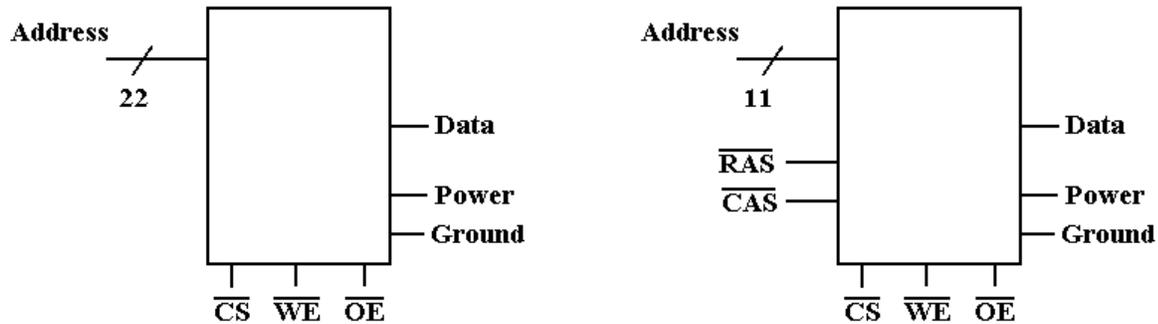Consider now the two-dimensional memory mentioned above. What pins are needed?



Pin Count

Address Lines	22
Row/Column	0
Power & Ground	2
Data	1
Control	3
Total	28

Address Lines	11
Row/Column	2
Power & Ground	2
Data	1
Control	3
Total	19

Separate row and column addresses reduce the number of pins required from 28 to 19, but require two cycles to specify the address. First RAS# is asserted and the 11-bit row address is placed on the address lines. Then CAS# is asserted and the 11-bit column address is placed on the address lines. The following table describes the operation of some of the control signals.

CS#	RAS#	CAS#	WE#	Command / Action
1	d	d	d	Deselect / Continue previous operation
0	1	1	d	NOP / Continue previous operation
0	0	1	1	Select and activate row
0	1	0	1	Select column and start READ burst
0	1	0	0	Select column and start WRITE burst
0	0	0	d	Error condition. This should not occur.

In the above table, “d” stands for “don’t care”. For example, when CS# = 1, the action does not depend on the values of RAS#, CAS#, or WE#. When CS# = 0, RAS# = 1, and CAS# = 1, the action does not depend on the value of WE#.

The CPU sends the 11-bit row address first and then send the 11-bit column address. At first sight, this may seem less efficient than sending 22 bits at a time, but it allows a true speed-up. We merely add a 2048-bit row buffer onto the chip and when a row is selected; we transfer all 2048 bits in that row to the buffer at one time. The column select then selects from this on-chip buffer. Thus, the access time now has two components:

- 1) The time to select a new row, and
- 2) The time to copy a selected bit from a row in the buffer.

Definition: A **strobe** is a signal used to indicate that an associated signal or set of values is valid. **RAS#** stands for **Row Address Strobe**; **CAS#** stands for **Column Address Strobe**. When RAS# is asserted, the address lines contain a valid row address. When CAS# is asserted, the address lines contain a valid column address. Recall that each of these signals is asserted low.

Parity Memory

In a byte-addressable memory, each addressable unit has eight data bits. Each data bit is stored in the basic memory cell in some electrical form. For modern DRAM, the bit is stored as a charge on a capacitor. Because of this, the value stored can be changed randomly by environmental factors such as cosmic rays or discharge of static electricity.

Suppose that you, as a student had a course grade stored in the computer as **0100 0001** (ASCII code for 'A'), and that a random event changed that to **0100 0011** (ASCII code for 'C'). As a student, you might not be pleased at the random drop in your otherwise perfect 4.0 average. Such an event is called a “**single bit error**”, because one bit in the 8-bit entry has been unintentionally changed. Double bit errors can also occur, but simple probability arguments show that these are much less likely.

Memory parity is a simple mechanism for detecting single-bit errors. In fact, this mechanism will detect any odd number of errors, and fail to detect any even number of errors. As the one-error case is most common, this is often a sufficient protection. We also note that parity memory is most often seen on large server computers that are expected to remain running for considerable periods of time. Your author recently spoke with a manager of an IBM mainframe that had been running for over seven years without a problem.

The idea behind simple parity is to add a ninth bit to every byte, called the **parity bit**. The number of 1 bits in the 9-bit entry is then set according to the desired policy. For even parity memory, the count of 1 bits should be an even number (including 0). For odd parity memory, the count of 1 bits should be an odd number. Odd parity is often favored, because this requires there to be at least one 1 bit in the 9-bit entry.

Consider the above example. The value to be stored in the 8-bit byte is **0100 0001** (ASCII code for 'A'). As that is, it has two bits with value 1. The parity bit must be set to 1, so that there are an odd number of bits in the 9-bit entry. Here is a depiction of what is stored.

Bit	P	7	6	5	4	3	2	1	0
	1	0	1	0	0	0	0	0	1

Suppose now that the 9-bit entry **1 0100 0001** has a single bit changed. For the bit error discussed above, the value becomes **1 0100 0011**, which has an even number of 1 bits. An error has occurred and the value stored is probably corrupted. Note that the simple parity scheme cannot localize the error or even insure that it is not the parity bit that is bad; though the odds are 8-to-1 that it is a data bit that has become corrupted.


Notice that any bit error can be corrected if it can be located. In the above example, bit 1 in the word as assumed the wrong value. As there are only two possible bit values, knowing that bit 1 is wrong immediately leads to its correct value; the corrupted value is **1**, so the correct value must be **0**.

Modern commercial systems, such as the IBM z/Series Mainframes, adopt a more complex error detection strategy, called **SECDEC** (**S**ingle **E**rror **C**orrecting, **D**ouble **E**rror **D**etection), which performs as advertised by localizing any single bit error, allowing it to be corrected. The SECDED strategy assigns four parity bits to each 8-bit datum, requiring 12 bits to be stored. This course will not cover this strategy; we just mention it to be complete.


Evolution of modern SDRAM

The earliest personal computer (the IBM PC) had a CPU with a clock frequency of 4.77 MHz, corresponding to a clock period of somewhat over 200 nanoseconds. This was about the cycle time of the existing semiconductor memory. As the CPU accesses memory on average every two clock pulses, there was a fairly good match between CPU speed and memory speed.

Beginning in the 1980's, CPU speeds began to increase markedly while the speed of the basic memory unit remained the same. Most early experiments with dramatically different memory implementations, such as GaAs (Gallium Arsenide) showed some promise but, in the end, presented significant difficulties and were not adopted. The only solution to the problem was to change the large-scale architecture of the memory system. The big changes occurred in the interface between the CPU and the memory; the DRAM core (pictured below) did not change.

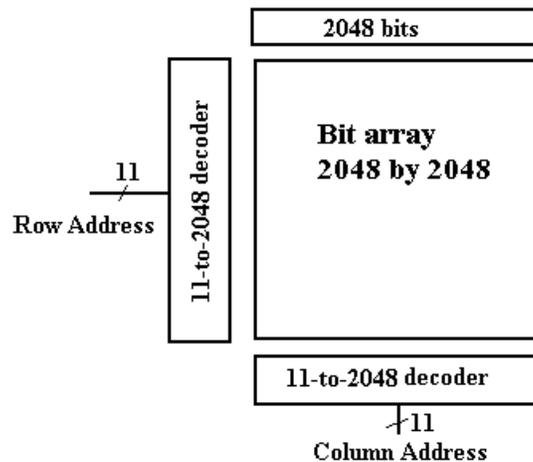

At the time that we pick up the narrative of memory evolution, the memory chips were already organized as two-dimensional arrays, as seen in the figure above copied from a few pages earlier. Most of the nature of the evolution relates to the top box labeled “2048 bits”. As always, the memory chips will be mounted in an 8-chip or 9-chip (for parity memory) module. In what follows, we assume no parity, though that does not change the basics of the discussion.

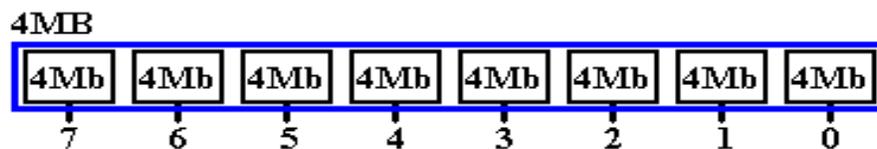

We begin by examining addresses issued to this chip. These range from 0 through 4,194,303. We want to consider four consecutive memory accesses, beginning say at address 10,240. The addresses are 10240, 10241, 10242, and 10243. Each of these addresses is sent to all eight chips in the module to cause access to the corresponding bit. If we assume a standard split between row and column addresses, all four addresses reference row 5 (each row in a chip contains 2048 bits and $10240/2048 = 5$). The references are to columns 0, 1, 2, and 3. In two-dimensional coordinates, the references are (5,0), (5,1), (5,2), and (5,3).

We shall now examine the timings for a sequence of memory READ operations; in each of these the CPU sends an address to the memory and reads the contents of that byte.

We begin with a description of the standard DRAM access. Note the delay after each access. This serves to allow the bit lines from the memory cells in the row selected by the row address to the sense amplifiers in the output buffer to recharge and be ready for another read cycle. A **sense amplifier** serves to convert the voltages internal to the memory chip to voltages that can be placed on the memory bus and read by the CPU. Here is the sequence.

Byte 10240 is accessed.

1. The row address is set to 5, and RAS# is asserted.
2. The column address is set to 0, and CAS# is asserted.
3. The value of byte 10240 is made available on the output lines.
4. The memory waits for the completion of the cycle time before it can be read again.

Byte 10241 is accessed.

1. The row address is set to 5, and RAS# is asserted.
2. The column address is set to 1, and CAS# is asserted.
3. The value of byte 10241 is made available on the output lines.
4. The memory waits for the completion of the cycle time before it can be read again.

Byte 10242 is accessed.

1. The row address is set to 5, and RAS# is asserted.
2. The column address is set to 2, and CAS# is asserted.
3. The value of byte 10242 is made available on the output lines.
4. The memory waits for the completion of the cycle time before it can be read again.

Byte 10243 is accessed.

1. The row address is set to 5, and RAS# is asserted.
2. The column address is set to 3, and CAS# is asserted.
3. The value of byte 10243 is made available on the output lines.
4. The memory waits for the completion of the cycle time before it can be read again.

One will note a lot of repetitive, and useless, work here. The same row is being read, so why should it be set up every time? The answer is that the early memory access protocols required this wasted effort. As a result, the memory interface was redesigned.

One of the earliest adaptations was called **page mode**. In page mode, the array of 2048 bits above our sample chip would hold 2048 sense amplifiers, one for each column. In page mode, data from the selected row are held in the sense amplifiers while multiple column addresses are selected from the row. In a 16 MB DRAM with 60 nanosecond access time, the page mode access time is about 30 nanoseconds. Most of the speed up for this mode is a result of not having to select a row for each access and not having to charge the bit lines to the sense amplifiers.

In hyperpage devices, also called **EDO (Extended Data-Out)** devices, a new control signal was added. This is **OE# (Output Enable, asserted low)**, used to control the memory output buffer. As a result, read data on the output of the DRAM device can remain valid for a longer time; hence the name “extended data-out”. This results in another decrease in the cycle time.

In EDO DRAM, the row address is said to be “**latched in**” to the memory chip’s row address. Basically, a latch is a simpler variant of a flip–flop, and an address latch is one that holds an address for use by the memory chip after it is no longer asserted by the CPU. With the row address latched in, the EDO can receive multiple column addresses and remain on the same row.

The next step in DRAM evolution is the **BEDO (Burst Extended Data–Out)** design. This builds on EDO DRAM by adding the concept of “bursting” contiguous blocks of data from a given row each time a new column address is sent to the DRAM device. The BEDO chip can internally generate new column addresses based on the first column address given. By eliminating the need to send successive column addresses over the bus to drive a burst of data in response to each CPU request, the BEDO device decreases the cycle time significantly.

Most BEDO timings are given in terms of memory bus cycles, which we have yet to discuss fully. A typical BEDO device might allow for a four–word burst. One a standard EDO device each access might take five bus clock cycles; we denote the four accesses by “5–5–5–5” to indicate that each of the four accesses takes the same amount of time. In a BEDO device, the burst timing might be “5–2–2–2”; the first access takes five memory bus clock cycles, but initiates a burst of three more words, each available two clock cycles after the previous word.

Another step in memory development, taken about the same time as the above designs, has to do with the basic structure of the memory chip. The memory chip illustrated twice above holds a square array of single bits. This is called a **single bank**. The chip delivers one bit at a time. With the increase of transistor density on a memory chip, it became possible to have multiple banks within the chip. Each memory bank is an independent array with its own address latches and decoders (though using the same row and column addresses). Consider a memory chip with four internal banks. This chip will deliver four bits per access. A module holding eight of these chips can deliver 32 bits per access; that is four bytes.

The use of multiple banks per chip is not to be confused with burst mode, as in BEDO. The two design options can complement each other. Consider a BEDO module with two chips, each having four banks. The module would deliver 8 bits, or 1 byte, per access. Now suppose that the byte at address 10240 is requested. The appropriate memory bank will be accessed. For a 5–2–2–2 memory, this would happen:

After 5 memory bus clock cycles, the byte at address 10240 would be available.

After 2 more memory bus clock cycles, the byte at address 10241 would be available.

The entire burst of four bytes would have been delivered in 11 clock cycles.

The next design, **SDRAM (Synchronous DRAM)**, is considered the first device in a line of commodity DRAM devices. This design differs from the EDO and BEDO devices in three significant ways: the SDRAM has a synchronous device interface, all SDRAM devices contain multiple internal banks, and the SDRAM device is programmable as to burst length and a few other advanced parameters allowing for faster access under special conditions.

One of the advantages of a synchronous DRAM unit is that it operates on a standard internal clock. The CPU can latch the address, control signals, and (possibly) data into the input latches of the memory device and then continue other processing, returning to access the memory if needed. On a write to memory, the CPU just latches the address, control signals, and output data into the memory unit and moves on.

In SDRAM, the memory is synchronized to the system bus and can deliver data at the bus speed. The earlier SDRAM chips could deliver one data item for every clock pulse; later designs called DDR SDRAM (for Double Data Rate SDRAM) can deliver two data items per clock pulse. Double Data Rate SDRAM (DDR-SDRAM) doubles the bandwidth available from SDRAM by transferring data at both edges of the clock.


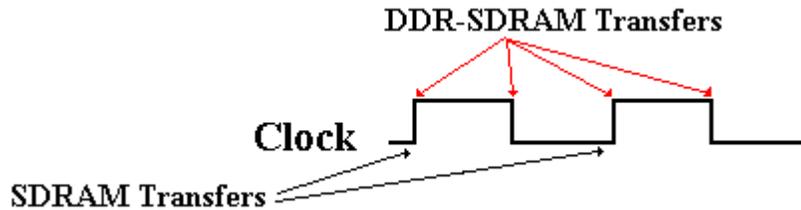


Figure: DDR-SDRAM Transfers Twice as Fast

There are two newer versions of DDR SDRAM, called DDR2 and DDR3. Each of these adds new features to the basic DDR architecture, while continuing to transfer twice per memory bus clock pulse. The DDR3 design has become quite popular, appearing on a commodity netbook device by Acer that retails for \$300 to \$600 depending on the wireless plan chosen. As indicated these devices are sold at stores, such as AT&T and Sprint, that sell cell phones.

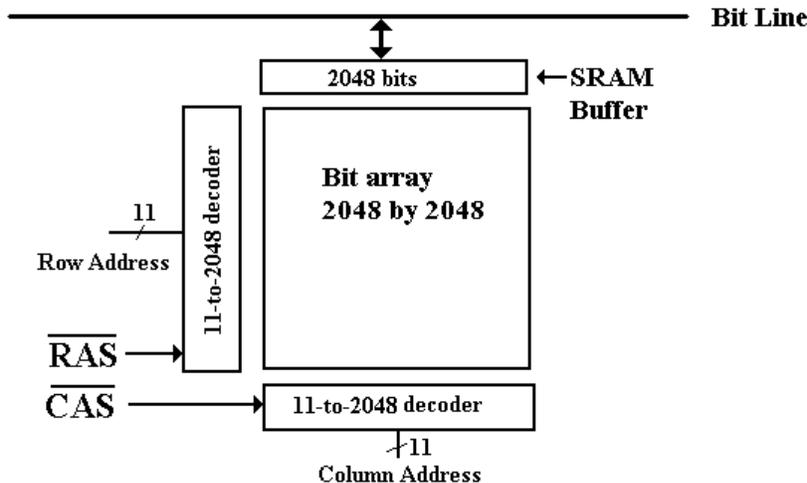Some manufacturers have taken another step in the development of SDRAM, attaching a SRAM buffer to the row output of the memory chip. Consider the 4Mb (four megabit) chip discussed earlier, now with a 2Kb SRAM buffer.



In a modern scenario for reading the chip, a Row Address is passed to the chip, followed by a number of column addresses. When the row address is received, the entire row is copied into the SRAM buffer. Subsequent column reads come from that buffer.

JEDEC Standards

Modern computer memory has become a commercial commodity. In order to facilitate general use of a variety of memory chips, there have been evolved a number of standards for the memory interface. One of the committees responsible for these standards is **JEDEC**. Originally, this stood for “*Joint Electron Device Engineering Council*” [R008, page 332], but now it is used as a name itself. DRAM standardization is the responsibility of the JEDEC subcommittee with the exciting name “JC-42.3”.

One Commercial Example

As an example, we quote from the Dell Precision T7500 advertisement of June 30, 2011. The machine supports dual processors, each with six cores. The standard memory configuration calls for 4GB or DDR3 memory, though the system will support up to 192 GB. The memory bus operates at 1333MHz (2666 million transfers per second). If it has 64 data lines to the L3 cache (following the design of the Dell Dimension 4700 of 2004), this corresponds to $2.666 \cdot 10^9$ transfers/second \cdot 8 bytes/transfer $\approx 2.13 \cdot 10^{10}$ bytes per second. This is a peak transfer rate of 19.9 GB/sec. Recall that $1\text{GB} = 2^{30}$ bytes = 1,073,741,824 bytes.

References

- [R008] Bruce Jacob, Spencer W. Ng, and David T. Wang, *Memory Systems: Cache, DRAM, Disk*, Morgan Kaufmann, 2008, ISBN 978 – 0 – 12 – 379751 – 3.
- [R009] Betty Prince, *High Performance Memories*, John Wiley & Sons, Ltd., 1999, ISBN 0 – 471 – 98610 – 0.